

OCTOBER, 1958

*Anniversary Issue*

*Amateur Radio*



25



YEARS OF SERVICE TO THE AMATEUR

1933-1958

PRICE:

1/6

# "HAM" RADIO SUPPLIERS

(KEN MILLBOURN, PROP.)

5A MELVILLE STREET, HAWTHORN, VICTORIA

North Balwyn Tram Passes Corner, near Vogue Theatre.

Phone: WM 6465

Money Orders and Postal Notes payable North Hawthorn P.O. Packing Charge on all goods over 10 lbs. in weight, 5/- extra

## NOTE THESE VALVE PRICES

Look at these Bargain		Priced NEW VALVES—	
1A5	5/-	6J5	7/6
1B5	2/6	6J5GT	7/6
1H6	3/6	6J6	12/6
1K4	5/-	6K6	7/6
1K5	2/6	6L7	10/-
1P5	5/-	6N7	10/-
1Q5	5/-	6N8	15/-
1R5	10/-	68C7	10/-
1S5	10/-	68F7	12/6
1T4	10/-	68J7GT	12/6
2A5	10/-	68L7	12/6
2X2	7/6	68N7GT	12/6
3Q5	5/-	68S7	12/6
3T4	12/6	6U7	10/-
3U4G	12/6	68H7G	4/-
5V4G	15/11	6V6GT	12/6
6AG5	10/-	6X5	10/-
6AJ5	7/6	7A6	5/-
6AG6	12/6	7A8	3/6
6B4	12/6	7C5	5/-
6C8	7/6	7E5	2/6
6F6G	10/-	7E6	3/6
	10/-	7W7	2/6
1C7	3/- each or 7 for £1		
2X7	7/6 each or 3 for £1		
6AC7	3/11 each or 8 for £1		
6C4	5/- each, or 5 for £1		
6H6G5	£1 a dozen		
6K7G	5/- each or 5 for £1		
6M7	5/- each or 5 for £1		
68H7GT	4/- each or 6 for £1		
7C7	2/6 each or 10 for £1		
7F7	5/- each or 5 for £1		
954, 955	5/- ea. or 5 for £1		

New Valves—VR55/EF39, direct replacement for 6U7. High gain, low noise, 5/- each or five for £1.

5CP1 5" Cathode Ray Tube	£3/10/0
7BP7 7" Cathode Ray Tube	10/-
EF50 and Socket	6/- the two

## THIS MONTH'S SPECIALS

Two-Gang Condensers, Broadcast	12/6
Pi Type Co-ax Plugs and Sockets	4/-
Co-ax Cable, 72 ohms, in 10-yard lengths	£1, or 2/- yard
BC733D Crystal Locked Receiver, tuning range 108-170 Mc. 1F. 6.9 Mc. Valve line-up: three 717As, two 12SG7s, one 12SH7, two 12SR7s, one 12SQ7, one 12A6. Also contains six miniature relays. Packed ready for rail. Bargain at £4/9/6	
Six-Second Soldering Irons and Transformers, three only to clear. Well known make.	£4/10/0

Meters—0-1 Ma. Scaled 0-80. Few only	30/-
Meters—0-30 Ma., 2 1/2" round type, American	40/-
Meters—0-100 Ma., 2" square, scaled 0-300, new	£1
Meters—0-0.35 amp. R.F. F86 and 101 type	10/-
P.M.G. Key Switches, two-way	10/0
Two-way Toggle Switches, S.F.D.T.	5/- each
1958 Call Books now in stock, 5/-	Log Books also available.

## No. 128

### PORTABLE TRANSCEIVERS

Frequency range: 2 to 4.5 Mc. Nine miniature Valves (1.4v. series), 0-500 microamp. Meter, Less Crystals. BARGAIN: £7/7/6.

APN1 Altimeter. Contains unit suitable for Wobulator. Complete with valves and genemotor	£6
Co-ax Cable, 98 ohms, in 100 yard rolls. £7/10/0 per 100 yard roll, or 1/9 yard.	
Co-ax Cable, 100 ohm, any length	2/- yard
Co-ax Plugs and Sockets, American Ampenol	5/- pair
Co-ax Right-Angle Plugs, American Ampenol	2/6 each
Command Receiver Flexible Drives, 12 ft. long	10/-
Relays—522 type, 5000 ohm	£1
Relays—522 type, aerial change-over	£1
U.S.A. I.F.F. Units, complete with Valves and Genemotor. £5/17/6. Less Genemotor, £4/17/6.	
AR8 Vernier Dials, new	30/-
APX1 24v. Shunt Motors, ideal for Small Beams, Works on A.C. new	£1/10/0
APX1 Chassis, top deck, containing 28 Miniature Ceramic 7-pin Valve Sockets, Condensers, Resistors, etc., etc. A good buy at	£2/5/0; postage 5/- extra
Local Valve Sockets	1/- each
Teletron Octal Valve Sockets	1/- each
24 volt to 230 volt A.C. Inverters, approx. 50 watts	£10
Type "S" Power Supply, 230v. A.C. Good condition	£25
AT21 Power Supply, 230 volt A.C. Good condition	£25
No. 19 Genemotors	£2/10/0

FOR OTHER BARGAINS—SEE PAGE 44 OF THIS ISSUE

## CRYSTALS

Following is a list of Crystal Frequencies available for immediate delivery. £2 each—

2000 Kc.	4535 Kc.	6200 Kc.	7116 Kc.	7930 Kc.
2096.25 Kc.	4600 Kc.	6400 Kc.	7125 Kc.	8014 Kc.
2103.1 Kc.	4700 Kc.	6487.92 Kc.	7163 Kc.	8015 Kc.
2112.5 Kc.	5000 Kc.	6522.9 Kc.	7171 Kc.	8017 Kc.
2442.5 Kc.	5020 Kc.	6525 Kc.	7198 Kc.	8018 Kc.
2524 Kc.	5095 Kc.	6530 Kc.	7275 Kc.	8019 Kc.
2600 Kc.	5166 Kc.	6547 Kc.	7300 Kc.	8050 Kc.
2990 Kc.	5410 Kc.	6550 Kc.	7325 Kc.	8161.53 Kc.
3055 Kc.	5435 Kc.	6625 Kc.	7400 Kc.	8171.25 Kc.
3395 Kc.	5450 Kc.	6650 Kc.	7450 Kc.	8200 Kc.
3450 Kc.	5456 Kc.	6830 Kc.	7487 Kc.	8284.6Kc.
3577 Kc.	5500 Kc.	6900 Kc.	7500 Kc.	8290 Kc.
3655 Kc.	5530 Kc.	6960 Kc.	7535 Kc.	8325 Kc.
4055 Kc.	5700 Kc.	7003 Kc.	7587.5 Kc.	8488 Kc.
4096.6 Kc.	5702.1 Kc.	7004 Kc.	7888 Kc.	8678.85 Kc.
4285 Kc.	5744.44 Kc.	7010 Kc.	7890 Kc.	10000 Kc.
4509 Kc.	5770 Kc.	7032.6 Kc.	7920 Kc.	10515 Kc.
4525 Kc.	6100 Kc.	7080 Kc.	7925 Kc.	10536 Kc.
3.5 Mc. Miniature Marker Crystal and Socket				£2/10/0
455 Kc. Crystals, few only at				£3

**EDITOR:**

R. W. HIGGINBOTHAM, VK3RN.

**TECHNICAL EDITOR:**

K. E. PINCOTT, VK3AFJ.

**PUBLICATIONS COMMITTEE:**

G. W. BATY, VK3AOM.

G. BILLS-THOMPSON, VK3AHN.

S. T. CLARK, VK3ASC.

J. C. DUNCAN, VK3VZ.

R. S. FISHER, VK3OM.

V. M. JONES, VK3YE.

J. G. MARSLAND, VK3NY.

**ADVERTISING REPRESENTATIVE:**LEATRICE TOUZEAU,  
96 Collins St., Melbourne, C.I.  
Telephone: MF 4505.**PRINTERS:**"RICHMOND CHRONICLE,"  
Shakespeare St., Richmond, E.I.  
Telephone: JB 2419.

MSS. and Magazine Correspondence should be forwarded to the Editor, "Amateur Radio," C.O.R. House, 191 Queen Street, Melbourne, C.I., on or before the 8th of each month.

Subscription rate in Australia is 18/- per annum, in advance (post paid) and A&I/1/- in all other countries.

Wireless Institute of Australia  
(Victorian Division) Rooms' Phone  
Number is MY 1087.

**THE CONTENTS**

The W.I.C.E.N. Communicator	3
An Experimental High Frequency Transistor Portable Superhet Receiver	6
75 Years of "Amateur Radio"	9
The TA2 Special	11
The Improved Dipper	13
Amateur Television—Part Eight	19
Know Your Own W.I.A. Division New South Wales	27
VK2WI—Headquarters Station of the VK2 Division and Central Control Station of W.I.C.E.N. in New South Wales	28
The New South Wales Division, W.I.A.	30
Applications of the Grid Dip Oscillator	33
Meet the Other Amateur and His Station—Ian Nichols, VK7ZZ	41
Binding "Amateur Radio"	41
Book Review: "Basic Mathematics for Radio and Electronics"	41
Rules: 1958 "CQ" World-Wide DX Contest	43
Hints and Kinks: Splicing 300 Ohm Ribbon	43
Correspondence	45
I.T.U. Fund Donations	47
Prediction Chart for October '58	47
DX	48
SWL	49
VHF	51
Notes	52
Contest Calendar	52

**AMATEUR RADIO**

JOURNAL OF THE WIRELESS INSTITUTE OF AUSTRALIA

Published by the Wireless Institute of Australia,  
C.O.R. House, 191 Queen Street,  
Melbourne, C.I.

**EDITORIAL****TWENTY-FIVE YEARS OF AGE**

On 1st October, 1933—twenty-five years ago—the first issue of "Amateur Radio", published by the Victorian Division of the Wireless Institute of Australia, went to press as the official organ of the Victorian Division of the Wireless Institute of Australia and the Royal Australian Air Force Wireless Reserve. Such was the enthusiasm with which it was received, that within two months it became the official organ of the Wireless Institute of Australia in all States in conjunction with the R.A.A.F. Wireless Reserve.

With the support of advertisers and its hard-working, far-sighted enthusiastic Committee, it continued in publication in octavo format up until the outbreak of World War II, bringing to the Australian Amateur a glossary of information pertinent to the hobby of Amateurs and providing a medium by which Amateurs could express their views and know what was going on in their unique field of communication.

During the years of the War, "Amateur Radio" continued in publication in a roneoed form and at the conclusion of hostilities came into print again in its present quarto format.

Between the lines is history! History of the work of an ardent few who have zealously sacrificed their private time in an honorary capacity to maintain its publication. With the advancing years and increasing interest in Amateur transmitting, the magazine has increased its standard until today—its 25th birthday—is seen its finest issue.

Throughout its twenty-five years of publication can be found an historical record of the pursuits of Amateur Radio in Australia; the writings of Amateurs who became known the world over and who are


now "silent keys"; men whose activities made milestones in the glorious progress of communication by radio waves; and others who are still active Amateurs and whose names appear in its columns symbolising a never-dying interest in the continuation of the work done by those who went before.

It is not possible to list all those who have done so much to maintain the publication of "Amateur Radio" over the past twenty-five years. To each and every one goes due credit for the work he has done. But one outstanding Amateur known to many who has devoted twenty-five years to its cause is Jim Marsland, VK3NY. From participating in its work from the inaugural issue to editing it and looking after its finances throughout its history, Jim Marsland has unselfishly devoted a virtual life-time and has paved the way for those who will ultimately follow in his footsteps to maintain the only Amateur Radio publication in Australia to a standard undreamed of in its early years.

The Wireless Institute of Australia is proud of its publication. It takes this opportunity of thanking all those people—the Advertisers, the Committee, the correspondents, the technical article writers, the printers, and the Victorian Division of the W.I.A. which has provided the finance to maintain it in publication. "Amateur Radio" today is a well established journal, selling through all leading booksellers and reaching out through members of the W.I.A. to readers all over the world. With new ideas and modern processes the Wireless Institute of Australia looks forward to another twenty-five years of publication for and on behalf of the Amateur Service in Australia.

FEDERAL EXECUTIVE.

# QTC1

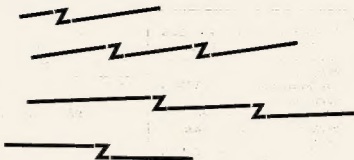

*Hearty Congratulations & 73!*  
*to WIA on 25th ANNIVERSARY—*  
*de*



***Simon Gray Pty. Ltd. & Principals:—***

28 Elizabeth St., Melbourne

***World-famous names when highest possible quality is discussed***

**Messrs. H. J. LEAK & Co. Ltd.**

Stereo & Single Channel Amplifiers & Pickups

**WHARFEDALE Loudspeakers**

Supreme for every Loudspeaker Application

**ORTOFON**

Stereo & Single Channel Pickups

**SIMON**

"Cadenza" Ribbon Microphones

**PARTRIDGE**

World-famous Transformers

**BURNE-JONES**

Stereo & Standard Pickups & Arms

**HARCROFT**

Recording Stylis

**KELLY**

Ribbon Loudspeakers

**NEUMANN**

Professional Recording Machines, Condenser Microphones

**TANDBERG**

Stereo & Standard Tape Recorders

**CHAPMAN**

AM/FM Tuners

**GRAMPIAN**

Recording & Domestic Amplifiers, Cutting Heads & Loudspeakers

**CECIL E. WATTS**

"Dustbug" ★ "Parastat" Record Cleaners

**HAMS** — Write for detailed specifications of items which interest you —

**Simon Gray Pty. Ltd., 28 Elizabeth St., Melbourne**

# THE W.I.C.E.N. COMMUNICATOR

BY BOB GODSALL,\* VK2ARG

THE circuit and details of this equipment were arrived at after considerable experiment. While it is not claimed that this is the ultimate in design, tests have proved that this set-up will give a good account of itself. Early experiments using an acorn super-regenerative detector were disappointing, the addition of the r.f. stage making all the difference.

To be useful for the type of service envisaged, the Communicator had to satisfy the following demands:

- Simplicity of operation;
- Reasonable battery life;
- Minimum cost of battery replacement;
- Must use batteries which are easily available in country centres;
- Must be waterproof to the extent that it can be used in heavy rain;
- Robust to withstand hard usage and vibration;
- Use parts which can be procured, keeping disposals parts to a minimum.

\* Pacific Road, Palm Beach, N.S.W.

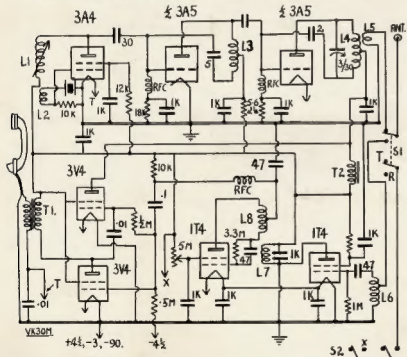
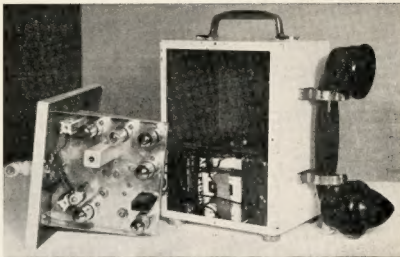


Fig. 1.

L1-5 turns 26 g. enamel,  $\frac{1}{4}$  inch diameter.  
L2-3 turns 26 g. enamel wound over cold end of L1. (Note the connection of this coil.)  
L3-10 turns 26 g. enamel, centre tapped,  $\frac{1}{4}$  inch diameter.  
L4-10 turns 20 g. spaced wire diameter,  $\frac{1}{4}$  inch diameter.  
L5-2 turns wound tightly over centre of L4.  
L6-13 turns 20 g. spaced three-wire diameter, tapped 3 turns from cold end,  $\frac{1}{4}$  inch diameter.

L7-5 turns 26 g. enamel,  $\frac{1}{4}$  inch diameter, iron dust slug.

L8-14 turns 26 g. enamel, centre tapped, see text.

Resistors— $\frac{1}{4}$  watt as shown.

Miniature potentiometer for the regeneration control should be 0.5 meg., not 5 meg. as shown in circuit above.

RFC-250 microhenry T.v. type.

The frequency of 57.8 Mc. was chosen for the following reasons: This frequency falls in a band which is a permanent Amateur allocation in Australia; it can be reached by the following crystal multiplications: 9.6 Mc.  $\times$  6, 7.2 Mc.  $\times$  8, and 6.4 Mc.  $\times$  9. This frequency is high enough in the band to be free of Amateur interference on the low end where activity normally takes place. Antenna efficiency is high using a small antenna; a quarter-wave stub is only four feet long!

The Communicator gives best results when used as a mobile/portable station working to a base station having higher power, a good antenna, and a sensitive receiver.

Over average hilly terrain, reliable communication can be maintained up to 20 miles; if both stations are well situated, considerably greater distances can be covered. Box to box, 5 to 10 miles can be expected.

With the addition of four feet of co-ax cable, several fittings and a small clamp to fit the window of a car, the Communicator can sit on the car seat and its own antenna fitted outside the vehicle, permitting mobile operation in any car at a moment's notice.

The equipment, complete with the batteries, is housed in a steel box measuring 9"  $\times$  6 $\frac{1}{2}$ "  $\times$  5 $\frac{1}{4}$ ". A P.M.G. type handset clips to the side of the box. Four rubber door stops permit sitting the Communicator on car or table without damage to paintwork.

There are only three controls: On/Off Switch, Send-Receive Switch, and the Regeneration Control. The transmitter is crystal controlled and the receiver fixed-tuned. The chassis and antenna are fitted to the removable panel, a gasket inside providing water-proofing.

The six batteries plug into the bottom of the box, and can be changed without a soldering iron. Two Type



422 45v. batteries connected in series provide the h.t.; the filaments run from three number 701 cycle lamp cells connected in parallel. The bias battery is a type 703.

## THE CIRCUIT

The transmitter uses a 3A4 pentode in an overtone circuit, giving output at three times the crystal frequency of 9.6 Mc., half a 3A5 double triode doubles to 57.6 Mc., driving the other half as a straight amplifier. This is plate-modulated by a 3V4 pentode using a miniature power choke as the modulation transformer. The receiver has a 1T4 pentode r.f. stage into another 1T4 super-regen. detector. Regeneration is controlled by a pot. in the screen lead. A separate 3V4 audio tube connects to the common input-output transformer.

The change-over from transmit to receive is achieved by switching the antenna and filaments circuits only. Extra switching could combine the function of modulator and audio output, but the price, size, and complication of a multi-contact switch is greater than that of the extra tube, and only one of these tubes is alight at one time.

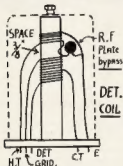


Fig. 2.

The combined transformer T1 can be either a microphone transformer (ex-AT5/AR6) or a midget speaker transformer, the former giving a better match to the handset, but the latter functions quite satisfactorily. The function of the transformer may need some explanation. The microphone and ear-piece are connected in series. One wire from the handset is grounded, the other is connected through the low impedance winding of T2 to the transmitter filament supply, being by-passed to ground with a 0.01  $\mu$ F. capacitor, which effectively earths this point at audio frequencies. When receiving, the audio tube (3V4) delivers power to the handset; when transmitting the 3V4 modulator grid is excited through the 0.01  $\mu$ F. coupling condenser. Bias to both tubes is supplied via the half-meg isolating resistors from the small "C" battery.

## HINTS

The r.f. plate and the super-regen. coils are wound on a small shielded t.v. type i.f. former, with a slug for each coil. The frequency of L8 can be set with a grid-dipper before placing the can in position, withdrawing the r.f. tube so as not to mistake resonance of L7. The same procedure is used for L7, by removing the detector tube.

Both coils should be tuned to about 54 Mc., as placing the can in position increases the frequency to around 57.6 Mc. Final tuning can be done on a weak modulated signal.

The 5 pF. feedback capacitor in the doubler circuit of the transmitter is rather critical. If the stage oscillates, this value should be reduced, although if the layout shown is used, no change should be necessary. The same applies to the neutralising condenser shown as 2 pF. The wire is extended from the end of the tank coil down through the chassis, and brought near the grid pin of the final half of the 3A5.

Obtaining drive to the final is the real problem. Two milliamps is necessary for full output. Sometimes removing the by-pass from the r.f. choke in the p.a. grid return will increase drive. Drive can be increased at the expense of h.t. milliamps, by removing the


double-pole on/off switch before any soldering changes are made. Also, be careful with a voltmeter probe.

The crystal is an ordinary variety, fitted in an FT243 holder. It was commercially re-ground to the specified frequency. Mention should be made if getting a crystal ground that it is to oscillate at 28.8 Mc. in an overtone circuit.

A 6.4 Mc. crystal can be used, but it is extremely difficult to obtain the full drive to the p.a.

The steel box is obtainable in Sydney from the firm, R. H. Oxford & Son Pty. Ltd., 97 Marriot St., Redfern. It is known as the "W.I.C.E.N. Communicator" box. The handle can be bought at any hardware store.

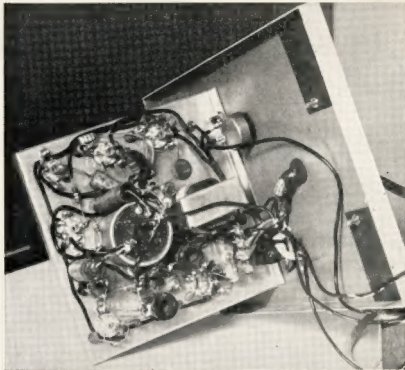The chassis is constructed from 20 gauge aluminium. The battery clips are constructed from brass strips and secured to the cabinet with  $\frac{1}{8}$ " brass



Below chassis view of W.I.C.E.N. Communicator.

resistor in the lead to L3, and running this stage at 90 volts.

The only snag in the receiver likely to be encountered is poor regeneration control. A moderate hiss should be audible with the pot control about halfway advanced.

Of several receivers built to this layout, one gave better control with a 10 meg. resistor in place of the 3.3 meg. shown. The r.f. tube is prone to oscillation with no antenna connected; this silences the regen. tube, so it is desirable to remove the screen voltage from the r.f. stage while making preliminary adjustments to the detector stage.

**Warning.**—Remember these are filament tubes—one touch of the 90 volts, and you blow the lot! Turn off the


bolts and nuts. The front panel is secured with four self-tapping screws, with a gasket of cork or other suitable material to give water-proofing.

Two plugs are available from most dealers to fit the two h.t. batteries, which lie on their sides one at each lower side of the cabinet. It is necessary to secure some insulating material such as mica on the inside of the front panel where it bears against the battery plugs. The three cycle batteries stand upright between the h.t. batteries making their earth contact with upright strips of brass. The top positive strips make contact with another brass strip secured under a piece of Masonite which is held down on an  $\frac{1}{8}$ " rod and also secures the batteries from move-

ment. The "C" battery can be soldered in—it will last for years!

It is not intended to give detailed comment on the overtone crystal oscillator as this has been well described in an article by Bob Winch, VK2OA, in "A.R." for Aug. '58. Also there is ample information on this in the Hand-book. Perhaps mention should be made here that this type of oscillator will only work on odd overtones, hence a 7 Mc. crystal cannot be used in the Communicator.

Since writing the original information on the Communicator, queries make it desirable to comment on the following: Many experiments were carried out using crystal multiplications of more than six times. While it is possible to obtain over one millilamp. drive, a great deal of fiddling is necessary and the crystal must be very active. It cannot be stressed too strongly that a 9.6 Mc. crystal be used. Any normal crystal (even in the FT243 holder) can be ground to the above frequency. The current charge to get this done is 35/-. Max Howden, VK3BQ, is one of our members who will do the job for you. (Another is Bright Star Radio.—Ed.) At least you don't have any further worries with the heart of the transmitter.

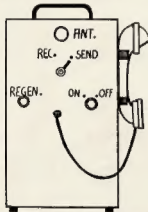

Front Panel Controls of Communicator.

The feedback on the doubler stage does increase the drive to the final a lot and, incidentally, does not help much if this stage triples. It is a help to be able to listen to the crystal and doubler stages during preliminary tests, on 28.8 Mc. or on 57.6 Mc. The doubler may oscillate with no drive, but the crystal holds it to the desired frequency. This is the idea of the regeneration.

In order to be certain that the crystal is controlling the frequency, bring a screwdriver near L1 while listening to the signal on 28.8 or 57.6 Mc. If the crystal has control, no change in frequency will occur.

The transmitter will draw approximately 40 milliamps. when loaded and delivering about 1 watt output. Current to the various stages is: Oscillator 8 Ma., Doubler 10 Ma., Modulator 10 Ma., and Final 12 Ma.

On the receive position, the current is only 12 Ma., which is less than that used by a small broadcast portable.

## ANTENNA

The most useful antenna is a centre-loaded 2 foot vertical. This can be made up from  $\frac{1}{2}$ " brass rod, threaded to screw into a short length of poly. rod, using a loading coil of 14 turns close wound of No. 20 g. on a  $\frac{1}{2}$ " poly. rod; the exact resonant frequency of the coil can be found with a g.d.o., but remember to remove the antenna from the box and stand it on a piece of metal sheet or grip the plug in a vice, making sure that it is connected electrically to the vice or metal sheet which acts as a ground plane.

A full quarter-wave whip is slightly more efficient and should be about 52 inches long. A cut-down b.c. car antenna can be reduced to one-third this length.

A small collapsible 50-inch whip can be supplied which can be secured by a suitable clip to the box when not in use.

An experimental dipole made from a tank type whip gave excellent results to a base station using a horizontal beam.

Polarisation is important over flat terrain but appears to be less so over rough country, but it is naturally desirable to use either vertical or horizontal at each end. A suitable vertical "J" or ground plane for the base station will be described later, with a base station rig at present under construction.

The Hand-set complete with wire can be purchased from Keep's, Elizabeth Street, Sydney, at a cost of 22/6. Clips to secure same to the box are made from spring steel but cost 8/- a pair.

## COILS

The formers for L1, L2 and L3 are those from an SCR522 receiver. There

appears to be no available slug-tuned former of this type available. These coils can be wound on  $\frac{1}{2}$ " poly. rod or pill tubes, L1 and L3 being tuned by Philips type 3-30 pF. trimmers.

The input and output coils (L4 and L6) were wound on small ceramic formers. It is suggested that they be either air-wound or wound on a suitable former such as poly. rod, poly. pill tube containers, or any material having low r.f. loss. The original formers were  $\frac{1}{2}$ " diameter. L4 has 10 turns of No. 20 gauge, spaced wire diameter. L5 (the link) is two turns of P.V.C. hook-up wire wound tightly over the turns of L4 at the centre, one turn either side of the centre tap.

L6 is also 10 turns but uses 26 gauge spaced three-wire diameters. The antenna tap is three turns from the earthed end. It was found that this coil resonated at the frequency and that no tuning was therefore necessary.

L7 and L8 are wound on a  $\frac{1}{2}$ " diam. t.l.v. former tuned with two iron dust slugs, details are shown in Fig. 2.

## UNIFORMS DUST COATS

for your Office Staff, Factory,  
Workshop, Servicemen.

★  
Bowls Frocks, Tennis Frocks,  
for the retail trade.

★  
**D. MILBURN & CO.**  
238 Flinders Lane, Melbourne

**SILVER JUBILEE!**

**U.R.D. and  
AMATEUR RADIO**

Ham operators know that U.R.D. have  
been serving them well for over 25  
years and will continue to do so.

U.R.D. have the stocks. U.R.D. have  
the staff. U.R.D. have the know-how.

**UNITED RADIO DISTRIBUTORS**

175 PHILLIP STREET, SYDNEY

Telephone: BW 3718

# An Experimental High Frequency Transistor Portable Superhet. Receiver

Coverage: 12 Mc. to 2.2 Mc. and 1600 Kc. to 550 Kc.

BY S. L. SKINNER,\* VK3AFL

**T**HE receiver about to be described is a double conversion superhet with a tuning range from 12 Mc. to 2.2 Mc. plus 1600 Kc. to 550 Kc. in four bands. It uses eleven junction type transistors and one diode.

The first section of the receiver consists of an OC44 mixer and an OC44 local oscillator. The mixer is an earth emitter type amplifier stage.

A signal from the low impedance winding on the aerial tuning coil is fed to the base of the mixer transistor, along with a small amount of r.f. from the local oscillator. The r.f. from the local oscillator is picked up by returning the bottom of the low impedance winding to earth via a few turns around the earth end of the oscillator coil. The OC44 local oscillator has its emitter earth returned, and the base is tapped towards the earth end of the tuning coil in order to match into the low impedance of the base. Generally speaking, the feedback coil winding to the collector requires a few more turns than would normally be used for valve circuitry, but if the base tap to the coil has too many turns, squealing will take place.

As this receiver was built mainly for high frequency work, the problem of second image was overcome by using a 2 Mc. first i.f. At this frequency, the stage gain of the second mixer is not greatly effected. Further more, with the local oscillator on 2.150 Mc., the harmonics do not fall into the tuning range of the Amateur bands.

The second stage. As already stated the input to the second mixer is at 2 Mc. Both the mixer and local oscillator use 2N112 transistors. Operation of the second converter is the same as for the first converter, the output frequency from the second mixer being 150 Kc.

The third stage. This stage is the main intermediate frequency stage at a frequency of 150 Kc. Various types of transistor intermediate amplifiers were tried, until it was decided to again use the grounded emitter type of circuitry, and feed the low impedance winding into the base of the transistor.

The frequency of 150 Kc. was selected in an attempt to obtain a reasonable amount of selectivity. By using a low gain transistor, either an OC71 or OC73, in the first position followed by a high gain transistor, either an OC44 or 2N112, it provided plenty of gain and remained stable without neutralisation.

Diode detection was selected for simplicity, but gain and a.v.c. action could be improved by using an OC71 transistor as a detector.

The beat frequency oscillator circuit is very simple and was copied from Phillips' Transistor Manual. No attempt was made to couple the b.f.o. to any stage of the i.f., stray coupling being sufficient.

The fourth stage. This is the audio stage and was also copied from the Phillips' manual, but with the following modification. In place of an OC71 transistor a high gain transistor 2N138 was used to compensate for the loss due to the use of the OA70 diode detector.

acitors and resistors identical with those used in the local oscillator of the receiver being built.

(f) Multimeter.

The test oscillator was constructed first, and was used to check the h.f. transistors to be used in the receiver and for checking the frequency coverage of the oscillator coils to determine the capacity values to be used in the padding capacitors.



## TESTING

For testing during construction of the receiver, the following equipment was used:

- Receiver CR300, tuning range 15 Kc. to 25 Mc. Used to check the frequency of the oscillator.
- Signal Generator covering 150 Kc. to 30 Mc.
- Grid Dip Oscillator, for checking frequency of coil windings.
- A second h.f. receiver with a calibrated S meter, used mainly to compare the output of various transistors used in the oscillator test set.
- Oscillator Test Unit, constructed breadboard style. This unit was constructed with values of cap-

On completion of the test set a coil was wound with 8 turns 18 g. primary, 41 turns 24 g. feed-back winding close wound to the primary, base tap 2 turns at earth end of coil. The tuning capacitor was rotated minimum to maximum and with the aid of the g.d.o., frequency coverage determined as 15 Mc. to 6.5 Mc. An OC44 transistor was inserted in the socket and the battery supply (-6v.) connected.

This transistor oscillated from 6.5 Mc. to 7.2 Mc. Alteration to the feed-back winding and base tap made no difference, it would not oscillate any higher in frequency. The current drawn was approximately 300 microamps. A second OC44 was tried. This one oscillated freely from 6.5 Mc. to 11.8 Mc., then from 11.8 Mc. to 12.5 Mc. the note of oscillation became very rough, and beyond 12.5 Mc. would not oscillate.

\* Lot 316 Aurum Crescent, Ringwood, Vic.





The current drawn was 150 microamps. A third OC44 was tried, this one stopped oscillating at 9.7 Mc. The current drawn was 230 microamps.

The second OC44 had the greatest output, so it was used as the local oscillator, the third OC44 being used as the mixer. From the tests made it will be noted that it is necessary to select transistors to be used in h.f. applications. Do not expect transistors of the same type number to have the same performance.

## CONSTRUCTION

The first section of the receiver to be constructed was the first converter. The layout and size of the complete receiver was worked out at this time.

The tuning capacitor and switch were mounted on the sub-chassis and the slow motion dial fitted. The OC44 mixer and OC44 local oscillator were wired up, coils for the switch position No. 2 were wound, checked, mounted in position and wired to the switch. A temporary 2 Mc. coil was wound and

cans and modify the coils to suit. There are two coils in each can. One coil is removed and the second modified as follows:

Two pies of the coil are used with a 500 pF. capacitor, which with the aid of the tuning slug, will tune to 150 Kc. From the top pie, 80 turns were unwound, about an inch of the wire twisted together and timed, then the 80 turns scramble wound back on top of the pie. The tap at 80 turns is the connection for the collector. The third pie, which was cut away, now becomes the secondary or base coil. For IFT1 and IFT2 unwind approximately 60 turns, leaving not under 35 and not over 40 turns. For the secondary of IFT3 leave approximately 60 turns. The wax is then heated and the base winding pushed up close to the primary winding.

The component parts associated with each stage are mounted on tag strips screwed to the base plate inside the coil can.

the multimeter to measure the output of the audio amplifier. The alignment of the i.f. coils was made by adjusting the iron slugs.

The second mixer coil, along with the second oscillator coil were mounted alongside each other in another coil can. (For details of coils, see drawing.) Inside the same can, the 2N112 oscillator transistor and component parts C6, C7, C8, C9, C34, C35, R6, R7, R8 and R9 were mounted. When wired, the stage was coupled up ready for alignment. Firstly, the local oscillator was checked for correct frequency of 2.150 Mc., using the CR300 receiver as a wave meter. Frequency adjustment was made by adjusting the slug in the oscillator coil. The signal generator was then set at 2 Mc. and the second mixer coil adjusted. The receiver was at this stage a single conversion superhet. Had the coils been altered, good performance would have been available on the b.c. band.

## Beat Frequency Oscillator

The b.f.o. was next wired and all components fitted into a coil can. The b.f.o. frequency was located on the CR300 receiver and adjusted with the iron slug.

## First Mixer and Oscillator

The next step was to couple the first mixer output to the 2 Mc. coil.

The test set, using the OC44 oscillator transistor from the receiver, was now used to check the frequency of the local oscillator coils. For example, the b.c. band frequency coverage of 1600 Kc. to 550 Kc. plus i.f. frequency of 2 Mc. = local oscillator frequency, 3.6 Mc. to 2.55 Mc.


The oscillator coil was wound and wired into the test set and frequency checked. The coverage was from 1.5 Mc. to 3.6 Mc., so a 150 pF. padding capacitor was wired between the tuning capacitor and coil to slow the oscillator frequency to the desired coverage of 3.6 Mc. to 2.55 Mc. All the oscillator coils were wound and the padding capacitors selected by the same means. The link coil was made adjustable in order to vary the amount of r.f. injection to the mixer.

The oscillator coils were then mounted and wired to their switch positions, the OC44 oscillator transistor replaced in the receiver, and each coil again checked for correct frequency coverage.

The mixer coils were the next problem. The test set was again used in conjunction with the g.d.o. to adjust these coils. The b.c. band coil is a Q Plus loop stick with 4 turns of 28 g. enamelled wire wound over the earth end of the loop stick winding for base input to the mixer. No tracking capacitor was required. The next band, 5 Mc. to 2.2 Mc. (switch position 4), as can be seen from the coil table, consists of 36 turns of 22 g. wire on a 3" diameter former, with 4 turns of 26 g. wire for the base winding. The base winding is interwound at the cold end of the primary. No tracking capacity was required, any adjustment required being made with the trimmer. The antenna is tapped half way down the primary coil through a 200 pF. capacitor.

The following band, 8.5 Mc. to 5 Mc. (switch position 3), was then wound

(Continued on Page 42)

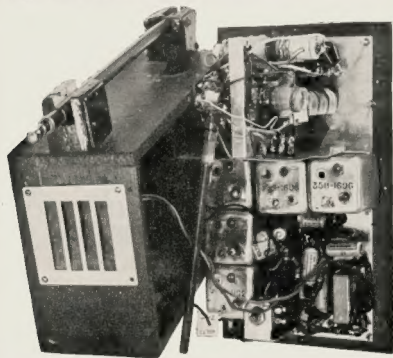

connected to the collector of the OC44 mixer. The output of the 2 Mc. coil was fed into the CR300 receiver which was tuned to 2 Mc. The converter was checked and adjusted. Satisfied the converter would work, it was put aside till later. Next the audio stage was wired and tested and the OA70 diode wired in, in readiness for the attempt on the intermediate frequency amplifiers.

## I.F. Amplifiers

After carrying out tests on various types of standard i.f. coils, it was found practical to use a disposal type coil can No. 358-1696 out of the BC966A I.F.F. equipment. The decision was made to build each i.f. amplifier in these coil

The first i.f. amplifier component parts are C13, C14, C15, R14, R15, R16, R17, IFT2 coil, transistor OC73 and socket. The second i.f. amplifier components are C16, C17, C18, R18, R19, R20, R22, IFT3 coil, the 2N112 transistor and socket.

## Second Mixer and Local Oscillator

The next section to be constructed was the second mixer and local oscillator. The second mixer transistor 2N112, together with IFT1 coil and components C10, C11, C12, R10, R11, R12 and R13 are mounted in the coil can in the same manner as already described. Before attempting the local oscillator, the 150 Kc. amplifier strip was aligned with the aid of the signal generator using

# 25 Years of AMATEUR RADIO

WITH the publication of this issue AMATEUR RADIO celebrates the 25th Anniversary of its publication as the official journal of the Wireless Institute of Australia.

In attempting to produce what might be termed a history of the magazine it has been found that many of the early records have been mislaid and consequently it has not been possible to adequately cover the stage dealing with the initial work which led up to the publication of the first issue of AMATEUR RADIO on 1st October, 1933.

Although the Victorian Division of the Wireless Institute of Australia had been founded in 1910, it was not until 1925 that the Division was incorporated. Radio, as we know it today, was still in its infancy and it was not until broadcasting commenced that any commercial magazines were produced. These were designed primarily to cater for the broadcast listener with most of the technical articles being written for the broadcast receiver builder and with large sections devoted to the programs of all stations.

Most of these journals, some of which were on the market for a short time only, did devote some space to news of Amateur activity, but it would have been unreasonable to expect that technical articles for the transmitting Amateur should be printed. It must be remembered that, in those days, the Amateur represented an extremely small percentage of the total population of Australia, and less than 700 Amateur Operator's Certificates of Proficiency had been issued up until the end of 1930.

Such news of happenings of interest to the Amateur were contributed by Amateurs acting on behalf of the various Divisions of the W.I.A. or Radio Clubs and, in some cases, by Amateurs acting in a private capacity. It had long been realised by the different Divisions of the W.I.A. that, whilst this system of a few pages in a commercial magazine was undoubtedly of value to members, it was far from ideal and in so far as the Victorian Division was concerned, it had been agreed that only by producing a magazine of our own which would be devoted entirely to Amateur interests, would it be possible to attempt to cover the interests of all members, and in particular those members who lived in country areas and were therefore unable to attend meetings and lectures.

It would appear to have been about the middle of 1933 that a sub-committee was formed by the Council of the Victorian Division to investigate the possibility of publishing an Institute magazine. This committee consisted of Harry Kinnear (VK3KN), Bill Gronow (VK3WG), Vaughan Marshall (VK3UK) and Bill Sones. No record is available

of the deliberations of this committee, but their enthusiasm convinced the Council that a magazine could be produced and that the Radio Trade would contribute by way of advertisements.

The first issue of AMATEUR RADIO appeared on 1st October, 1933. This issue ran to 20 pages and cover with a page size of 8½ inches by 5½ inches, just half the size of the present page. Three pages and portion of the covers were devoted to paid advertisements. The only technical article, "Simple Crystal Control," by Max Howden (VK3BQ), occupied two pages and the remainder of the journal was taken up with notes from the different sections of the Victorian Division, from affiliated clubs and from the R.A.A.F. Wireless Reserve.



for the 1933 Australian Five-Point Relay Contest were included, together with results of the 1933 A.R.R.L. Contest, the first two places in Australia being filled by R. H. Cunningham (VK3ML) and R. E. Jones (VK3RJ).

This first issue of AMATEUR RADIO was solely a Victorian one, but the November issue saw the inclusion of notes from New South Wales, Queensland, South Australia and Western Australia. To quote from the N.S.W. notes, "We are solidly behind this attempt to firmly establish a really 100 per cent. Amateur journal for the Commonwealth." This statement reflected the true Amateur spirit, as it later transpired that the Association of Radio Amateurs (N.S.W.) had also been in-

vestigating the possibilities of publishing an Amateur journal and abandoned their proposal when it was found that Victoria had already produced a magazine.

During November 1933, Bill Sones retired from the committee and Jim Marsland (VK3NY) became Secretary with Harry Kinnear (VK3KN) as Editor, and Bill Gronow (VK3WG) and Vaughan Marshall (VK3UK) as Sub-Editors. The latter two with Jim VK3NY formed the nucleus of the committee for over seven years and Jim VK3NY is still a member of the committee. In March 1934 Bob Cunningham (VK3ML) became Technical Editor and Len Moncur (VK3LN) took over the distribution of the magazine.

For the first year of publication the advertising salesmen were the Editor, Harry Kinnear (VK3KN) and Sub-Editor Bill Gronow (VK3WG), and some amusing stories are told of their efforts to sell space in the journal. It is reliably reported that, on one occasion, when a particularly hard-hearted member of the trade offered to pay 10/- for a full page instead of the £4 being asked, VK3KN somewhat tersely replied that the day would come when the same man would be glad to pay £10 a page. That rate has been reached but the prospective advertiser is no longer catering for Amateurs. However, our Amateur salesmen must have convinced the members of the trade generally that it was good business to advertise in AMATEUR RADIO as they continued to support the magazine with their advertisements and many of those early advertisers are still solidly behind AMATEUR RADIO as an advertising medium.

After twelve months the printing of the magazine was transferred from Messrs. Wilkie & Co. to the Elsum Printing Company and Mr. Elsum, Snr., became the Advertising Representative. In June 1936, both Harry Kinnear (VK3KN) and Len Moncur (VK3LN) retired from the committee and Cedric Serie (VK3RX, now VK3ARX) and the late Ernie Kilborn (VK3KE) were co-opted. Bill Gronow (VK3WG) became Editor at this stage and continued to act in this capacity until January 1941. Ern Kilborn (VK3KE) died suddenly in June 1937 and the existing committee carried on until February 1938 when Thorburn Powers (VK3PS, now VK3APS) joined the committee and in July 1939 Herb Stevens (VK3JO) took over the distribution of the magazine.

With the outbreak of war in September 1939 both Vaughan Marshall (VK3UK) and Bob Cunningham (VK3ML) were called up for service with the Royal Australian Air Force. Vaughan and Bob had both played a leading part in the formation of the R.A.A.F. Wireless Reserve and at the outbreak of war, Bob VK3ML held the rank of Flying Officer and was Federal Commander of the Reserve. Vaughan VK3UK, with the rank of Pilot Officer,

ERRATA: Should read: "Continued on Page 46."

was Divisional Commander for Victoria. Bill Gronow (VK3WG) also enlisted in the R.A.A.F. in July 1940. All three served with distinction. Vaughan Marshall (VK3UK) rose to the rank of Group Captain and became Director of Telecommunications for the R.A.A.F. Bob Cunningham (VK3ML) held the rank of Wing Commander and served as Chief Signals Officer in various areas in both Australia and the Pacific. Bill Gronow (VK3WG) also became a Wing Commander and officer in charge of Technical Development of Signals and Radar Equipment, and its production in Australia.

All three continued to act on the Editorial Committee until, with the publication of January 1941 issue, the Victorian Division was no longer in a position to continue to print the magazine. However, AMATEUR RADIO

was not destined to disappear "for the duration" as so many other Amateur publications were forced to do. It was realised that, with so many members of the W.I.A. serving with all branches of the Defence Forces and scattered all over the world, something would have to be done to keep them in touch with one another, and it was decided that a duplicated version of AMATEUR RADIO should be produced.

After missing only one month, the committee was reorganised with Tom Hogan (VK3HX) as Editor, and Jim Marsland (VK3NY), Herb Stevens (VK3JO), Charlie Quin (VK3WQ, now VK2AWQ), Alec Clynne (VK3VX), Ken Ridgway (now VK3CR) and the late Bert Burdakin as members of the committee. A hand-operated rotary duplicator was purchased and from March 1941 until September 1945 the wartime version of the magazine appeared each month. The amount of work that went into this production was colossal as the magazine grew from 10 pages to 16 pages quarto size and over 600 copies were being produced for most of the time. When it is realised that every page represented one turn of the duplicator and that allowance had also to be made for "spoils", some idea of the magnitude of the task can be obtained. The duplicator was most temperamental, quality of paper available left much to be desired, and while two men operated the duplicator the others were busy checking and counting the printed pages. The pages had then to be collated, inserted in the cover which had been printed and then stapled together, also with a hand-operated machine. Finally, copies had to be wrapped, addressed and posted.

For the whole of this period, every member of the committee gave up two full Saturday afternoons every month to cope with the printing alone as well as hours of spare time in keeping the routine work up to date.

Although technical articles were included in the war-time issues, the main purpose, of course, was to keep members in touch with one another and, as no transmitting was permitted, any notes published were in the main personal items. With increasing numbers serving with the Defence Forces, one of the main features was "Slouch Hats and Forage Caps." This section was conducted by Jim Corbin (VK2YC) from November 1941 until September 1945 and involved a considerable amount of work, mainly by correspondence.

Throughout the whole of the four and a half years of production of the duplicated magazine, the "printing office" was located at the home of Jim Marsland (VK3NY) and the committee were indebted to Mrs. Marsland for her co-operation. She not only assisted with the sorting and collating of pages, but supplied innumerable cups of tea, biscuits and cakes throughout the whole period.

With the cessation of hostilities in August 1945, it was immediately decided that printing of AMATEUR RADIO should re-commence. The services of Mr. W. J. Lewis were obtained as Advertising Representative and arrangements were made for Messrs. H. Hearne & Co. to print the magazine and in October 1945 publication was

resumed in the present form. It was immediately apparent that the goodwill which had been fostered, firstly by Harry Kinnear (VK3KN) and Bill Gronow (VK3WG), and built up by our Advertising Representatives during the pre-war period was still existent and our advertisers again came to our assistance with their support.

Tom Hogan (VK3HX) continued to act as Editor, Ken Ridgway (VK3CR) became Technical Editor, Herb Stevens (VK3JO) Distribution Officer, and Jim Marsland (VK3NY) continued as Business Manager. In March 1947 Ron Higginbotham (VK3RN) joined the committee as Notes Editor and in March 1948 Jack Duncan (VK3VZ) became Technical Editor when Ken Ridgway (VK3CR) resigned through pressure of private business. Alan Head (VK3AKZ) joined the committee as Assistant Technical Editor in July 1947 and Jim Irvine (VK3TU) took over the distribution from Herb Stevens (VK3JO) in September 1948. During the past ten years circulation has been in the hands of Stan Zeunert (VK3SZ), Ian Sewell (VK3IK) and Bill Tregear (VK3TX).

After serving as Editor for over fifteen years, Tom Hogan (VK3HX) resigned in May 1956 and Jim Marsland (VK3NY) took over as Editor with Ron Higginbotham (VK3RN) as Associate Editor. Ken Pincott (VK3AFJ), who had been recruited to the committee in February 1954, became Technical Editor in August 1955 when Jack Duncan (VK3VZ) vacated the position, although he continued to assist on the committee.

During the post-war years the Technical Editors have been assisted by Jack Fisher (VK3AFZ), Doug Newman (VK3UC), Ron Fisher (VK3OM) and Alec Morrison (VK4MA), all of whom have contributed many hours of work in the preparation of circuit diagrams.

With the expansion of AMATEUR RADIO it was necessary to completely re-organise the Editorial staff in May of this year and Ron Higginbotham (VK3RN) became Editor with Ken Pincott (VK3AFJ) continuing as Technical Editor. The committee has been considerably enlarged and now consists of George Baty (VK3AOM), George Bills-Thompson (VK3AHN), Sid Clark (VK3ASC), Jack Duncan (VK3VZ), Ron Fisher (VK3OM), Vern Jones (VK3YE) and Jim Marsland (VK3NY).

Since June 1949 the printing of AMATEUR RADIO has been in the hands of the "Richmond Chronicle" and the co-operation of Mr. Roberts and his staff cannot be spoken of too highly. Our Advertising Representative, Miss Beatrice Touzeau, has also done a sterling job and our readers with the trade have never been better.

Notwithstanding the work which has been put in to the production of AMATEUR RADIO over the past 25 years by members of the Editorial Committee, we must not lose sight of the fact that a magazine cannot be produced without an army of contributors. Many hundreds of technical articles have been written for the magazine and it would be impracticable to name the writers, all of whom have contributed in an honorary capacity. To them, and also to the writers of regular features such as DX Notes, V.h.f. Notes, Federal and Divisional News, the Editors are indebted for their support and co-operation at all times.

# Low Drift Crystals

## FOR AMATEUR BANDS

ACCURACY 0.02% OF  
STATED FREQUENCY

3.5 Mc. and 7 Mc.

Unmounted ..... £2 10 0

Mounted ..... £3 0 0

12.5 and 14 Mc. Fundamental  
Crystals, "Low Drift,"  
Mounted only, £5.

THESE PRICES DO NOT  
INCLUDE SALES TAX

Spot Frequency Crystals  
Prices on Application.

Regrinds ..... £1/10/0

**MAXWELL HOWDEN**  
15 CLAREMONT CRES.,  
CANTERBURY, E7.  
VICTORIA

# THE TA2 SPECIAL

BY CDR. C. M. STURKEY, JR., U.S.N., W7TNA

THE reason for the title will remain obscure for the present. Primarily, it is a device to encourage you to read further. My interest in preparing this little article resulted from a recent round table with VK3JK and W7IAA. These two were using s.s.b.s.c. and I was using d.s.b.s.c. (double sideband suppressed carrier). After giving a brief run down on my "home brew" d.s.b. rig, pointing out its simplicity, both from the standpoint of construction and adjustment, and taking several deep bows as a result of the compliments passed on the shapeliness and quality of my signal, the subject of the conversation got around to a discussion of the difficulties confronting the average Ham who wishes to get started in s.s.b.

Because of the ample availability of excellent "store bought" Amateur s.s.b. transmitters in this country, well-heeled U.S. Hams have no problem. However, it might come somewhat as a shock to some VKs who have heard the many KWS-1's, KWM-1's, HT-32's, etc., on the bands, that the average U.S. Ham cannot afford this kind of equipment. The dwindling group of "home brew" artists also have their problems with s.s.b. Assuming that they have a better grasp of technical know-how than the average, the cost of acquiring the necessary test equipment is often prohibitive. For the VK Ham and most outside of the U.S., the problem of getting started in s.s.b. is a much more serious one. Do not misunderstand me—I am not running down s.s.b. or discouraging you from giving it a try, but only pointing out why there are not more on the bands, particularly outside the U.S. and Canada, who are taking advantage of this wonderful medium of communication.

All you physiologically maladjusted Hams who are obsessed with a suppressed desire to talk back to the "Donald Ducks" should not be discouraged. The "TA2 Special" is the solution to your problem. Not only can you work the s.s.b. boys without a word of apology for your signal, with this transmitter it will not even be necessary for you to sever social intercourse with your old friends on the c.w. and a.m.

If I have not lost your interest by now, it should be safe for me to clue you on the name chosen for this rig. It all started in Turkey in 1952 during my tour of duty as U.S. Naval Advisor at a Turkish shipyard near Izmit. A few VKs may still have my QSL card (TA2EPA) around the shack. Since the first prototype of this transmitter was built and operated in Turkey, it has been dubbed the "TA2 Special". Using this rig, I had the doubtful honor of turning in the top Turkish score in the DX contest. It would only be honest to tell you that I was the only TA entered that year.

If there is anything original about the "TA2 Special" it is that it combines the features of d.s.b.s.c. transmission which has recently received much attention by our U.S. publication "CQ

Magazine"<sup>1</sup> and d.s.b.r.c. (double sideband reduced carrier) which was covered in "QST"<sup>2</sup> by a two-part classic by George Grammer in 1951. Fig. 1 is a simplified circuit of a proposed medium-powered version of the "TA2 Special". Most will notice immediately that basically it consists of a balanced modulator plus a grounded grid linear amplifier. While the grounded grid linear provides a very efficient and fool-proof way of increasing power output, it is not a "must" as a balanced modulator can go directly to the antenna. By using heavy duty pentodes or tetrodes with proper characteristics (ones requiring relatively low screen grid voltage would be preferable), it is possible to get a high-level output without the linear amplifier.

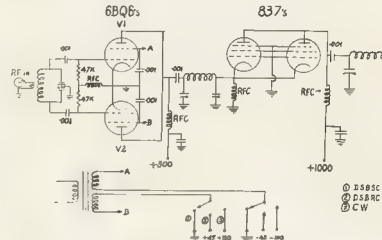


Fig. 1.—Simplified circuit of "TA2 Special".

Looking at Fig. 1 again, it will be noticed that the modulation transformer has a split secondary. This makes it possible to apply separate screen grid voltages to the two tubes. In position 1, both screen grids are at d.c. ground potential. With approximately balanced components and tubes a carrier suppression of about 40 db. will result. When audio is applied to the screen grids, d.s.b.s.c. is produced. In position 2, a positive voltage is applied to one screen grid and an equal negative voltage is applied to the other, this gives d.s.b.r.c.

I will not go into too much detail on d.s.b.r.c. here because those interested should check their back files of "QST" or visit the library to read George Grammer's articles in "QST". However, here is a somewhat oversimplified explanation. In the absence of audio, the tube with the negative screen grid voltage is effectively removed from the circuit except for the fact that it continues to act as an excellent neutralizing condenser for this stage. The tube with the positive screen grid voltage operates as a class C amplifier at reduced efficiency. This is because of the relatively low screen grid voltage being

used. From this it may be seen that the amount of carrier developed depends on the screen grid voltage applied, always keeping an opposite and approximately equal voltage on the other screen grid.

Up to the point of 100% modulation this stage performs like a conventional single-ended screen grid modulated transmitter. When 100% modulation is exceeded, the tube with a negative d.c. voltage on the screen grid starts to work. Assuming theoretically perfect tubes, if we use 50 volts positive on the screen grid of V1, 50 volts of audio would give 100% modulation. Even though we also are applying this audio to the screen grid of V2, nothing happens because on the positive swing the 50 volts of audio subtracts from the

minus 50 volts of fixed d.c. giving us zero voltage. Now, consider what happens when we increase our audio—say 100 volts of audio is being used. On the positive swing, the V1 has +150 volts and V2 has -150 volts. When the audio voltage reaches the peak at the opposite swing of the cycle, V1 will have -50 volts and V2 +50 volts. At the point when V1 stops working, V2 picks up the load. Fig. 2a shows 100% modulation using the 50 volts of audio as per example above. Fig. 2b shows the over-modulation that would result with a single-ended stage under the same conditions with 100 volts of audio. Fig. 2c shows the results of 100 volts of audio with two tubes operating in a "balanced modulator".


While we are on the subject of oscilloscope patterns, we might take a look at the presentation resulting from d.s.b.s.c. signals. It is interesting to note that with single sideband transmission it is necessary to use two tones to get this presentation, but only a single audio tone is necessary to make this check with d.s.b.s.c. Fig. 2d shows what you will see with good carrier

(Continued on Page 16.)



# Mullard TELEVISION VALVES

## IS2 EHT RECTIFIER

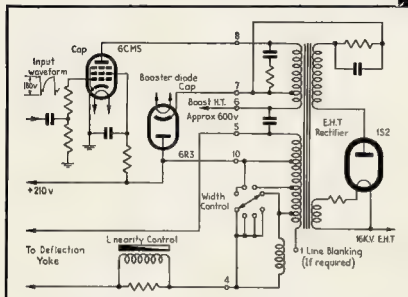

### TYPICAL OPERATING CONDITIONS

D.C. output voltage	18 kV
D.C. output current	150 $\mu$ A


### MAXIMUM RATINGS

P.I.V.	22 kV
D.C. output current	0.8 mA

The **IS2** is a half-wave rectifier designed for use in television EHT supply units deriving their input from the line time-base fly-back pulse. The peak inverse rating of 22 kV enables an EHT of 18 kV to be obtained with an adequate safety margin. The heater requirements of 1.4V at 0.53A may be supplied by a winding on one limb of the line output transformer. Additional data is available to design engineers on request.



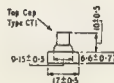ISSUED BY THE TECHNICAL SERVICE DEPARTMENT



All dimensions in mm

MULLARD-AUSTRALIA PTY. LTD., 35-43 CLARENCE ST., SYDNEY, BX2006, & 592 BOURKE ST., MELBOURNE, MU2366  
ASSOCIATED WITH MULLARD LTD., LONDON, MULLARD EQUIPMENT LTD., MULLARD OVERSEAS LTD.

# THE IMPROVED DIPPER

Here is a new model streamlined so the instrument can be manipulated in one hand

WILFRED M. SCHERER, WZAEF

THE IMPROVED DIPPER includes several refinements over the original instrument described by the author.<sup>1</sup> It is a more compact design, greatly facilitating handling and operation.

The new model is a.c. operated and entirely self-contained in one small case. The grid meter is located directly in the same line with the tuning dial and the probe coil, so it may be easily observed.

The line cord is connected by means of a plug for easy removal for substitution of a separate cable when battery operation is desired. (Here in Australia, we will have to use a separate power supply.—Ed.) Self-contained battery operation was at first planned, but was abandoned because available tubes having small filament drain were not found rugged enough for general portable operation. The use of batteries, in most cases, is not required except under some conditions of antenna measurements where it may be more convenient. And batteries too often have a habit of running down at just the psychological moment.

The tuning dial is arranged so that the instrument may be held and tuned at the same time by one hand. The frequency range, 1.7 to 275 Mc., is

covered using seven coils, each having a tuning ratio of 2.5 to 1. The Amateur bands are located at the low frequency end of each scale where there is slightly greater spread (the variable capacitor is one of straight line wavelength). Considerable overlap between ranges is also included so the second harmonic of each band may be read directly on its same scale. All the scales up to that covering 65 Mc. may be checked directly with WWV.

The entire range of the instrument could be covered using only six coils, but with a sacrifice of overlap and spread on each Amateur band. The range may be extended up to 350 Mc. or below 1.7 Mc. with additional coils for which an eighth dial scale, reading from 9 to 10, is provided for reference calibration. Each coil is protected by an insulated sleeve.

## CIRCUIT

The circuit is shown in Fig. 1. With the exception of the power supply, it is basically the same as that of the original instrument. The oscillator itself is the Split-Colpitts. Power is obtained directly from the 117-volt a.c. line; however, complete isolation is included in order to eliminate the hazard of shock. This is accomplished by bypassing the negative of the power supply to the metal shield case with a

The Improved Dipper, having a range of 1.7 to 275 Mc. The toggle at the lower left is the filament switch, the one at the right is the plate switch. The Jones power receptacle is at lower center bottom.


0.002  $\mu$ F. capacitor (C7). At first a 0.02  $\mu$ F. capacitor was used and, although its reactance at 80 cycles was sufficiently high to limit the current below the minimum safe value, enough "tickle" was experienced between case and ground to scare one into dropping the instrument. No sensation is experienced using the 0.002  $\mu$ F. capacitor, even with wet hands.

Although headphones are usually completely insulated, an additional precaution has been included for their use. When the phones are plugged into the jack, a 50,000 ohm resistor (R4) is automatically inserted in the grid return to reduce the maximum possible current below the minimum safe value. The sleeve end of the jack is also connected to the case through a 0.002  $\mu$ F. capacitor (C6). The resistor could be left in the circuit at all times and the phone jack could then be connected across the resistor through a small capacitor, but the grid current would then be too low when utilizing a 0-1 mA. meter. (A 0-200  $\mu$ A. meter would be the obvious solution, but a 0-1 mA. meter costs less.)

Plate power is obtained through a half-wave selenium rectifier and RC filter. A resistor line cord of the correct value to operate 83v. 0.15 amp. tube was not obtainable; therefore, a resistor (R5) is connected in parallel with the tube filament to enable the use of a standard 390-ohm line cord. In the event of the line cord becoming defective, it may be easily replaced at the Jones power plug instead of requiring internal soldering of connections. When 117 volts a.c. is to be used, a jumper must be connected between terminals 1 and 4 of the line plug to connect the internal parallel filament resistor. When battery operation is to be employed, the jumper is omitted, removing the resistor and thereby reducing the filament battery drain.

The original Dipper utilized a 955 acorn tube which was soldered in place to eliminate socket inductance and thus increase the upper frequency limit. From a practical standpoint, it was deemed advisable to employ a tube with a socket. The 9802 was chosen because, compared with the 955-plus-socket, it
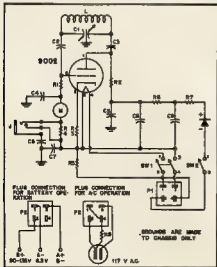
<sup>1</sup> Reprinted from "CQ", Feb. 1949.  
1 Scherer, "The Dipper", "CQ", May 1947



taken up less over-all space and with a given high frequency coil it will oscillate at about the same frequency.

## CONSTRUCTION

The material used for the case is 0.040 inch No. 25 half-hard aluminum. Other material such as copper may be used. The bending can be done easily in the home workshop as follows: Using a pair of "C" clamps, secure the material between a pair of steel bars, or right angle stock, aligned with a scribed line where the bend is to be made. The bars should have a smooth and clean right angle edge. Place the bars securely in a vise and bend the material, using a heavy wood block for leverage. This will make a bend that is slightly round at the edge. To true up the edges, place a flat piece of steel on top of the bend and hammer the steel piece until the bent edge is clean and sharp. The "C" clamps are used only to keep the bars aligned with the scribed line until they are placed in the jaws of the vise. When making the scribed lines, allowance must be made in the dimensions for a slight loss in the bend. Before making the final bends, it may be wise to make a few practice operations with scrap metal. Dimensions of the case are: Length 5½" width 2¼" depth 2¾". The depth will depend on the size of the condenser (C1) used.

The case is made in the shape of a long "U" with a side plate measuring 5½" x 2½" with two flanges along the long edges. The bottom plate is 2½" x 2½" with flanges round all edges.

The top of the case is a piece of polystyrene, ¼" thick. The coil mounting posts are located in the polystyrene, but they should not be drilled until the variable capacitor is installed and their location is determined, bearing in mind that the length of the leads from the coil socket to the condenser must be as short as possible.

The meter shown in the photograph is a surplus 1½" meter and should be mounted on the rear side of the hole in the case with the flange on the rear side so only the round lip of the meter face protrudes through the case.

The coils are wound on ¼" polystyrene rod. Dimensions are given in Fig. 2. Each coil must be undercut approximately 1/32" where the wire is to be wound to allow passage of the polystyrene sleeve over the coil. If a lathe or machine shop is not available for this work, the sleeve may be omitted. In this case, if protection and insulation are desired, the coil should be coated with coil dope and then wrapped with scotch tape.

At the top of the coil-form a hole (No. 48) is drilled through its diameter. A slot is then cut with a hack saw, about 1/16" deep from this hole lengthwise down the side of the rod. This will make it possible to bring the lead from the top of the coil through the hole and down under the coil to one of the banana plugs on the base. The other lead from the coil is then brought through a hole drilled at the bottom edge of the coil and at right angles to the top hole. Another slot is cut from the top hole so the sleeve will clear the lead running from this hole to the base. Each coil should be coated with coil dope.

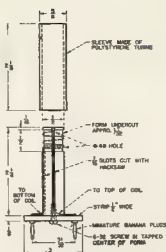


Fig. 2—Dimensions for the Dipper plug-in coil forms.

When selecting the material for the coil forms and the sleeves, be sure the sleeve will slide snugly over the rod. Before installing the sleeve, the coil dope must be dry to prevent smearing of the sleeve. Slide all but 1" of the sleeve over the coil form and, to cement it in place, put a drop of coil dope on either side of the form at the base of the sleeve. Slide the sleeve on until the top is flush with the top of the coil form. Place a coat of coil dope over both the edge of the sleeve and the coil form at the top.

The coil form is screwed to the plug-in base; however, coil dope should also be used as cement at this point to prevent accidental twisting of the rod and subsequent breaking of the leads running to the banana plugs. The banana plugs shown are those used in the ARCS series of surplus equipment and are press fit and peened in the plug-in strip. Other types of banana plugs may be used.

Dimensions of spacing for the banana plugs are given, but these should be first checked against the actual spacing between the receptacle holes after the coil posts are mounted.

The dial for the instrument is made of 1/16" thick lucite and is 2¼" in diameter. The fiducial line is scribed across the diameter and is then filled with black wax crayon. The dial is screwed to a standard ¼" knob which is supplied with three screw holes for this purpose. Before the regular dial is permanently mounted, a substitute

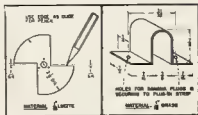


Fig. 3 (left)—Substitute calibration dial to enable marking of the permanent scale. Fig. 4 (right)—Dimensions and method of construction for 210 to 975 Mc. inductance.

calibration dial is first installed. This is shown in Fig. 3. It is cut out along its diameter to permit marking of the scale during calibration, using this edge as a guide for a hard pencil. The scale is made of white Bristol drawing board and is cemented to the case.

## TESTING

Before testing the Dipper, connect an ohmmeter to the two terminals on the 117v. a.c. plug. Turn on the filament switch, and without the 9002 in its socket, the ohmmeter should read 430 ohms. This is the total series resistance of the line cord resistor and the parallel filament resistor. If this reading is not obtained, the filament resistor is not connected across the filament terminals. This should be checked to prevent damage to the tube. If the ohmmeter reads around 40 ohms, the resistor leg of the line cord is most likely incorrectly connected.

If the filament circuit is properly hooked up, insert the tube in the socket, plug the line cord into the 117v. a.c. line and turn on the filament switch. The 9002 filament should light. Measure the filament voltage at the socket terminals. It should be 6 to 6.3 volts.

As a personal safety measure, connect a 1000 ohm-per-volt a.c. voltmeter between the instrument case and ground (water pipe, radiator, etc.). If no reading is indicated on the meter, reverse the a.c. plug. The voltmeter reading should be no more than 10 volts. If the voltage is higher than this, either there is a short between the case and one side of the 117 volt line, or the isolating bypass C7 is incorrectly wired or of the wrong value.

Insert the lowest frequency coil into the posts and turn on the plate switch. Grid current should be indicated on the meter and should vary between 0.6 mA. and 0.9 mA. over the tuning range of the variable condenser. The other coils should be checked in order. It will be noticed that the grid current will be higher with the next lower frequency coil and then will drop off as each higher frequency coil is used. The highest frequency coil will vary between 0.1 and 0.3 mA. In all cases the grid current variation should be gradual.


The plate voltage should be measured between the B+ terminal on C5 and the negative side of C8-C9. This should be approximately 117 volts. If the grid meter reading is too high (off scale) when using the lower frequency coils, it may be reduced by increasing the value of the grid resistor R1.

## CALIBRATION

Calibration may be made using either an absorption-type frequency meter, a calibrated receiver, or a receiver in conjunction with a secondary frequency standard.

The following method is employed with the absorption meter. First, to check the range of each coil, set the Dipper capacitor at minimum and, with the absorption meter loosely coupled to the Dipper coil, adjust the absorption meter to the point where the Dipper's meter shows a marked dip. This then indicates the highest frequency obtainable with the particular coil in use. The same procedure is followed for checking the low frequency

(Continued on Page 45)

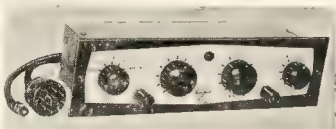

## THE NEW


# AEGIS PRE-AMPLIFIER

## MARK 2

High sensitivity! Beautiful ultra modern panel INPUTS for tape, microphone, radio tuner, pick-up, with pre-set input control. Independent selection of TS and L.P. playback curves. Tape re-record and playback jacks on front panel, together with input selector switch, bass and treble controls and volume control with mains switch. Incorporates two EF86 valves. Size 12 x 3 x 1 1/2 inch. £26/15/6

*Australia's own Brand*

**EQUAL TO THE  
WORLD'S BEST**

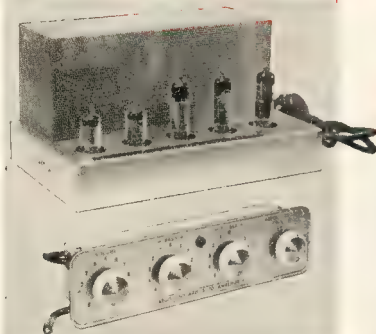

## HIGH-FIDELITY EQUIPMENT

also entirely suitable for

## STEREOPHONIC SOUND REPRODUCTION

### AEGIS 5-10 ULTRA LINEAR BASIC AMPLIFIER

If you're interested in experimenting and building your own hi-fi system, here is the essential part of your equipment. The overall size of the Amplifier is 11 1/4 x 8 1/2 x 6 inches. VALVES: 1 x EF86 low pentode input stage, 1 x 12AX7 double triode phase splitter, 2 x 6AQ5 pentode push-pull output stage, and 1 x 6V4 full wave rectifier. £40/5/0

Two Aegis 5/10's with the new Dual Control Head is the ideal combination for Stereo!

### AEGIS AMPLIFIER CONTROL UNIT

Incorporates input selector switch for tuner and pick-up, bass and treble boost and cut controls and volume control (without AC mains switch) on attractive front panel. Recommended for crystal pick-ups and tuners only. Measures 12 x 3 x 1 1/2 inches. £7/17/6

CONTROL UNIT for adapting 5/10 for Stereo £17/15/0

- Other AEGIS HIGH-FIDELITY UNITS available include PRE-AMPLIFIER Mark 1 FIDELITY TUNER Mark 1 (incorporates OWN POWER supply). FIDELITY TUNER Mark 2 (power drawn from existing amplifier).

Manufactured  
in Australia by

**AEGIS MANUFACTURING CO.**

PTY.  
LTD.

208 LT. LONSDALE STREET, MELBOURNE, C.1, VICTORIA

PHONE: FB 3731

Agents in all States. If you have difficulty in obtaining Aegis Products, WRITE US DIRECT!

## (Continued from Page 11)

The above explanation is only an effort to help you understand what happens in this circuit. Even though you may not understand all of this or may not have even seen an oscilloscope, there is no reason why, by following a few simple ground rules, your end product can not be good.

It has always been a source of amazement to me that following the articles in "QST" in 1951 on d.b.r.c. there was not an immediate interest developed in this new technique. On paper it looks like the answer to the "holy man's" prayer, at least it does, however, I believe that I know the answer. Those few of us that tried d.b.r.c. in an effort to obtain peak efficiency operated in the 300-400% modulation range. At this level, except when the fellow receiving the signal uses a crystal filter or Q multiplier in a receiver (it's called carrier's exception) the sidebands are balanced between the carrier and sidebands) the audio distortion is quite pronounced.

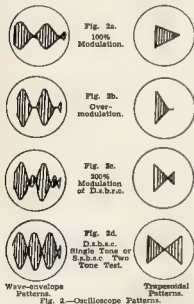


Fig. 2.—Oscilloscope Patterns.

When using d.s.b.c. most stations worked, even before being given information on my rig, remarked on the audio level being high in comparison with the carrier. One station said recently, "My S meter shows S3 but your audio sounds like 20 db. over 8". Others remarked that my signal stands

I do not want to go into detail on d.s.b.c. except to say that the results have exceeded my expectations. Anyone familiar with the technique of receiving s.s.b. has little or no trouble

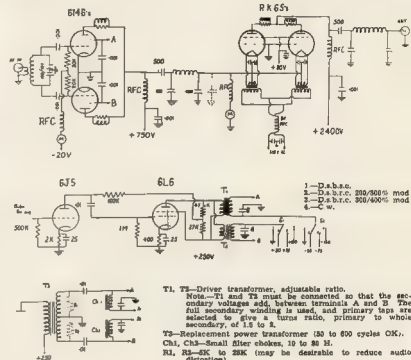


Fig. 3.—"TAS Special"

Now on the practical side of things. I will try to give sufficient information so that without test equipment you can duplicate my results. For best results your receiver should have good frequency stability and should have at least a crystal filter, Q multiplier, or some other method of giving you sharp band-pass. Two or three kc's. is about optimum. If you would like to check your receiver on some s.a.b. signals, back off the r.f. gain, open up the audio gain and listen on the b.f.o. for the best results 1 time m.s. b.f.o. pitch control approximately 1000-1500 cycles plus or minus depending on the sideband (upper or lower) and tune the

The v.f.o. exciter used in my case is a re-built Command Transmitter (BC 457) with 1-3 watts output on 40, 20, 15 and 10 metres. The only requirement to remember here is that the



The pi-network between the balanced modulator and the grounded grid linear was used to make possible a good impedance match and to permit adjusting the load of the balanced modulator. The proper loading of both the balanced modulator and the linear amplifier is the real key to success in this transmitter.

There are a number of ways to isolate the filament of the grounded grid final from r.f. ground. My method is a compromise to make it possible to use existing parts. A bifilar wound choke in the secondary might be better (commercial units are available in the U.S. from Barker and Williamson, Inc.). My filament transformer was a high voltage rated open-frame type with two 2½ volt windings in series. The capacity between the secondary and primary was approximately 100 pF. This gave satisfactory results on 40 and 20 without the r.f. choke in the primary. However, the additional choke was necessary to reduce losses on 15 and 10 metres.

When the linear was first tried, both the control grids and the screen grids were directly grounded, which gave a static plate current of only 20 Ma. at 2,400 volts (others have reported static plate currents as high as 40 Ma.). As I found the linear somewhat hard to drive, I tried using positive voltage on the screen grids and found 90 volts to be optimum. In my case this gives me 100 Ma. standing plate current on the two 6K6s. It was easy to drive the linear to a full kw. peak input under these conditions and having a meter to read screen grid current was a real boon to loading and resonating the final. Unless some method is available to indicate r.f. power out, tuning for maximum screen grid current is the only way to be sure the final is at resonance.

## TUNING UP

Now we are ready to tune up the rig. I hope, for the sake of your fellow Hams, that you have a dummy load for this purpose. If you are fortunate enough to get hold of some "Globar" non-inductive resistors, or the equivalent, you will find that it is worthwhile to duplicate the simple unit (Fig. 4) that I used. Electric light bulbs are a last resort as their resistance varies with input.

In any case, start off with the balanced modulator coupled to a dummy load or antenna. Approximately 50 ohms is best as that is close to the input impedance of the grounded grid linear. Use Position 3 for tuning up, adjust the drive to the grid circuit for approximately 5 to 6 Ma., dip the final and increase loading by reducing the output capacity of the pi-network while keeping the final in resonance until the power output no longer increases with an increase in loading. At this point you should have approximately 45 Ma. plate current. There is only a relatively small increase in plate current from the no-load conditions.

Now, slowly increase the audio gain until the plate current is kicking up to about 75 Ma. on voice peaks. To be sure you are not "flat topping", a sharp whistle should drive the plate current to approximately 150 Ma. If the plate current does not go up high enough on

a whistle, a further increase in loading should do the trick. This setting should give you approximately 250% modulation.

A word of warning here if you do not want your tubes (6146s) to go soft as my first pair did. In spite of the relatively low plate current, it is easy to exceed the safe plate dissipation of the 6146 with positive a.g. voltage operating as it is at relatively low efficiency. In an effort to get more output from my balanced modulator on d.s.b.c. I tried operating at 900-1000 volts. The slight show of red on the plate should have been warning enough, however, it was not until my tubes started to go soft after about three months of operation that I decided that 800 volts was my limit on Position 3. 900 volts was found to be safe on Position 2. With d.s.b.c. (Position 1) I have found that my full 1100 volts is quite safe. When going to Positions 1 and 2 from Position 3 a slight reduction in audio is necessary. In Position 2 the standing plate current will be approximately 38 Ma. with 900 volts and voice peaks will hit between 60 and 90 Ma., depending on the percentage of modulation desired. In Position 1 a standing plate current is about 30 Ma. at 1100 volts and the plate meter hits approximately 100 Ma. on voice peaks.

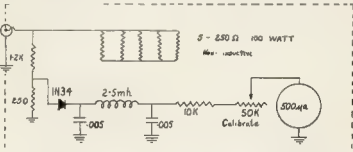


Fig. 4.—Dummy load with output meter. Meter calibrated for 150 r.f. volts at full scale.

At this point some "on-the-air" checks, using the balanced modulator, is in order, or better still, check your own signal as I did. With the rig loaded into a dummy antenna and the antenna removed from your receiver check for distortion products (splatter). If you happen to have a sharp receiver with an S meter and a 1000 cycle signal audio tone to excite the transmitter, switch to Position 1 and increase the audio until the plate current is approximately 100 Ma. With the crystal filter or Q multiplier in a sharp position, locate one of your fundamental sidebands and adjust your r.f. gain so the S meter reads approximately 40 db. over 9. Now tune slowly away from the carrier frequency one kc. off you will find your second order distortion product. One kc. further you will find your third order distortion product, and on down the band you will hit fourth, fifth, sixth, etc., distortion products.

Being careful not to damage your tubes, this test should be repeated with 150 Ma. plate current. In my case, with 150 Ma. plate current, I found the second and third order products down

approximately 40 db. on the S meter of my HRO-60, and down to about S5 or 60 db. down on the seventh order products. This was almost too good to be true as 25 db. down on the second and third order is not considered too bad. Rough on-the-air checks showed very low distortion products but I doubt if it is as good as the —40 db. indicated by my tests. The adjustment that did the most in reducing my distortion productions (from 20 to 40 db down) was the reduction of the fixed bias on my balanced modulator from —60 to —20 volts. I do not know exactly why this should have made so much difference.

We are now ready to load the grounded grid amplifier. When connected to the final, the loading of the balanced modulator should be re-adjusted using the same procedure as outlined above. This is necessary because the input impedance of the grounded grid linear will probably be different from your antenna or dummy load used in the previous test. Using Position 3 again, load your final much the same way as you did the balanced modulator. It will be necessary to increase the loading up to or past the point of maximum output. When properly loaded in Position 3, speech audio will result in the p.a. plate current kicking up from approximately 160

Ma. to 275 Ma. and whistles up to approximately 400 Ma. These, and other current figures, are for 15 metres and somewhat higher but proportional readings will be found on lower frequencies. The check for distortion should be repeated as before. If the final amplifier is operated properly, little or no increase in distortion products will result. In my case, I do not find it necessary to make any adjustments in loading between Positions 1, 2, and 3. A reduction in loading of the balanced modulator and grounded grid linear will probably be necessary in Position 4 for best efficiency on c.w.


Although my versions of the "TA2 Special" may be too much power for most, for those who wish a simpler and lower power version, I would suggest a pair of 6BQ6s or 6DQ6s for the balanced modulator with two or three 837s for a grounded grid linear, as shown in Fig. 1. This would give something in the order of 200-300 watts input. The 837s are "tried and true" in grounded grid service, and the 6BQ6s worked well in d.s.b.c. and should be okay for d.s.b.c.


(Continued on Page 46)




# PERFORMANCE PROVED TRANSISTORS

## IN THE NEW JETEC 30 CASE

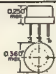PNP GERMANIUM GENERAL PURPOSE RADIO FREQUENCY TRANSISTORS Temperature Range —65° C to +85° C		JETEC-30 Type	V <sub>CE</sub> max volts	I <sub>CB</sub> avg. mA	h <sub>FE</sub> ave.	C <sub>ob</sub> avg. pF	f <sub>T</sub> <sup>a</sup> ave. MHz
		2N413	—18	2.5	25	12	70
		2N414	—15	6	40	12	80
		2N416	—12	10	60	12	90
		2N417	—10	20	80	12	100


PNP GERMANIUM GENERAL PURPOSE AUDIO TRANSISTORS Temperature Range —65° C to +85° C		JETEC-30 Type	V <sub>CE</sub> max volts	h <sub>FE</sub> ave. small signal	Power Gain Class A dB	I <sub>CO</sub> ave. mA	Noise Factor ave. dB
		2N422	—20	90	40	6	6 max
		2N464	—40	22	40	6	12
		2N465	—30	45	42	6	12
		2N466	—20	90	44	6	12
		2N467	—15	180	45	6	12

PNP GERMANIUM AUDIO RADIO RECEIVER TRANSISTORS Temperature Range —65° C to +85° C		Type	Circuit Usage	Supply Voltage max. volts	Power Gain	
					Class A dB	Class B dB
		2N359	Output	—16	40 <sup>a</sup>	37 <sup>b</sup>
		2N360	Output	—16	37 <sup>a</sup>	34 <sup>b</sup>
		2N361	Output	—16	34 <sup>a</sup>	31 <sup>b</sup>
		2N362	Driver	—16	41 <sup>a</sup>	—
		2N363	Driver	—16	37 <sup>a</sup>	—

### BASE DIAGRAM KEY

1. EMITTER
2. BASES
3. COLLECTOR

<sup>a</sup> @ 50 mV, 5 volt supply    <sup>b</sup> @ 120 mV, 5 volt supply    <sup>c</sup> @ 1 mV, 5 volt supply

PNP GERMANIUM IF AND RF RADIO RECEIVER TRANSISTORS Temperature Range —65° C to +85° C		Type	Circuit Usage	V <sub>CE</sub> max. volts	I <sub>CB</sub> max. mA	f <sub>T</sub> <sup>a</sup> ave. MHz	C <sub>ob</sub> pF	Gain dB/Hz	Conv. Gain dB
		2N481	Osc.	—12	10	70	12 ave.	—	—
		2N482	IF	—12	10	80	12 ± 2	31	—
		2N483	IF	—12	10	90	12 ± 2	35	—
		2N484	IF	—12	10	100	12 ± 2	39	—
		2N485	Conv.	—12	10	80	12 ave.	—	26
		2N486	Conv.	—12	10	90	12 ave.	—	30

### PLEASE NOTE :

Type 2N481 replaces ... 2N111    Type 2N484 replaces ... 2N271A    Types 2N113A, 2N362, 2N363, 2N417, 2N422,  
 " 2N482 " ... 2N111A    " 2N485 " ... 2N112    2N483, 2N485, 2N360 and detector diode  
 " 2N483 " ... 2N112A    " 2N486 " ... 2N271    1N295 available now through your wholesaler.

### SOLE AUSTRALIAN AGENTS

## ELECTRONIC INDUSTRIES IMPORTS PTY. LTD.

139-143 Bouverie Street, CARLTON - - Phone: FJ 4161

#### SYDNEY

713 Parramatta Road,  
Leichhardt, N.S.W.  
Phone: LM 6327

#### BRISBANE

52 Bowen Street,  
Brisbane, Q'land.  
Phone: B 6462

#### ADELAIDE

90 Grote Street,  
Adelaide, S.A.  
Phone: LA 5295-6-7-8

#### PERTH

68a Railway Parade,  
West Perth, W.A.  
Phone: 283111

# AMATEUR TELEVISION

## PART EIGHT

BY E. E. CORNELIUS,\* VK6EC/T

### A VIDEO OSCILLOGRAPH

During early experiments with a flying spot scanner on 243 lines and a 1 Mc. bandwidth, a Dumont c.r.o., with a bandwidth 3 db. down at 100 Kc. was used. This provided a severe limitation, and over a period, a number of requirements for a c.r.o. suitable for this work, were formulated. These were—

1. Y channel flat to 5 or 6 Mc., calibrated in volts per inch.
2. Sweep—a hard valve time base for reliable triggering, calibrated in frequency, and a triggered sweep for pulse measurement, calibrated in time, with calibrated trigger time delay.
3. Z axis modulation facility.
4. Direct on plates shift controls.
5. "Earth free" operation facility.
6. Zero line insertion.
7. Remote power supply.

These features were all incorporated, but each had its price, either in complexity or cost.

1. A 6 Mc. bandwidth involved low gain video amplifiers, with power tubes as deflection amplifiers, to obtain adequate deflection. This called for a sizeable power supply, about 250 mA. Using push-pull 6CL6s with 400 volts h.t., only 2" undistorted Y deflection could be obtained at 6 Mc. bandwidth.

This is adequate, but for greater deflection, the anode loads are switched in steps to permit up to 6" deflection, with a 2 Mc. bandwidth. To maintain 6 Mc. bandwidth, with high input impedance, at all levels, a compensated step attenuator was introduced at the input socket, at the front panel. It is switched on 1, 3, 10, 30, 100, basis feeding a cathode follower. This enables a low impedance co-axial to be used to take the signals to the rear, where the main amplifier is situated. It also permits the use of a potentiometer type gain control, also calibrated in voltage, as a vernier, near the main amplifier.

This amplifier is a 6AU6, 6CK6 to push-pull 6CL6s, all using standard video techniques. The 6CL6s are a "long tailed pair" push-pull circuit, with signal injected to the grid of one. This leaves the grid of the other unused, which permits a useful facility outlined in 3 below.

At full bandwidth, the maximum sensitivity is 0.4 volt per inch, and 0.13 volt per inch on the 2 Mc. bandwidth. It was not considered worthwhile to add another video stage for greater sensitivity. For gain stability, and a stable display, regulated h.t. was now essential.

2. X Deflection.—A reliable hard tube time base was incorporated using a Miller circuit, with a range from 10 c.p.s. to 200 Kc. The deflection amplifier is a 6SN7, also in a "long tailed pair" circuit. The Miller transistor readily lends itself to triggered operation, but this, together with the trigger delay facility, is costly in tubes, nine being required, counting the sync. amplifier.

This could be simplified considerably, by a diligent search of the literature and considerable thought and experiment, but as it has worked well for three years, I have not as yet made time to attempt simplification.

The beauty of the Miller circuit is that the sawtooth is remarkably linear and almost completely independent of tube parameters, and provided regulated h.t. is used, with stable components, can be calibrated accurately in frequency, time, and time delay.

As the fastest triggered sweep is 20  $\mu$ sec. and must be linear, the deflection amplifier has to be reasonably wide-band. This limits the X amplitude to about 7". This has been no disadvantage. On triggered sweep, the sweep width is adjusted by the components always to be 4", and the width control bypassed. The trigger delay is also directly calibrated in time from 5  $\mu$ sec. to 17.5 msec., by calibrated potentiometer, and multiplier.

3. Z axis modulation (c.r.t. grid) was considered to be a desirable feature, but has hardly ever been used. But it was seen on design, that it would be easy to switch the Z amplifier to the otherwise unused grid of the Y deflection amplifier, and effectively have two independent Y channels.

This amplifier is a single 6AC7 with about 1 Mc. bandwidth, and has proved invaluable for a type of "double beam" display for waveform superimposition, but without any separation of the two traces. No compensated input attenuator is provided, the high impedance input being direct to the grid of a cathode follower and then via co-axial cable to a low impedance gain control to the amplifier input at the rear. This circuit limits the input voltage to the effective grid base of the cathode follower, about 25 volts peak to peak.

4. Direct on plate shift controls mean that the shift potentials are fed direct to the c.r.t. plates, independently of the amplifiers. This avoids the probability of distortion on extreme shifts, when the shift potentials are fed through the amplifiers, but involves dual potentiometers and slight sluggishness of the shift.

5. In t.v. it is often desired to observe a waveform of low amplitude at a circuit point at high d.c. potential, possibly with ripple superposed. This is particularly so when measuring the current in line and frame deflection circuits. The normal power supply ripple, or ripple caused by the line or frame time bases themselves, can completely mask the waveform to be seen, when measured against earth.

It is advisable therefore to be able to lift the whole c.r.o. circuit above earth potential and operate the earthy terminal at (say) h.t. potential (complete with ripple). This leaves the desired waveform clean for observation. The practice can be highly dangerous, of course, unless precautions are taken.

The whole of the power supply circuit, and c.r.o. "innards" are left free of earth and the c.r.o. chassis assemblies

insulated from the main case, which is earthed. A 0.1, 600v. capacitor is connected between the c.r.o. earth and true earth, with a panel-mounted switch across it.

Throwing the switch to "FREE" (open) allows the low potential connection of the c.r.o. to be connected to points up to 600 volts "hot", the only hazard then being the c.r.o. input terminals themselves, in this case co-axial connectors, which are insulated from the case and as protected from accidental contact as possible. A worthwhile refinement would be to have a conspicuous red panel lamp to light under "EARTH FREE" conditions.

This facility has proved invaluable, and is in use continuously. Note that many of the test points (t.p.) shown in earlier circuits have been at high potential, and in these cases the c.r.o. is clipped across the measuring resistor under "free" conditions.

6. Zero Line insertion was discussed in Part Seven last month. The vibrator is plugged into its socket which is close to the Y, (Z) input (the narrow bandwidth channel) and short circuits the co-axial input socket for dotting in the baseline. It was included in this channel to avoid adding extra capacitance to the wide band Y channel. Not that this vibrator must be connected directly across the input connector, as any point after a coupling capacitor loses the d.c. component it is designed to show.

7. By the time all these facilities were included, the total of tubes was considerable and power supply requirements in proportion. The proximity of a 500V 1A power transformer always raises the problem of shielding the tube, so it was decided to use a separate unit for the power pack and mount it remotely, on the floor for instance. This minimised trouble from magnetic deflection of the c.r.t. and made two units of reasonable weight, easier to handle than one very heavy unit.

### CIRCUIT

The circuit is shown in Fig. 40.

#### Y Amplifier

V1A and B, mounted on the Y attenuator shield, are the two input cathode followers, co-axial cables leading to the rear panel, where the video amplifiers are located. The Y<sub>1</sub> channel is V2, V3, feeding the grid of V4, which with V5 is the deflection amplifier. V2 and V3 use I.R.C. 1000 ohm 3w. wire wound resistors for anode loads, which provides excellent compensation in this layout, flat to 6 Mc. Pure chance of course! V4 and V5 also use the same resistors for anode loads, 2000 ohms for 6 Mc. bandwidth, 4000 ohms for 3 Mc. and 6000 ohms for 2 Mc. Additional shunt inductors are switched in for the narrower bandwidths. The 20 ohm cathode resistor provides bias, and the 1000 ohms the "long tail" for cathode drive to the second tube.

The grid of V5 is normally earthed to signal by a 0.5  $\mu$ F. capacitor, but via

\* 157 Wood Street, Inglewood, Western Aus.

# BOOKS FOR RADIO AMATEURS!

The Radio Amateur's Handbook 1958. The standard manual of Amateur Radio Communication. A.R.R.L.	48/3
Australian Radio Amateur Call Book 1958. W.I.A.	5/9
Radio Amateur Call Book U.S.A. Quarterly. Every Call Sign in the World	67/6
P.M.G. Handbook of Regulations for Operators	3/6
Radio Operator's License Q. & A. Manual—Kaufman	69/9
Broadcast Operator's Handbook—Harold E. Ennes	57/6
Novice and Technician Handbook—Wm. Orr, W6SAI	35/6
A.M.E.C.O. Amateur Radio Theory Course	46/9
Beam Antenna Handbook—Wm. Orr, W6SAI	34/-
Better Shortwave Reception—Wm. Orr, W6SAI	34/-
So You Want To Be a Ham—Robt. Herisberg, W2DJJ	26/9
Getting Started in Amateur Radio—J. Berens, W2PIK	25/6
The Radio Amateur Report Pad	8/6
Surplus Radio Conversion Manuals, Vols. 1 and 2. Each	36/-
Command Sets. Compiled by Editors of "CQ"	20/3
Radio Amateur DX Guide. Just Arrived!	20/-
A.M.E.C.O. Question and Answer License Guide	7/-
A.M.E.C.O. Mastering the Morse Code	10/6
Single Sideband Communications—Field Engineering	56/6
Panel Signs—Permanent Paint Transfers—Three Sets, 1. Receivers and Amps; 2. Test Insts; 3. Panel Words	6/6

## A.R.R.L. PUBLICATIONS:

The Radio Amateur's License Manual	8/9
Learning the Radiotelegraph Code	4/-
Hints and Kinks for the Radio Amateur	17/9
A Course in Radio Fundamentals	18/-
Single Sideband for the Radio Amateur	25/-
The A.R.R.L. Antenna Book	31/6
The Mobile Manual for Radio Amateurs	40/-
The New "CQ" Mobile Handbook—Wm. Orr, W6SAI	37/3
"CQ" Magazine, 8/- per copy. Yearly	60/-
"QST" Magazine, 6/- per copy. Yearly	49/6

## RADIO FOR BEGINNERS:

Questions and Answers on Radio and T.V.	10/9
A Beginner's Guide to Radio—Camm	13/3
A First Course in Wireless—"Decibel"	20/9
Wireless for Beginners—Boltz	16/9
Radio for Boys—Crystal Sets and Simple Receivers	16/6
Fun With Radio. Simple Projects and Circuits	16/9
The Boys' Book of Radio, T.V., and Radar	15/9

## VALVE AND TRANSISTOR MANUALS:

R.C.A. Receiving Tube Manual	11/-
R.C.A. Transmitting Tube Manual	14/9
Philips Valve Data Book	19/9
Philips "Minivatt" Transistors and Diodes	7/3
Raytheon Transistor Applications, Vol. 2	10/9
How to Make a Transistorised Portable—Sylvania	6/6
Crystal Diode Circuit Kinks—Sylvania	8/-
Early Uses for Germanium Diodes—Sylvania	8/-
Transistors and Other Crystal Diodes—How To Use	8/-

## RIDER ELECTRONIC TECHNOLOGY SERIES:

R.F. Transmission Lines; L/C Oscillators; Wave Propagation; Limiters and Clippers; Crystal Oscillators; Amplitude Modulation; A.M. Detectors. Each Priced at	13/9
Frequency Modulation; F.M. Limiters and Detectors. Es.	11/6
Multivibrators 10/3; Electrostatics 14/9; Vacuum Tube Rectifiers 16/9; D.C. Circuit Analysis	15/-
Superheterodyne Converters and I.F. Amplifiers	11/-
Antennas 17/9; Impedance Matching	28/6

## RADIO SERVICING:

Wireless Servicing Manual—Cocking New Edition	39/6
Practical Wireless Service Manual—Camm	38/-
Radio Upkeep and Repairs—Witts	24/9
Australian Radio Service Manual, Volume 14	25/6

## GENERAL RADIO:

Radio Handbook—Editors and Engineers. Latest Edition	88/-
Foundations of Wireless—Scroggie, New Edition	26/6
Radio Laboratory Handbook—Scroggie. Sixth Edition	43/6
Wireless Fundamentals—Armitage	33/6
Outline of Radio, T.V., and Radar. Eleven, etc.	38/9
Practical Wireless Encyclopedia—Camm. 13th Edition	28/-
Radio Data Charts—Beatty and Sowerby. 5th Edition	13/6
Basic Mathematics for Radio and Electronics	30/3
Basic Radio Course—Frye	24/9
V.H.F. Radio Manual—Keller	51/-
Frequency Modulation—Keen. 1958 Edition	49/6
Frequency Modulation Simplified—Kiver	77/-
Newnes Short Wave Manual—Camm	11/-
Short Wave Radio—Reynor	17/6
The Superheterodyne Receiver—Witts	10/6
Worked Radio Calculations—Witts	20/9
Wireless Terms Explained—Decibel	5/6
Practical Wireless Circuits—Camm	30/3
Radio Circuits Step by Step—Miller	9/6
Wireless Coils, Chokes, and Transformers—Camm	11/-
Radio Receiver Circuits Handbook—Squire	22/6
Mathematics Essential to Electricity and Radio—Cooke and Orleans	55/6
The Superhet. Manual—Camm	13/3
Radio Receiver Design—Sturley	57/6
Radio Receiver Laboratory Manual—Levey	21/9
Radio Electronics Made Simple—Martin Schwartz	24/9
U.H.F. Antennas, Converters and Tuners—Kiver	16/3
Introduction to Valves—"Wireless World"	15/3
Electrical Interference—Hale	28/-

**NOTE!** All prices quoted include postal and packing charges. These amounts deducted if goods purchased at shop. Remit by Cheque, Money Order or Postal Notes, but not C.O.D. Please.

# TECHNICAL BOOK & MAGAZINE COMPANY

295-299 SWANSTON STREET, MELBOURNE, C.I., VICTORIA

S4 can accept signal from V6, as the 1 Mc. bandwidth Y<sub>1</sub> channel, for that second input. The arithmetic sum of the waveforms is displayed, the two traces not being separable on a true double beam basis, but very useful for al. that. The other position of S4 allows grid modulation from V6, for marker pips, or switched free for convenience. The Z (Y<sub>2</sub>) input co-axial connector has the zero line vibrator across it, as mentioned earlier.

#### Time Base

The time base can run either under continuous or triggered conditions. Under continuous sweep, V7, 16, 17 and 18 are used. V7 is a sync. amplifier, reasonably wide band, with either internal sync. (from the cathodes of V4, 5) or external sync. from the sync. input socket. It feeds to V16, a Miller integrator, followed by V17, a cathode follower. The cathode follower is in series with the Miller capacitor, selected by S9. It has a number of advantages, among them a considerable improvement in fly back time, and its low impedance output.

On continuous sweep, a 0.047  $\mu$ F. capacitor is switched between screen and suppressor of V16, by S10A and S10C. This provides a transition circuit for free running, sync. being injected at the screen. The sawtooth frequency is controlled by the time base fine and coarse controls, arranged to multiply each other, and is taken from the cathode of V17 via a co-axial cable and width control to V18. This is another "long tail" circuit, with unequal plate and equal bias voltages, swings and unequal bias on the grids, for optimum grid base for each tube half.

#### Triggered Sweep

On "Trigger", V16 is no longer free running, the screen being bypassed, and a "gate" pulse is applied to the suppressor through a diode biasing circuit (V15B). The Miller tube is cut off, with high anode potential, until arrival of the trigger, when the suppressor goes positive, and the anode potential falls linearly until the gate is again closed, by suppressor cutoff, the anode flies positive, until the next trigger. A negative going sawtooth, of duration fixed by the gate pulse width and amplitude fixed by the Miller capacitor (selected by S17), is available from the cathode of V17.

The generation and control of the gate pulse is the job of the circuitry of tubes V8 to V15 inclusive. The trigger signal is amplified as before by V7 and fed to V8 via S5B. The two diodes are poled and biased to conduct at a specific voltage, preset by the potentiometers under S8B, and polarity selected by S6.

On conduction of the diode, V9 cycles. This tube is a flipflop, emitting a negative pulse of duration about 4  $\mu$ secs., on receipt of a trigger. Switch S6 selects either the positive going or negative going component of the triggering pulse, and switches other circuits to maintain correct polarity throughout. S8A selects the appropriate input polarity. S8B alters the bias on V9A so that this stage is cutoff before a positive pulse, or conducting before a negative. S6C and S6D select the negative going anode of V9 for either

polarity input, feeding it to the delay circuit V10, 11, or undelayed to V13.

**Trigger Delay.**—This is another flip-flop whose cycle duration is under control from the panel by the switched delay capacitors in 57A and the fine control, a 2 megohm potentiometer designated "MICROSECONDS". V12A acts as a clamp for the suppressor of V10, to ensure the suppressor always returns to earth potential, preventing random variations in pulse length and hence the delay, causing "jitter".

V13 accepts the delayed or undelayed pulse, it being differentiated to a spike by the 14 pF., 47K circuit in its grid. The tube amplifies and inverts the pulse, and the spike, now positive, is fed via V12B to the gate flip-flop V14. This cycles on each spike, emitting a square gate pulse, positive going, from the anode of V14B.

Two outputs are taken from the anode, one clamped by V15B to cut off the suppressor of the Miller tube, and the other clamped to +110 volts, to the c.r.t. grid, as a "brightenup" pulse for brightening the trace for the duration of the sweep.

The tricky parts of this circuit are:—(1) The trigger flipflop V9, where some juggling of the values of the cathode resistor and the grid resistor of V9B (shown as 33K) may be needed. (2) The gate flipflop, where similar juggling is necessary for the grid resistor of V14B, shown as 220K and 1M in parallel.

On triggered sweep, the X gain control is bypassed, as it can distort the short duration sawtooth. The width of the trace is adjusted as close to 4" as possible by adjustment of the value of the capacitors switched by S8B. Then, with 4" of sweep for each duration, the graticule will measure specific times. For instance, on 20  $\mu$ secs., it will be 5  $\mu$ secs. per inch.

With triggered sweep, the beam is undeflected till a trigger pulse is received, then sweeps across the screen at the predetermined rate and then awaits the next trigger pulse. No trigger, no sweep. The sweep delay acts as a very fine and flexible sweep expansion, as varying the delay moves the whole display bodily across the screen. A delay of 1000  $\mu$ secs. on a sweep of 20  $\mu$ secs. is possible, and equal to an expansion of 50 times—17 feet!

#### Power Supply

No circuit of this is given as it conforms closely to the other power units described. It supplied +400 volts unregulated at 100 mA., +200 volts regulated at 120 mA., +110 volts regulated at 20 mA., —2000 volts from an r.f. e.h.t. supply, and —70 volts for bias of V13. This last is obtained by having the whole of the filter system in the negative leg, using it as a back bias resistor. With the components used, this gives —70 volts, and the components of V13 were adjusted to suit. As in the c.r.o. proper, the earth bus floats and is connected through to the c.r.o. cabinet for safety, there via the "EARTH FREE" switch.

The filament supplies are similar to other circuits, allowing adequate insulation for the 5BP1 filament, and a separate winding for V4, 5, 11 and 18, this being kept at +110 volts, to reduce heater cathode potential in these tubes. The +110 supply is derived from a

series regulator tube which has its grid held at +105 volts from the 0C3 reference tube used for the main regulator, similar to the +150 supply in the c.e.u. power pack.

#### Mechanical

To provide the "earth free" facility, the whole of the c.r.o. circuitry was mounted on a separate inner carcass, mounted within and insulated from, the metal outer case, which measures 14" x 10" x 8". See Fig. 41.

The inner carcass was therefore constructed as follows:—A set of 5 vertical panels, all to the same outside dimensions of 13 1/2" by 9", with 3/4" flanges all round, are used as chassis and mounting panels. They are spaced at intervals shown in the sketch and held in place by angle pieces at each corner from front to back. Each panel is drilled to suit the tubes and components that are to mount on it, with clearance holes for the extension shafts running forward to the front panel.

The carcass has four transverse bakelite bearers 3/8" x 1 1/2" x 3/16" which are in turn screwed to it at top and bottom, front and rear. These bearers are later screwed to the outer metal cabinet, thus serving to support the carcass inside and insulating it from the case proper. Clearance is provided between the front panel and the front of the case, this last having rubber grommets in 3/8" holes, to support and insulate the shafts projecting through it.

The front panel mounts:

1. The Y<sub>1</sub> attenuator and cathode follower.
2. All co-axial input sockets.
3. The zero line switch and vibrator.

Panel (2) mounts:

1. The c.r.t. shield, and hence the tube itself.

Panel (3) mounts:

1. All the time base circuits, tubes and panel controls.
2. The trigger plus and minus threshold preset controls.

On panel (4) we have:

1. The Y<sub>1</sub> amplifier, deflection amp. and controls.
2. The Z-Y<sub>2</sub> amplifier, access switch and controls.
3. The shift, focus and intensity pots.
4. The astigmatism preset control.

Panel (5), rear, carries the two power receptacles (chassis male) for connection to the external power pack and is back about 3" from the rear of the case, which has large clearance holes for inserting the plugs.

Fig. 41 shows the major details of each of panels 1 to 4. Fig. 42 shows the front panel as designated. Note that the front panel of the case has clearance holes for the four co-axial inputs, these being the only danger points under "earth free" conditions.

The first panel has the Y<sub>1</sub> attenuator in a shield case shown dotted, which encloses the Z-Y<sub>2</sub> input, and mounts the 12AU7 cathode followers on its rear. The 3 to 30 pF. trimmers on the attenuator are placed so that they are accessible for adjustment via the side doors of the case, for adjustment in situ. The vibrator socket, on standoffs, is immediately above the attenuator box. A cutout at extreme left allows





clearance for the "earth free" switch, which is the only component mounted on the front of the case proper.

Panel 2 has no components and is mainly used for support of the front of the c.r.t. shield, and the tube. The shield, fixed by brackets to this panel is made of two concentric funnels of 20 gauge galvanized iron, the inner conforming to the shape of the c.r.t. and lined with tinfoil. The outer slides firmly over it, spaced by a piece of felt. This provides a shockproof mount and grips the tube lightly but firmly.

Panel 3 is for the time bases, with all tubes and electrolytics (coded C on the sketch) projecting forward from the panel, potentiometers and switches being on the rear. The layout is not critical, but that shown allows reasonable access. The wiring of these panels

can be done on the panel as a unit, enabling testing to be done in the clear before assembly. For the time base coarse switch S9 and the trigger duration switch S8, an extra dummy wafer was used as a convenient tag plate for the capacitors. Holes coded X, Y, S, on the sketches, are for the co-axial cables from panel to panel.

Panel 4 has the deflection and e.h.t. circuitry, with the e.h.t. network at the top right hand corner, behind the focus potentiometer. The switched anode loads of the 6CL6s are on narrow horizontal tag strips supported by the tube sockets and the "DIVIDE BY" switch. Decoupling and screen dropping components are mounted remote from the tubes on a strip behind the X shift potentiometer. A full length strip across the bottom is used for termination of

the power leads and for power distribution. Each of the three active panels 1, 3 and 4 have captive power plugs and free sockets on short cords, to carry power forward between panels.

#### Cathode Ray Tube

A calibrated graticule for this c.r.o. is easy to make and invaluable. The front panel of the instrument has a 5 1/2" hole, through which the tube may be inserted or removed. It is arranged such that the front of the tube is just flush with the inside of the panel. A circular disk of 1/16" perspex fits neatly into the hole and rests firmly against the front of the tube.

A cast brass c.r.o. bezel from a radar indicator (using a 5FP7) is screwed to the front panel, retaining the perspex

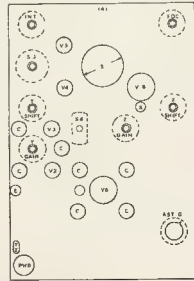
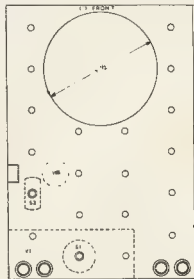
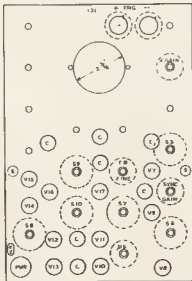
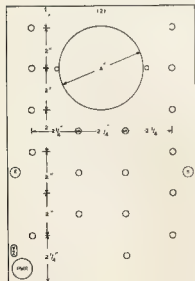
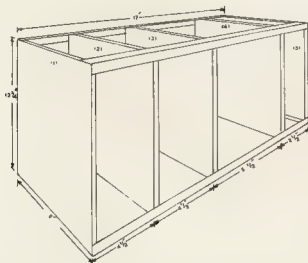


FIG. 41-CONSTRUCTION

# "Q-PLUS" TV KIT SETS

## NOW AVAILABLE IN 4 "EASY-TO-PAY-FOR" STAGES

INSTRUCTION MANUAL IS NOW AVAILABLE FOR 11/6.  
THIS AMOUNT WILL BE REFUNDED TO YOU IF YOU  
PURCHASE A KIT

### STAGE 1

MAIN CHASSIS and  
FRAME COMPONENTS. ALL TRANS-  
FORMERS and  
CHOKES, BOLTS  
NUTS and WASHERS  
SOCKETS, KNOBS,  
ION TRAP FUSE,  
FUSE HOLDER.

#### PRICE

17" £23.5.0

21" £26.5.0

INCLUDING  
SALES TAX


### STAGE 3

SPEAKER  
Q-PLUS I.F. STRIP  
90 deg. YOKE  
POTENTIOMETERS

#### PRICE

£32.8.9

INCLUDING  
SALES TAX

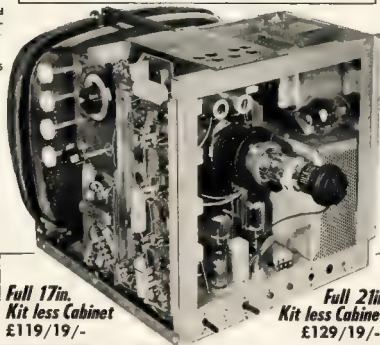

*Full 17in.  
Kit less Cabinet*  
£119/19/-

*Full 21in.  
Kit less Cabinet*  
£129/19/-

ALL PRICES INCLUDE SALES TAX.

### STAGE 2

RESISTORS  
INDUCTORS  
TAG STRIPS  
CAPACITORS  
HOOK-UP WIRE  
SOLDER

#### PRICE

£10.10.0

INCLUDING  
SALES TAX

### STAGE 4

Q-PLUS TURRET  
TUNER VALVES

#### PRICE

£33.8.9

INCLUDING  
SALES TAX

TO COMPLETE YOUR PROJECT "Q-PLUS" WILL SHORTLY RELEASE

★ CABINETS ★ SAFETY GLASS ★ MASKS

### "Q-PLUS" NOW ANNOUNCE THE RELEASE OF THEIR TESTED "Q-PLUS" TV TURRET TUNER

- ★ COVERS ALL AUSTRALIAN CHANNELS 1-10
- ★ FULL BANDWIDTH
- ★ FULL 360 DEG. 12 POSITION SELECTOR
- ★ COMPLETELY TESTED AND ALIGNED
- ★ LOW "Z" LINK OUTPUT
- ★ FEATURES NEW HIGH Mu LOW NOISE SUPER CASCADE R.F. AMPLIFIER CIRCUIT
- ★ OSCILLATOR COMPENSATED FOR FREQUENCY DRIFT DUE TO TEMPERATURE VARIATIONS
- ★ HOLDING BAR PREVENTS SILVERED CONTACTS FROM RUBBING AGAINST BISCUIT AT THE SAME TIME ALLOWS MAXIMUM TENSION TO BE APPLIED TO WIPERS
- ★ SPECIAL IMPORTED HI-STABILITY LO-LOSS "ALKYD" RESIN USED ON BISCUITS
- ★ COIL FORMERS THREADED PREVENTING TUNING CORES BECOMING LOOSE
- ★ NEW TYPE CIRCUIT GIVES MINIMUM NOISE, MAX. GAIN AND HIGH STABILITY
- ★ LO-LOSS AERIAL INPUT FILTER WITH INBUILT 36 MEG. VIDEO TRAP ENSURES EXCELLENT REJECTION OF FREQUENCIES BELOW CHANNEL 1



#### PRICE

£14/5/6

Q PLUS KITS ARE AVAILABLE NOW FROM ALL RADIO, T.V. DEALERS SPECIALISING IN KITS  
OR FROM THE MANUFACTURERS, WHO HAVE A SPECIAL QUERY SERVICE FOR ALL BUYERS.

*Demonstration Kits may be seen in operation at these Addresses:-*

**R. W. STEANE & Co. Pty. Ltd.**

SYDNEY: 8 Cadow St., Pymble, JX3556.

MELBOURNE: 2A Montrose St., Auburn. WB3377-8-9

in place, but allowing rotation with the tips of the fingers for alignment with the trace. The perspex is engraved on the inside, using a sharp scriber, with 1" and 1/10" calibration lines, the 1" marks being deeper than the others. These scribed grooves are filled in black, using a finger moistened with Indian ink, the surplus being polished off when dry.

To improve contrast, a light filter of dark green cellophane is fixed to the tube face itself as described in Part Two for the camera viewfinder, but due to tube face curvature, rather more care is necessary to stretch the cellophane without tearing it. The filter reduces incident light considerably, but passes the green trace almost without loss, enabling the c.r.o. to be used in quite high light levels.

## CALIBRATION

After a functional test to ensure that all parts function normally, calibration of the measuring circuits can be done as follows.

### The Y Attenuator

The resistor values for this unit should be accurately measured, and while absolute values are unimportant, the ratio of each pair should be accurate, 1:2 for the 3 range, 1:9 for the 10 range, and so on. The attenuator is frequency independent if the series arm R.C. is equal to the shunt arm R.C., this last absorbing strays. For h.f. compensation, the series trimmer C<sub>1</sub> is adjusted as follows:

Apply a square wave to the input, from the square wave generator described last month, at between 5 Kc. and 15 Kc. If the square wave is obtained from any other source, it must be above suspicion and without overshoot, or rounding. Display the square wave on the one volt per inch range, on 8 Mc. bandwidth, via an attenuator pad made up with resistors of 100 ohms or less, thus ensuring that there is no frequency discrimination there. Use short leads and low capacitance cables. The square wave should be perfect, with no overshoot, undershoot, or rounding.

Set the attenuator to the 3 volt range and adjust the series trimmer to give no overshoot or rounding. The transition will be quite clear and sharp. Check the 10 volt and 30 volt ranges similarly, removing the pad to obtain 1" or more deflection. On the 300 and 1000 volt ranges, compensation is difficult due to the low voltage available, but with the Y gain control full on, and 1" on the screen, accurate setting of the compensation is possible. The "DIVIDE BY 3" range may be used, if need be, on the higher ranges to obtain greater sensitivity.

### Y Gain Control

Inject a 50 cycle a.c. signal of say 50 volts r.m.s., measured on an accurate a.c. voltmeter. This is  $5.0 \times 2.8 = 14$  volts peak to peak. Set the Y attenuator to the 10 volts/inch range. Set Y gain to give 1.4" deflection (DIVIDE BY 1 position), and mark Y attenuator setting 1.0.

Using a potentiometer, reduce input to 1 inch (10 volts). Increase Y gain to give 2" deflection and calibrate this point as 0.5. Follow this pattern similarly to give other convenient calibration points.

### Time Base (Continuous)

This assumes that all time base capacitors have been checked on a bridge before fitting. Check points on one range will then agree on all other ranges. Set coarse range to 1. Inject 50 cycles per second and display two sine waves, with the absolute minimum of sync. gain to hold the pattern, using the time base fine potentiometer. Calibrate this point 25. Display 3, and calibrate this point 17, 4 for 124, and 5 for 10. Using other known frequencies, or the more complex Lissajous figures, find the other calibration points on the fine pot, between 10 and 40.

### Trigger Adjustment

Inject a low level pulse signal such as line pulses, at about 4 volts level to both Y and SYNC. inputs. Adjust sel-

ector to + polarity, and adjust positive trigger threshold selector to give a stable display, with minimum sync. gain. Keep backing off the sync. gain and readjusting the trigger threshold for a stable display until the trigger loses control. Repeat for the negative triggering position. These settings, once found, will not need major adjustment, although an occasional touch up for very low level or very high level signals may be necessary.

On high speed sweep—20 microseconds for instance—the triggering signal itself must have a sharp leading edge. A stable 20  $\mu$ secs. sweep from a 50 c.p.s. sine wave trigger is not possible, but is quite feasible from the good sharp 50 cycle driving pulses from your sync. generator.

(Continued on Page 48)

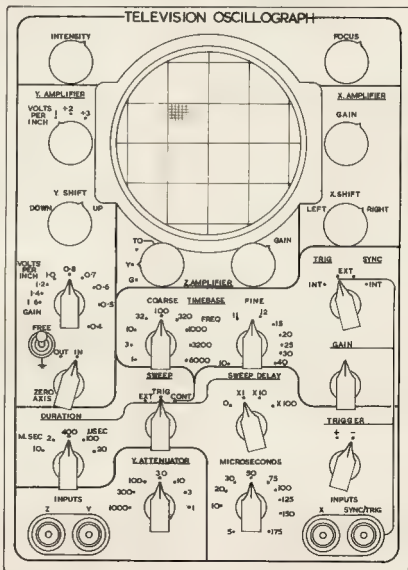


FIG 42—FRONT PANEL

# SERVICEMEN!

make your service  
pay, by using the  
latest in test equipment

from the most comprehensive range of test  
equipment available for immediate delivery.



## ADVANCE

H1, Audio Oscillators.  
62, Radio & TV Oscillators.  
65, FM-AH Oscillators  
Q1, TV Oscillators.  
P1, Radio Service Oscillators.  
T1, "Q" Meters.

## ASTOR

TV1, C.R. Oscilloscope.  
Pattern Generator.

## AVO

Multi-meters.  
Vacuum Tube Voltmeter.  
New Res. Cap. & Inductance  
Bridge.  
Valve Testers, Probes.

## BELCLERE

Portable C.R. Oscilloscopes.

## B.W.D.

Crystal Calibrator.  
Comb. Sweep, Marker and C.R.O.

## COSSOR

Sweep and Marker Generator.  
C.R. Oscilloscope.

## GOSSEN

Multi-range Ohm-meters.  
Insulation Testers.  
Transistor Testers.

## HANSEN

Multi-meters.

## HARTMANN & BRAUN (Grundig)

Multi-meters.  
Bridges.  
Sweep and Marker Oscillators.  
C.R.O's.  
Electro-Medical, etc.

## KLEMT

Field Strength Meters.

## KLEIN & HUMMEL

Pattern Generator and Test  
Oscillator.

## MASTER

Panel Instruments.

## METRIX

C.R. Oscilloscopes.  
Sweep Generators.  
Mutual Cond Valve Testers.

## PALEC

Exposure Meters.  
Multi-meters.  
Ohm-meters.  
Power Analysers.  
Vacuum Tube Volt-meters.  
Probes.  
Valve Testers.  
Picture Tube Adaptors.  
Panel and Switchboard  
Instruments.

## SANWA

Multi-meters.

## SEAL

Field Strength Meters.

## TAYLOR

C.R. Oscilloscopes, 31A and 32A.  
Probes, H.V. and Xtal.  
Oscillators, T.V., R.F., Sweep.  
Audio, Gradation, etc.  
Pattern Generators.  
Multi-meters, 71A, 77A, 88A,  
120A, etc.  
Picture Tube Adaptors.  
R.C. Bridge.  
Vacuum Tube Voltmeter.  
Insulation Tester.

## TELE-EQUIPMENT

720, C.R.O. for T.V.

## UNIVERSITY

Multi-meters.  
Panel Instruments.  
Current Transformers.  
Pattern Generators.  
Signal Tracers.  
Vacuum Tube Voltmeters.  
Probes.  
Battery Testers.  
Meter Stands.  
C.R. Oscilloscopes.

Ask for our test equipment specialist, Mr. Harry Braidwood,  
or write for prices and catalogues, etc.

# RADIO PARTS Pty. Ltd.

PHONE

FY 1251


City Depot at 157 Elizabeth Street, Melbourne.





KNOW YOUR OWN W.I.A. DIVISION

# NEW SOUTH WALES

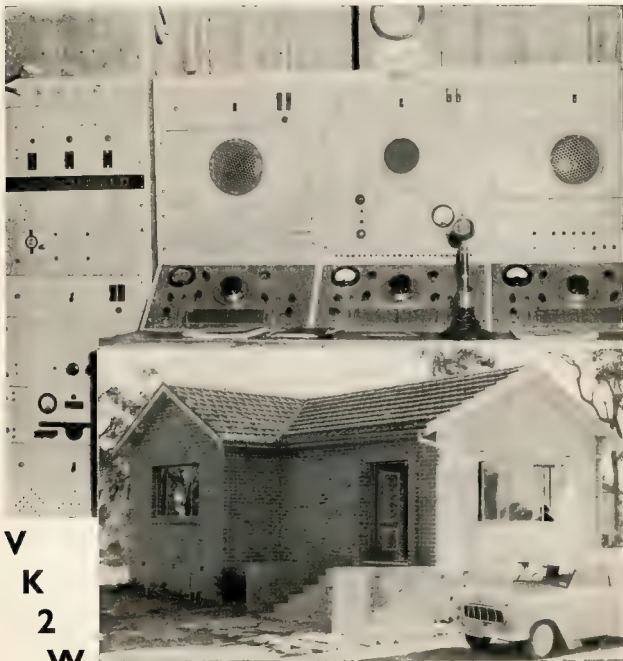

The Official Station of the New South Wales Division and Central Control Station of the W.I.C.N. organisation in that State. Top: Operating Console in the VK2WI Control Room. Bottom: Main Building housing Divisional transmitting and receiving equipment, together with library and other facilities.

# V K 2 W I

## Headquarters Station of the VK2 Division and Central Control Station of W.I.C.E.N. in New South Wales

**I**N Clause 3 of the Memorandum and Articles of Association dated 26th May, 1922, setting out the aims and objects of the New South Wales Division of the Wireless Institute of Australia, Paragraph (g) deals with the establishment of Club Houses and Workshops for use by Members.

It is thirty-six years since these thoughts were put on record. Since then through the efforts of Members in recent years, these thoughts have become an actual fact.

The N.S.W. Division now has an official central focal point located on a five-acre property in Quarry Road, Dural, at the top of a ridge 750 feet above sea level, twenty miles northwest from the heart of Sydney.

The main building is brick tee-shaped construction of 500 sq. ft.; provision has been made to extend to 1,000 sq. ft. This building houses all the transmitting and receiving equipment

together with the library and kitchen facilities.

Situated 150 feet to the rear of the main building is a 25 x 14 ft. steel frame building housing a 25 kva. three-phase emergency power plant, work benches and general storage area; underground cables connect the power plant to the main building.

### ANTENNAE

Placed in suitable positions well clear of the main building are six 60 ft. tubular steel masts carrying 80, 40, and 20 metre dipole antennae.

Separate receiving and transmitting antennae are used on these bands, feeders to the transmitting antennae are co-axial cable, run underground to junction boxes on 8 ft. steel poles directly underneath the antennae. From these boxes to the antenna any suitable type of feeder can be used and matched to the co-axial cable.


The v.h.f. antennae consists of a 144 Mc. four-bay turnstile on a 60 ft. pipe mast, for general coverage. A sixteen element phased-array and a five element yagi on 56 Mc., fully rotatable, on top of a 45 ft. pole are close to the main building. The phased array and yagi have been constructed from standard t.v. antenna fittings and, like the turnstile, are fed with co-axial cable, terminating on an Antennae Patch Panel in the Control Room.

### BUILDING

The main building is divided into three sections. The section immediately inside the entrance has the library, kitchen and dining facilities and is furnished with modern chromed steel framed chairs and tables.

The second section contains five operating positions for h.f. and v.h.f. bands and are being fitted out for general use by Members, also multi-

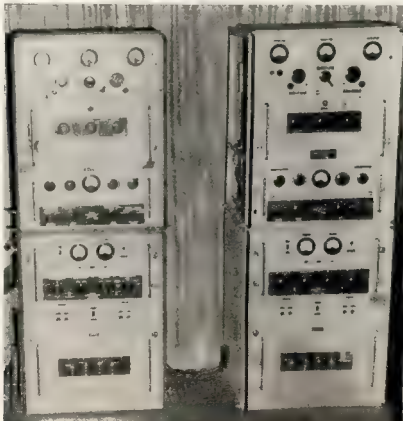★  
Looking through the control room doorway at the two AT14 350-watt h.f. transmitters.  
★



★  
Not shown on the left is a BC810E 500-watt h.f. transmitter. To the right of the AT14's is the v.h.f. transmitter rack.  
★

band call-backs after Divisional Broadcasts and W.I.C.E.N. activities, when a number of channels are operated simultaneously.

The transmitters, together with their modulators and power supplies, will be mounted in standard 6 ft. racks, while the receivers and operating controls will be mounted on the operating desks.

The third section is partitioned off from the other sections by double glass and acoustic wall board and is the VK2WI Control Room. The walls are draped from ceiling to floor with green floral-patterned tapestry, with a matching floor covering.

## EQUIPMENT

The equipment consists of a BC610E 500-watt plate modulated transmitter, two AT14 350-watt grid-cathode modulated transmitters for the high frequency bands, and 100-watt 144 Mc. transmitter.

The operating console has three AR7 receivers, together with operating controls for all transmitters, patching panel from audio splitting amplifiers for modulators and public address system, speakers for each receiver,

mounted in this rack and is used for remote control of the VK2WI transmitters during W.I.C.E.N. exercises and broadcast relays.

Alongside the AT14 h.f. transmitters is a 6 ft. standard rack containing the 100-watt 144 Mc. transmitter together with its power supply and class AB1 807s modulator. Provision has been made for the installation of a 56 Mc. 100-watt transmitter which is in the course of construction.

Each Tuesday night at 8 p.m. a W.I.C.E.N. Exercise is carried out when Stations throughout N.S.W. discuss problems associated with emergency work and practice message handling. The frequency used is 3525 Kc.

The purchase of the property and the construction of the building has been made possible by cash donations from Members, while a very large percentage of the equipment has been donated to the Station by Members. The



Above View of the rear of the main building where the control room is. The open window is one shown on left of the kitchen view. Left: Interior view showing kitchen curtain and on left the partition and doorway to the VK2WI control room.



microphone and tape recorder input controls.

Mounted on the rear of the console are power supplies for the receivers and radio amplifiers, together with supplies for relay-controlled circuits for the transmitters.

A standard 7 ft rack adjacent to the operating console contains the antenna patching panel for the h.f. receivers and the v.h.f. transmitters and receivers, also the 144 Mc and 56 Mc converters together with their associated power supplies. Provision has been made for patching the output of v.h.f. converters to the antenna input of the AR7 receivers. A complete 5 metre receiver, which is interconnected with the relays controlling the h.f. transmitters, is

Test equipment includes a Bendix frequency meter, 5 inch cathode ray modulation checker, monitors, crystal calibrator, multimeters, modulated oscillator, and grid dip oscillators.

## ACTIVITIES

The main activities connected with VK2WI are the Divisional Broadcast each Sunday morning at 11 a.m. when simultaneous transmissions are made on 7146 Kc., 3573 Kc. and 144.89 Mc., followed by transmission on 7050 Kc. for the purpose of taking reports from Members and giving information requested by those reporting in. Also the V.h.f. Broadcast each Sunday night at 730 p.m. on the 144 Mc. band.

work involved in modifying and re-building equipment, together with the major portion of the construction of the building, has been carried out by Members on an entirely voluntary basis.

This is VK2WI as it is at the present time, the accompanying pictures show various sections of the station and the installations. With these facilities already available and the continued interest by Members, there seems little doubt that progress will continue to be made.

The surrounding grounds are ideal for the holding of Conventions and similar Divisional activities and provide an excellent place for Members to bring families and friends for a picnic in the bush, or a location where country Members or Members of other Divisions touring by caravan could visit during their way through Sydney.

Visitors are always welcome at VK2WI and arrangements can be made for overseas Amateurs to inspect the Station at times most convenient to them. The Station is open all day each Sunday and generally Tuesday evenings. A phone call to Dural 289 will ascertain if anyone is in attendance.

Members of the VK2 Division are proud of VK2WI and its place in Amateur Radio activities.

New South Wales Division,  
Wireless Institute of Australia,  
Box 1734, G.P.O., Sydney.

# THE NEW SOUTH WALES DIVISION, W.I.A.

The New South Wales Division of the Wireless Institute of Australia was incorporated as a Company in May 1922 to cover the whole of New South Wales, Australian Capital Territory, and Lord Howe Island.

The Division is governed by a Council of seven, elected annually by Members.

Within the Divisional Organisation there is the:

Hunter Branch,  
V.h.f. and T.v. Group,  
Central Coast Section,  
Blue Mountains Section,  
Short Wave Listeners' Section.

Also several Zones, the most active being the South West and North Coast Zones

Each of these are controlled by their individually-elected Committee in liaison with the Divisional Council through one of their officers, while the Australian Capital Territory (VK1) is catered for by the Canberra Radio Society.

The objects and aims of the Division, as set out in the Memorandum and Articles of Association, is to encourage and assist all persons interested in any or all aspects of Amateur Radio and Allied Techniques.

Membership is divided into two grades.

Grade "A" ("Full Members")—Those who have obtained their Amateur Operator's Certificate of Proficiency or the Limited Amateur Operator's Certificate of Proficiency, and

Grade "B" ("Associate Members")—Those studying for their Certificates or who are interested in some aspect of Radio Science.

While Honorary Life Membership has been bestowed on those who have rendered valuable assistance to the Division or to Radio Science.

Services which are available to Members are:

- Divisional Broadcast each Sunday from VK2W1 at 11 a.m. on 7146 Kc., 3573 Kc., and 144.89 Mc. Also at 7.30 p.m. on 144.89 Mc.

- Lectures: Divisional Meeting on the fourth Friday of each month at 7.45 p.m. in Science House, Gloucester Street, Sydney.

V.h.f. and T.v. Group Meeting 8 p.m. on the first Friday of each month at the North Sydney Technical College, Gore Hill.

Shortwave Listeners' Section Meeting 7.30 p.m. on the second Friday each month at the Railway Institute Rooms, Castlereagh St., Sydney.

Hunter Branch Meeting second Friday each month, 8 p.m., University of Technology, Tighs Hill.

Central Coast Section, Gosford, third Friday each month, 8 p.m., School of Arts, Gosford.

Blue Mountains Section third Friday each month, 8 p.m., R.S.L. Hall, Springwood.

- Magazine "Amateur Radio" each month

- Divisional Monthly Bulletin.
- QSL Bureau—Inward and Outward Cards.
- Procurement of Disposal Equipment for sale to Members.
- Library of current magazines, overseas publications and text books.
- Facilities at Divisional Headquarters Station, Quarry Road, Dural.

For those requiring Educational assistance for the A.O.C.P. examination, a lecture course of 48 lectures over a period of 24 weeks is available and is completed twice each year. For those unable to attend the lectures and may be resident in any part of the Commonwealth and Territories, there is a correspondence course covering the same syllabus as the lecture course. This course can be started at any time and rate of progress is dependent on the individual. Participation in either of these courses does not require becoming a Member of the Division.

Should it be necessary as a service to the community, in the case of emergency, and in co-operation with the State Civil Defence Organisation, Members of the Division's Wireless Institute Civil Emergency Network are participating in weekly exercises on a State-wide basis with the Divisional Station VK2W1 as Central Control. Also the use of Mobile Stations in conjunction with home-based stations is being organised and further exercises planned.

During the year, apart from local functions organised by the various sections, there are six main Divisional functions:

- (1) The Annual Convention held on the Australia Day week-end in January (Eighth Annual was held at VK2W1 Dural on Jan. 25, 1958 Attendance was close to 250.)
- (2) The North Coast Convention at Urunga at Easter.
- (3) The Hunter Branch Annual Dinner and Field Day held on the Six-Hour Day week-end, in October.
- (4) South-West Zone Convention, generally held on the Six-Hour Day week-end and is held in various places in the Zone.
- (5) Blue Mountains Section's Field Day, late October at Katoomba.
- (6) Central Coast Section at Gosford during November

The Membership of the Division at the time of going to press was nearing the 1,000 and it is anticipated that by now that figure has been exceeded as the average monthly rate of increase from March to the end of August was 11%.

Membership Fees:

Full Member, £2/2/0.  
Associate Member, £1/5/0

Full details of any of the Division's activities can be obtained from the Secretary, Box 1734, G.P.O., Sydney.

Members holding office in the various sections of the Divisional organisation in 1958 are listed, but there are many more who, through their efforts, both in the past and at present time, have helped to make the VK2 Division what it is today.

## COUNCIL OF THE

### NEW SOUTH WALES DIVISION

Div. President - Pierce Healy, VK2AFQ  
Secretary - Norm Board, VK2ALJ  
Treasurer - Cedric Smith, VK2ED  
Federal Councillor & W.I.C.N. Officer - Bob Godsell, VK2ARG  
Officer in Charge of Dural, Dove, Buff, VK2GE  
Technical Education, Max Sobels, VK2GT  
Asst. Sec. - Maurice Marsden, VK2VW

### OFFICERS OF THE DIVISION

QSL Bureau Manager - Frank Hime, VK2QL  
Assistant - Allan Smith, VK2AH  
Class Manager - L. C. Parr-Smith, VK2AOJ  
Assistant to Officer in Charge of Dural, George Turley, VK2LR  
Circulation Manager "Bulletin" - Bill Lewis, VK2VR  
Hon. Solicitor - William Clark  
Auditor - Bill Yates, VK2AWY

### DIPLOMA COMMITTEE

Dr. Ains. Dan, VK2ABU  
Allan Williams, VK2FH  
Harry Solomon, VK2AJZ

### DIVISIONAL REPRESENTATIVES ON AMATEUR ADVISORY COMMITTEE

Graham Hall, VK2AGH  
Dr. Leo McMahon, VK2AC  
Lyle Woolnough, VK2GW

### HUNTER BRANCH

Branch President - Lionel Swain, VK2GS  
Vice-Pres. - Stuart Fairbairn, VK2DF  
Secretary - Charles Arghel, VK2ARV  
Treasurer - Bill Hall, VK2KT  
Branch Correspondent, Bob Reid, VK2AGH  
Social Secretary - Gordon Sutherland  
Social Treasurer - Bob Bailey

### V.H.F. & T.V. GROUP

Chairman - Jim Cumming, VK2PM  
Vice-Chairman - Bob Winch, VK2DA  
Secretary - Les Cook, VK2ZQA  
Committee - Alan Hennessy, VK2RX  
David Andrews, VK2JAW  
Members - Jim Webster, VK2ZCW

### CENTRAL COAST SECTION

Chairman - Major Collett, VK2RU  
Secretary - Reg Brook  
Educational - Rex Black, VK2YA

### BLUE MOUNTAINS SECTION

Chairman - Wal Cronie, VK2NZ  
Secretary - Bill Moore, VK2HR  
Treasurer - Norm Durham, VK2QA  
Publicity Officer - Bob Lear, VK2ASZ

### SHORT WAVE LISTENERS' SECTION

Chairman - Barney Smyth, W1A-1201  
Secretary, Barry Cartwright, W1A-1202  
Committee - Bob Luther, W1A-1206  
Members - John Dawson, W1A-1205  
David O'Day, W1A-1209

### SOUTH-WEST ZONE

Zone Officer - Jim Edge, VK2AJD

### NORTH COAST ZONE

Zone Officer - Noel Hanson, VK2AHH

### W.I.C.N. AREA OFFICERS

Area 1 - Noel Hanson, VK2AHH  
Area 2 - Jack Hill, VK2ADT  
Area 3 - Hugo Sitt, VK2WH  
Area 4 - Col. Fletcher, VK2AFS  
Area 5 - Jim Edge, VK2AJD  
Sydney Zone - Ted Howard, VK2KX  
Blue Mountains - Bob Reid, VK2AGH  
Wymong - Doug Pearson, VK2ASA

### LIFE MEMBERS

(in alphabetical order)

F Adeock - M. Berry  
J B. Corbin, VK2YC J A Pike, VK2JP  
E H Cox, VK2IG R H F Power  
D Dae, VK2EO K A Fridge, VK2RA  
P M Gwyn, VK2UX G Reed, VK2R  
W Lewis, VK2YB W P Reusnach  
W H Moore, VK2HJ L Swain, VK2CS  
R F Yates  
McKenzie, VK2JF J F Wilson  
J Moyle, VK2JU W J Zech, VK2ACP

C BATTERY

RESEARCH  
DATA

# RADIOTRONICS

A TECHNICAL MAGAZINE  
CATERING FOR ALL PHASES  
OF ELECTRONICS

TRANSISTORS AND THEIR PARAMETERS

VIDEO I-F AMPLIFIER

A SYNC CLIPPER-AMPLIFIER  
Using the RARIOTRON 15A07

HIGH  
FIDELITY

TRANSISTORS

ARTICLES BY PROMINENT ENGINEERS

TELEVISION

PLEASE SEND ME  
MY **FREE** SAMPLE  
COPY OF RADIOTRONICS

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_



AMALGAMATED WIRELESS VALVE COMPANY, 47 YORK STREET, SYDNEY



# THE "MACRON" CRYSTAL TURNOVER PLAYER CARTRIDGE TYPE H.F.11

Made in Australia to suit Australian conditions

by MACRON ELECTRONICS PROPRIETARY LIMITED, 54 High Street, Glen Iris, Victoria

## LET US LOOK AT THE FACTS:

- ★ Clip-in Insert. Can be replaced without removal of mounting bracket.
- ★ Half inch and centre mounting interchangeable with standard arms.
- ★ Robust construction with positive positioning for "Standard" and "Longplay" positions.
- ★ Non-hygroscopic adhesives used throughout in the manufacture of the crystal element.



- ★ Slip-in Sapphire stylus, interchangeable with standard makes.
- ★ Replacement stylus available, also fit other standard cartridges
- ★ High compliance, which ensures good tracking, thus resulting in low record wear.
- ★ Wide frequency response, enabling the utmost realism from modern wide-range recordings.
- ★ Attractively and safely packed in sealed clear-plastic container.

AGENTS: D. K. NORTHOVER  
115 Murray Street, PERTH, W.A.

NEIL MULLER LTD.  
8 Arthur Street, UNLEY, S.A.

JACOBY, MITCHELL & CO. PTY. LTD.  
409 Kent Street, SYDNEY, N.S.W.

Marketed by ZEPHYR PRODUCTS PTY. LTD., 58 HIGH STREET, GLEN IRIS, S.E.6, VICTORIA

We, the Staff of

## "AMATEUR RADIO SERVICE"

would like to express our congratulations on the occasion of the TWENTY-FIFTH BIRTHDAY of the Wireless Institute's Official Magazine . . .

### "AMATEUR RADIO"

Also we offer our congratulations and sincere thanks to the Wireless Institute as a whole, the staff members of the Magazine, Federal Executive, and to all those both past and present who have been linked with "Amateur Radio."

Signed

*D. C. Haberecht*

(Proprietor) for . . .

## "AMATEUR RADIO SERVICE"

605 ABERCORN, STREET, ALBURY, N.S.W.

# Applications of the Grid Dip Oscillator\*

By E. MILES BROWN, W2PAU, in collaboration with W. M. SCHERER, W2AEF

WHEN, in the course of Hamming events, it becomes necessary to seek out the cause of t.v.i., parasitic oscillations and off-frequency warnings; when that new antenna won't load the rig; when you need an r.f. signal to test out the new pre-amp; when your home workshop special does not work the way the article said it should; when by-passes just don't by-pass—then brother, you reach for the "grid dip oscillator"! Small wonder that this simple device has won a place near the top of the list of test equipment necessary for proper operation of a Ham Station.

The fields of application of the grid dip oscillator are apparently limitless. Several articles on this subject have already appeared in periodicals and a wealth of information is available in the instruction books supplied with the commercial and amateur versions of the instrument. But, despite this thorough coverage of the subject, "CQ" still receives many requests for additional information on how to use the "dipper". It is also surprising to see how often we note a fellow Amateur struggling to get an answer to his particular r.f. measuring problem, using a grid dip oscillator under conditions where it could not possibly do a good job.

The purpose of this article is to review some of the previously published material on the use of grid dip oscillators, and to attempt to point out some of the possibilities for confusion that might be encountered in their use.

## GENERAL CIRCUIT DESCRIPTION

In order to operate a device properly one must understand what it is and why it works (women drivers notwithstanding). So let's spend a little time on the general subject of grid dip oscillator design.

It is certainly safe to assume that all grid dip meters include a tuned circuit. This usually consists of a variable capacitor and a series of plug-in coils which provide a wide-range frequency coverage. The tuning dial should be calibrated—preferably direct reading in terms of frequency. The readability and ease of dial adjustment are important design factors. The accuracy of the dial determines the potential precision of frequency measurements made with the unit. The most expensive commercial jobs are hand calibrated and can usually be relied upon to have a dial accuracy of better than  $\pm 2\%$ . Somewhat poorer results might be expected from a unit with a pre-calibrated dial, although the grid dip meters examined by the authors were fairly good in this respect. The accuracy of a home-made device depends on the care taken with the initial calibration and the inherent stability of the components. No instrument of this type will remain accurate under conditions of extreme abuse, so don't expect precision from a unit which has been dropped on the floor hard enough to deform the case or con-

denser frame, or from a coil that has been too intimate with a hot soldering iron! Lastly, keep in mind that the grid dip meter is not designed to be a frequency standard.

The tuned circuit section of the grid dipper may be used as a passive absorption wavemeter. This possibility is noted here because it is often convenient to use the unit without plugging it into a power source.

The tuned circuit must be used in connection with some form of oscillator. Almost any type of oscillator circuit may be used. The most popular one for this application seems to be the Colpitts, using a split-stator tuning condenser connected between the grid and plate of a triode oscillator tube. This circuit offers possibilities for good high-frequency performance, as the tube capacitances are effectively in series. It also provides reasonably uniform feedback across the tuning range. By using resistors, rather than chokes, in the grid and plate leads, the number of stray resonances may be minimised.

The Colpitts circuit is not too well suited for very low frequency operation, but fortunately it can be converted into a form of Hartley oscillator by the addition of a coil centre tap.<sup>1</sup> The Colpitts has another advantage for dipper applications—both sides of the coil are "hot" with respect to ground. This implies that r.f. energy may be coupled from either end of the coil using local capacitive coupling.

It is worthy of note that the sensitivity of the meter has some bearing on the ultimate sensitivity of the instrument when used as an r.f. voltmeter (more on this point later). In general, it is desirable to use a sensitive meter to provide good up-scale indications of grid current without the necessity of running excessive power in the oscillator circuit.

With a tuned circuit, a tube, and a meter, we have the makings of a tuned r.f. voltmeter. Fortunately, the circuit changes necessary to adapt the oscillator to this function are very minor. The grid and cathode of the oscillator tube can act as a diode rectifier, to measure the r.f. voltage developed across half the tuned circuit. This is accomplished by simply removing the plate voltage from the oscillator. The sensitivity of this type of r.f. voltmeter will depend to a certain extent on the meter used. However, there is a definite limit to the sensitivity that can be realised, since in any simple vacuum tube diode detector, the phenomena of "emission potential" produces a small meter reading even under no-signal conditions. Signals which are small compared to this "emission potential" will generally be masked by it. This is the chief reason why most conventional grid dip meters are limited in their ability to detect weak r.f. signals. Secondly, the relatively high grid-leak resistance required for good oscillator operation tends to limit the sensitivity.

<sup>1</sup> "Extending the Range of the Grid-Dipper," Scherer, "CQ", April 1956.

## SENSITIVITY CONTROLS

To enable the r.f. meter to handle a wide range of input voltages, some sort of sensitivity control is desirable. This control is also of value in setting the indication of oscillator grid circuit to a mid-scale value. (Despite the best efforts of expert designers there is bound to be some variation of activity across any given tuning range, with the oscillator usually becoming least ambitious on the higher frequency ranges.) A variable resistor, connected as a shunt across the d.c. meter, or as a multiplier in series with it, will serve the purpose. This type of control reduces the meter sensitivity.

Given the basic tuned-circuit/r.f. voltmeter/oscillator combination described above, certain refinements practically suggest themselves. If we're going to use the unit as an r.f. detector, it might be nice to arrange a system for plugging a pair of headphones into the detector circuit to provide a means of listening to the signal being detected. This converts our instrument into a passable phone transmitter monitor. If the headphones are left in the circuit when it is switched to the oscillating condition, we have the equivalent of a regenerative receiver, which can be used for monitoring the frequency and tone of c.w. signals.

Since the oscillator generates an r.f. signal, which may be used for testing receivers, etc., it might be desirable to provide some system for applying modulation to the signal. Though a modulated oscillator probably won't produce the highest quality type of a.m. signal, it still might be useful for tests involving the receiver audio system, or for detecting and identifying the grid dipper signal.

## AS FIVE BASIC INSTRUMENTS

Summarising the material outlined above, we have shown that the grid dipper is a device capable of serving as five basic instruments:

1. **Grid Dip Oscillator (g.d.o.)**  
A calibrated r.f. oscillator equipped with a meter indicating the oscillator activity.
2. **Oscillating Detector**  
Equivalent to a simple regenerative receiver for detecting r.f. signals by the heterodyne method using headphones.
3. **Non-oscillating Detector**  
For the detection of r.f. signals using the built-in meter to measure relative signal strengths, or using headphones to detect the presence of a.m. on the signal.
4. **Signal Generator**  
To generate strong r.f. signals of known frequency. Modulation, if provided, will probably be a combination of a.m. and f.m.
5. **Absorption Wavemeter**  
A passive calibrated tuned wavemeter.

\* Reprinted from "CQ", January 1953.



# MINIATURISED RADIO & TV Components



TYPE CAE — Screw mounting stand-off variety in capacity ranges at 150 pf. min. to 3000 pf. max.




TYPE CAC 100 — Feed-thru flange mounting type can be soldered direct to the chassis or shield plate in inner coils. From 50 pf. min. to 1500 pf. max.

The disc ceramic with its short rf current path, when soldered direct to the tube terminals, reduces the inductance to very small values.



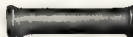Type TV high voltage disc capacitors encased in "DUPRITE" for T.V. and other high voltage applications



Ceramic, used as a dielectric, prevents instability occasioned by ionisations, pores and air pockets.

Silver electrode for maximum conductivity



Heavily tinned leads soldered direct to silver electrode



Electrodes permanently fired to ceramic complete stability at all temperatures



Ducon Potentiometer with switch



Ducon "Midwest" Paper Tubular Capacitor



Ducon Sub-miniature Electrolytic Capacitor



Ducon Miniature Metal-oxide Tubular Capacitor



Ducon High voltage Ceramic Transmitter Capacitor



Ducon Leaf-Through Discs in slotted Capacitor



Ducon "M-L" Disc Ceramic



Ducon Ferrite Rod Yokes & Cores



Ducon High voltage Ceramic Transmitter Capacitor



TYPE CAC — Feed-thru flange mounting type can be soldered direct to the chassis or shield plate in tower girds. From 50 pf. min. to 1500 pf. max.



TYPE CAE 100 — Stand-off flange mounting style mounted by soldering to the chassis. From 50 pf. min. to 1500 pf. max.



New modern Leightonfield Works provide further expansion for Ducon manufacture and expedience of delivery.



## DUCON CONDENSER LIMITED

Christina Road and Birmingham Avenue, Villawood, N.S.W. 2058

### SUBSIDIARY COMPANIES

Smaller Products Pty Limited  
Meca Products Pty Limited  
Aurum General Ceramics Pty Limited  
Ducon (N.Z.) Limited, 21 Grey St., Wellington.  
VICTORIAN OFFICE:  
Ducon Condenser Limited, 83 Wilson St., Melbourne  
INTERSTATE AGENTS  
Wm T. Matthews Ltd., 95 Grenfell St., Adelaide  
P. H. Phillips Pty Ltd., 468 Brunswick St., Brisbane  
H. J. McQuillen Pty Ltd., 7 Queen's Place, Perth, W.A.

### ASSOCIATE COMPANY:

P. R. Mallory & Co. Pty Ltd.

## THE GRID-DIP FEATURE

Let's first consider the possibilities of the unit operated as a grid dip oscillator. When an oscillator is coupled to a circuit which is capable of taking r.f. power from the oscillator, its activity will decrease. This is analogous to the situation encountered in a transmitter output stage—when an antenna is coupled to the transmitter and starts to draw power from it, the amount of r.f. voltage floating around in the final tank is reduced. Obviously, if the load circuit is tuned, it will accept power more readily at the particular frequency where it is resonant. If the grid dip oscillator is coupled to a non-resonant type of load (such as a low inductance link feeding a pure resistance) power will be accepted by the load over a wide range of frequencies, and the effect on the oscillator will be a general reduction of grid current regardless of the oscillator dial setting. It may be virtually impossible to detect resonant effects in a circuit of this nature. If, on the other hand, the oscillator is coupled to a low-loss parallel-tuned L/C circuit, power will be absorbed most efficiently at the resonant frequency of the load circuit, and a well-defined dip in the oscillator grid current will be noted as the oscillator is tuned across this frequency. The higher the "Q" of the coupled circuit, the sharper the dip.

Any electrical circuit which displays resonance effects may be investigated using the grid dipper. Parallel-tuned L/C circuits, sections of r.f. transmission lines, quartz crystals, antenna elements, filter sections, r.f. choke coils (with distributed capacity), r.f. by-pass capacitors (with lead inductance), stray resonant circuits formed by long wiring leads and their associated stray capacitances . . . the list is probably endless. Before attempting to use the grid dip oscillator to check the resonant frequency of any electrical system, it's quite important to figure out in advance just what sort of circuit is involved. Unless one can visualize the nature of the resonant circuit, it is difficult to determine how to couple the power output of the grid dipper into it.

## SINGLE TUNED CIRCUITS

Let's take a simple example—a parallel-tuned circuit consisting of a coil and its tuning capacitor. In practice, this arrangement is frequently encountered in oscillators, transmitter interstage and output tank circuits, wavetraps, circuits, v.h.f. receiver front ends, antenna tuners, etc. From experience with transmitter circuits, most of us know how such a circuit behaves when power is fed into it at its resonant frequency. If one end of the coil is grounded, high r.f. voltages appear on the other end. If the coil has a centre tap and this is grounded, both ends of the coil become hot with respect to ground. Most of us are also familiar with the means used to transfer power from one tuned circuit (the d.c. coil) into another (the circuit under test). If we can get the driver coil close enough to the driven coil we can provide mutual-inductance coupling between the coils. Tightest coupling will exist when the driving coil is actually placed inside the driven coil, with the coil axes parallel. Some degree of

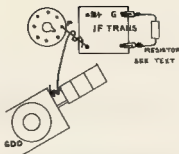


Fig. 1.—Method of checking the resonant frequency of a double-tuned shielded I.F. transformer. Note the clipped-in resistor across the other winding of the transformer, and the use of a short piece of hook-up wire wrapped around the coil prongs at the grid dipper, which provides coupling into the shielded circuit.

coupling may be obtained by placing the coils side-by-side, with their axes parallel. And that's the logical way to approach a simple single-tuned circuit with the grid dip oscillator.

However, suppose the coil is inside a shield can, or is so arranged that we can't move in close enough to it with the dipper coil? Well, what do we do in a transmitter in order to get power from a driver stage into the following grid coil when we can't arrange the layout so the coils are close together? One way out is to use capacitive coupling. Since both the grid dipper tank circuit and the circuit under test are high-impedance circuits (at resonance), the amount of coupling capacitance required to transfer power between the hot ends of the coils may be very small.

Occasionally, adequate capacitive coupling may be obtained by bringing the end turn of the dipper coil, or one of the coil plug leads, close to a hot lead on the tuned circuit under test. If this is not sufficient, a little extra capacitance may be added in the form of a "gimmick" (Fig. 1), made by wrapping one end of a short length of insulated hook-up wire around one of the coil prongs of the dipper, and the other end around one of the hot leads on the tank circuit under test. The loosest possible coupling should be employed, since the added stray capacitance on the grid dipper coil will tend to upset its dial calibration. The wire should be insulated at both ends—it merely provides a small amount of coupling capacitance and an extension lead between the dipper and the circuit under test.

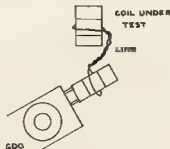


Fig. 2.—Coupling by means of a short link.

Another means of transferring power between two widely-separated tuned circuits is by link coupling (Fig. 2) and this system may also be used with the grid dipper. In fact, some commercial models of the dipper are furnished complete with a small link-coupling device. In general, the links should be small, and exhibit as little self-inductance as possible, in order to avoid resonance effects in the links themselves. The transmission line between the links should be short, for the same reason.

It often happens that the parallel-tuned circuit under investigation is not composed of a single coil and compact capacitor, but rather consists of stray-type reactive elements. For example, we often employ r.f. choke coils to serve as blocking devices to prevent r.f. currents from flowing into a circuit. It is desirable to have an r.f. choke look like a very high impedance at the frequency it is supposed to block. The highest impedance obtainable in an r.f. choke occurs when it looks as if it were a parallel-resonant circuit. Resonance effects are present because the distributed capacitance between coil turns acts like a tuning capacitor across the coil winding.

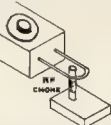


Fig. 3.—This is the method of determining the natural resonant frequency of a common v.h.f. r.f. choke coil. In this case, the choke is acting as a parallel-tuned circuit, in which the capacitance is formed by the stray capacitances between the individual turns of the coil. Note that both ends of the choke coil should be insulated from ground and dressed away from grounded objects.

We can therefore treat the r.f. choke like a combination of inductance and capacitance, and "dip" it just like any other tuned circuit. In Fig. 3, which illustrates this application of the dipper, mutual inductance coupling is employed, and both terminals of the choke coil are insulated from ground. Multiple-winding chokes may display more than one resonance.

The converse of the case just described might be a capacitor with distributed inductance in its leads or internal structure. In an r.f. by-pass circuit we generally desire the lowest possible impedance from the by-passed point to ground. At low frequencies, most capacitors look and act like capacitors—the effects of lead lengths, etc., are negligible. But at very high frequencies, the inductive effects are noticeable, and the impedances of the by-pass actually rises with increasing frequency. It is often handy to know at what frequency the inductive and capacitive effects tend to cancel out and produce the best by-passing action. This can be checked by connecting the ends of the capacitor leads together to form a one-turn loop, which can be treated as a simple parallel-tuned cir-

# **The All-New VHF HANDBOOK**

**BY WILLIAM I. ORR, W6SAI  
AND HERBERT JOHNSON, W6QKI**

**The First Complete Handbook devoted to the  
Very High Frequency Spectrum!**

THE VHF HANDBOOK covers in detail the generation, propagation and reception of VHF signals. Four chapters are devoted to all modes of VHF propagation, including detailed information about "beyond-ionosphere" and moon-echo transmission. Three chapters cover the field of VHF circuitry, receiver design, and receiver construction. Many types of VHF receiving equipment, together with full construction information are shown, including the "ultimate" preselector having a noise figure better than 2 db!

Two chapters are devoted to VHF transmitter design and construction—covering the power range of 2 watts to a kilowatt unit designed for moon reflection work! Other chapters cover VHF test equipment and the discussion of noise figure and noise generators.

THE LATEST COMPLETE, UNPUBLISHED DESIGN INFORMATION FOR LONG YAGI PARASITIC ARRAYS IS GIVEN FOR THE FIRST TIME IN THE VHF HANDBOOK! COMPLETE DESIGN CHARTS AND CONSTRUCTION INFORMATION ARE INCLUDED. ALSO SHOWN IS NEW THREE-BAND VHF BEAM FOR 50-144-220 Mc.!

**PRICE 36/- plus 1/3 postage**

**ORDER NOW!**

**McGILL'S  
AUTHORISED NEWSAGENCY**

**183-5 ELIZABETH STREET, MELBOURNE, C.1, VICTORIA**

"The Post Office is Opposite"

**PHONES: MY 1475-7**



cuit. The dipper can then be inductively coupled to the single turn loop (Fig. 4).

The resonant frequency as determined by this method is actually the frequency of best by-passing action, but it should be remembered that at frequencies above the resonant point the capacitor acts more like an r.f. choke! The approximate resonant frequency depends so much on the type of capacitor being choked that it is impossible to estimate the frequency range in which you should start looking; typical paper-roll type units may resonate in the low megacycles, micas may go up into the hundred megacycle or so range, and some of the tiny ceramic units now available will probably resonate beyond the range of most Ham dippers!



Fig. 4.—Using the g.d.o. to check the resonant frequency of a paper tubular capacitor with the leads short-circuited. The dip may be hard to find on some units because of their high Q at resonance.

Even the simplest single-tuned circuit displays "parasitic" resonances. The coil, as we have pointed out, has distributed capacitance between its turns. The leads to the tuning condenser and the frame of the condenser have inductance. Thus, in addition to its main, low-frequency resonance, the circuit will exhibit additional resonances where the v.h.f. effects come into play. Such resonances are often a serious problem in high-powered transmitter circuits where the components are necessarily large. Coupling the grid dipper to these "invisible" resonant circuits is a problem that requires the use of good judgment and common sense, because it is next to impossible to predict just where the "coil" section of the parasitic resonance is located and where the "condenser" is! In fact, these circuits quite often do not take the form of "coils" and "condensers" but rather are more similar to transmission lines; a condition which merits a separate discussion.

To best approach such a set-up, couple the grid dipper coil as closely possible to the wiring loop formed by the leads between the coil and the capacitor. In the case of a transmitter, the "capacitor" might well consist of the tube capacitances and not the big variable! After a little experience you'll be able to judge quite accurately where the long leads will resonate, and where the "hot spots" of the parasitic circuit are located. There's no set rule. We can't even say that the plates of the tubes are "hot" at the v.h.f. resonant frequency because of the long leads inside the tube. Fig. 5 shows a typical approach. We were able to couple sufficient energy by placing the dipper coil close to one plate lead, which probably gave a combination of inductive and capacitive coupling. Here's a good point to remember: when such a situa-

tion as this exists, it is often possible to increase the coupling by reversing the position of the coil in the grid dipper—it may produce addition, not cancellation, of the two modes of coupling.

It's wise to spend a little time after you build a new rig searching out the various stray resonances. It pays off. The unit had a strong resonance right in the middle of t.v. channel 7. It would have been a darned sight easier to make minor changes in the wiring layout to QSY that peak to a less occupied frequency than it would be to shield the entire transmitter to the extent that would prevent radiation of the strong channel 7 harmonic! By luck, however, the grid circuit of this particular rig resonated on a different frequency. If it had resonated on channel 7 also, think of how difficult it would have been to clean up that tendency of v.h.f. oscillations.<sup>2</sup> Similar remarks apply to receiver circuits. It took a grid dipper to locate the stray resonance in an r.f. choke used in the plate circuit of our two-metre r.f. amplifier which was causing said r.f. stage to pass along more noise at the i.f. of 7 Mc. than signals at 144 Mc!



Fig. 5.—Checking the frequency of a stray resonant circuit formed by the leads between the plate cap and the associated circuit elements in a medium power transmitter. The coupling in this case is probably a combination of inductive coupling to the loop formed by the leads, and capacitive coupling between the dipper coil leads and the plate cap of the tube. It was no surprise to find it resonating in the middle of t.v. channel 7!

Before leaving the subject of single-tuned circuits, a few practical operational tips are in order. Generally, when attempting to "dip" circuits associated with tubes, the filaments as well as the plates should be off. This is due to the fact that the grid and cathode of any tube act as a diode. This diode, connected across a tuned grid circuit, can so "de-Q" the circuit that the dip on the g.d.o. meter may be broadened beyond the point of recognition. Another illustration of this problem is the input coil of a grounded grid r.f. stage. Under normal operating conditions the coil acts as if it is loaded by a parallel resistance of about 100 ohms! It's vitally important, however, for proper performance of the stage, that it be tuned to resonance.

Antenna coupling circuits (in transmitters and receivers) should be checked without the antenna connected, at first, since the antenna will load the

coil and may introduce spurious resonance effects. At the higher frequencies, when the antenna is disconnected, the coil will most likely be detuned because of stray reactances in the antenna connector system. We usually pull out the input link or un-solder the tap on the input coil to be on the safe side.

When working in the close confines of modern miniaturized chassis, it may be hard to tell whether the grid dipper is actually coupled to the desired tuned circuit or to some other circuit resonant near the same frequency. The quickest way to check this point is to de-tune the desired circuit slightly, using its trimmer, or by touching a "hot" section of said circuit with the tip of a wooden lead pencil. (We've found that a "subtle" de-tuning of this nature is more indicative of resonance on the v.h.f. bands than the "brute force" method of shorting the coil with a metal screwdriver or the like. Admittedly, more drastic de-tuning than the pencil provides may be required on low-Q low-frequency circuits!) This sort of test probing may also furnish interesting information on the distribution of r.f. voltages around the circuit. The "hotter" the point of contact of the pencil tip, the more noticeable the reaction of the grid dip meter.

## TRANSMISSION LINES

In some ways, transmission lines act like simple tuned circuits. Consider a length of transmission line with one end open-circuited and the other short-circuited. At some frequency this line will appear to be quarter-wavelength long. If power is coupled into the transmission line at this frequency, the line will behave like a simple parallel-tuned circuit. A high r.f. voltage will appear across the open-circuited end, and high current will flow through the short circuit.

Knowing the physical length of a transmission line and the "velocity of propagation" factor for that type of line (obtainable from the handbooks or the manufacturer's catalogues), we can calculate the frequency at which the line will be a quarter-wavelength long. On the other hand, knowing the resonant frequency (which we can easily measure with the grid dipper) we can determine the effective length. A full wavelength in space (expressed in metres) is equal to 300 divided by the frequency in megacycles. To convert metres to inches, multiply by 39.4. The wavelength in a transmission line is less than the wavelength in free space, so to get the length of transmission line equivalent to a wavelength in air we simply multiply the wavelength in air by the "VP" of the line; which may run around 0.95 for flexible co-axial line, around 0.80 for twin lines, about 0.99 for open-wire lines, etc.

The grid dipper can be coupled to a shorted section of transmission line by considering the shorting jumper as a low inductance link, and coupling the dipper to it. In the case of co-axial cable, it may be necessary to form a small loop of the inner conductor outside the shield when short-circuiting the line, to provide a link to couple into. If it's impossible to get at the shorted end of the line, measurements may be made at the open end, by using capacitive coupling techniques as described

<sup>2</sup> Orr, "The Cure and Elimination of Parasitic Oscillations," Dec. 1950. This is a must for the transmitter designer!

for simple tuned circuits. This method is disadvantageous in that the added capacitance de-tunes the transmission line as well as the g.d.o.

A transmission line which is not short-circuited at either end can resonate as a half-wavelength section. To check this mode of resonance, we should couple to the centre of the line, though it may be difficult to obtain enough coupling. Try reversing the coil, if at first the dip is not sufficient. Obviously, in the case of co-axial lines at half-wavelength resonance, we cannot couple in the centre, so we must couple on an end, using capacitive coupling techniques.

Everything that was said above with regard to quarter-wave line sections also applies to  $\frac{3}{4}$ ,  $\frac{5}{4}$  and any odd number of quarter-wavelength sections. In addition, everything that was said about half-wavelength lines also applies to full-wavelength,  $1\frac{1}{2}$  wavelengths etc. lines. Thus, it is necessary to do a little preliminary calculation to estimate in what general frequency range the line under test will act as a quarter-wavelength line, or what have you. If the physical length of a section of line is not known, a link can be hooked across one end, the other left open, and a series of checks made to check the various odd-quarter-wave resonances. From these readings the fundamental resonance can be found.

For example, suppose we had a roll of RG-8/U (52 ohm), and wanted to determine its length (Fig. 6). Coupling the grid dipper into a short-circuit on one end (better use an ohm-meter to see if the other end is open circuited!) we might find dips at 22.9, 16.3 and 9.3 Mc. Looking for a common denominator in this series we note that 9.3/3 equals 3.1 Mc. and 22.9/7 or 3.25 Mc. dip would be located at 3.25 Mc. also, if we had looked there. So the line is effectively quarter-wavelength long at 3.25 Mc, or 92 metres. Electrically, it would be a full wavelength at 23 metres. Allowing 66% for the velocity of propagation, the line is then  $23 \times 0.66$  or 15.2 metres physical length (800 inches). This example also serves to illustrate the numerous modes of resonance that may be encountered when using a non-terminated length of transmission line. Little wonder that they sometimes lead to confusing results in antenna measurements!

Obviously, all these remarks on transmission lines apply only to sections of lines which are actually open or short circuited—if a line is connected to a load such as an antenna, all bets are off! If it is desired to check a line when it is connected to a load on its far end, arrange to short-circuit the load end, and use capacitive coupling methods on the "sending" end. Be sure to use low-inductance leads to accomplish the short-circuiting, otherwise stray inductance in the shorting lead may upset the readings.

## COUPLED TUNED CIRCUITS

When tuned circuits are coupled together, the problem of determining the resonant frequency of an individual section of the combination is somewhat complicated. One approach is to separate the circuit under test physically and electrically from the other sections of the network. This is often easy to do in the constructional phases of a

job, but once the job is finished it may be impracticable. For example, in constructing a t.v.i. filter, one might take the trouble to pre-align the individual series-tuned and parallel-tuned traps which make up the filter to the desired rejection frequencies before combining the sections in the final arrangement. (Series-tuned traps, incidentally, can be short-circuited and treated as parallel-tuned circuits.) After assembly of the unit, it is extremely difficult to adjust to the proper trap resonances because in a typical filter all adjustments interact.

It must be admitted that the pre-alignment method described above is not fool-proof. Often the slight changes in tuning which may be involved in moving the components to their final location are too important to neglect. One of the best puzzles we've run into is how to line up the coils of a Wallman cascade r.f. amplifier for v.h.f. use. Essentially, this circuit has three parallel-tuned circuits, wired in series with each other. The capacitors of the parallel-tuned sections usually consist of tube capacitances only. It's well-nigh impossible to separate the components of this circuit for alignment

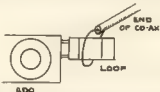


Fig. 6—This is how the g.d.o. is used to check the resonant frequency of a section of co-axial transmission line open-circuited on one end and short-circuited on the other. This line about nine feet long, resonated at 19 Mc. The dip will be quite sharp due to the relatively high Q of the line.

with a g.d.o., which simply means that we're still using the old cut-and-try design methods on this circuit! Neither is it practical to separate the primary and secondary windings of a typical r.f. or i.f. transformer, their tuning adjustments interact. The safest procedure in this case is to swamp out the Q of the unused winding by clipping a loading resistor (in the order of about 10,000 ohms) across it. This will also drop the Q of the coil under test but by judicious selection of the value of loading resistance it should be possible to retain reasonable sharpness of dip and still minimise the effects of tuning of the loaded coil.

We might refer back to the paragraph where we mentioned the method of checking for resonance effects, using a lead pencil or the like as a test probe. This method is also valuable whenever coupled tuned circuits are being checked. And don't forget that often it is not obvious that two circuits are coupled—for example, the tuned circuit in the signal input grid of a receiver mixer tube is often coupled (accidentally or deliberately) to the oscillator tuned circuit.

And the antenna feed line is usually coupled to a resonant antenna . . .

## ANTENNAE

Much has been said about the use of the grid dip oscillator to tune antennae. It is true that the natural resonant frequencies of a radiating wire

can be determined quite nicely with a grid dipper by treating it in much the same fashion as the transmission lines described above. But when we hear a Ham talking about the way he pre-tuned his close-spaced five-element Yagi array using only a grid dipper, we wonder just how the design was accomplished. Coupled antenna elements are as hard to deal with as coupled tuned circuits. Take an element out of an array and both the element and the array are de-tuned. Even if it were possible to check the individual element resonant points, how would we be sure just what significance this data might have in calculating the directional pattern or feed impedance of his beam antenna? In short, it is the opinion of these writers that grid dip oscillators may be used effectively to test single-element antennae (straight or folded dipoles, ground planes, mobile whips, etc.), but it is extremely difficult to obtain useful data on a beam array with the unaided g.d.o.

Before attempting to test an antenna with the g.d.o., stop to figure out the current and voltage distribution of the antenna. If it is a centre-fed straight dipole, on its fundamental frequency it will be current-fed, and the feed point should be shorted for the test. On the second harmonic frequency the same antenna will be voltage-fed, and to test the array on this band the feeders should be removed and the two sections of the antenna treated separately. A ground plane antenna or a resonant mobile whip is usually fed at a low-impedance point, so the feed point should be shorted. An end-fed Zepp antenna is a tough one to describe because the feed line is actually part of the radiating system. About the safest statement to make here is that precise tuning of the antenna itself or the feed line itself is not generally required in a system of this type. By tuning the feeder reactance at the sending end,


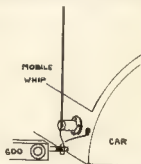


Fig. 7—This is a popular method of checking the resonant frequency of mobile antennae. Note that the feeder has been removed inside the base insulator and a low-inductance link coil substituted across the base.

with an antenna tuner, one can make the antenna take power, and if there's enough wire up in the air, it will radiate!

To couple the g.d.o. into an antenna. If coupling at a high voltage point use the methods of capacitive coupling described earlier. To couple at a current feed point, the feed line should be removed and a shorting jumper installed in its place. (The line must be removed, otherwise it will represent a resonant system loosely coupled into

# NOW!

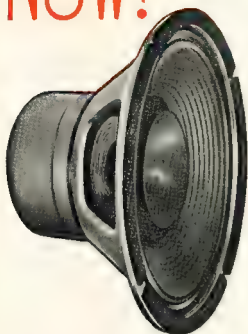

# A Full Range of ROLA

## WIDE RANGE

and

## HIGH FIDELITY LOUDSPEAKERS

These nine combinations of Rola loudspeakers have been evolved to give the high fidelity enthusiast a choice which will ensure the best possible performance from his equipment.

As shown diagrammatically at the right, they start with a single 8-inch low frequency unit and a high frequency tweeter combination intended for use where cabinet space is limited.

In successive stages, they progress from multiple 8-inch and 12-inch speaker combinations to the extended range coaxial models, culminating in the famous Hi Fi 12Ux, unquestionably the finest loudspeaker money can buy.

No matter what your Hi Fi requirements, there is a Rola loudspeaker or group of loudspeakers which will fully meet your requirements in both performance and cost . . . Rola Quality is Traditional.



### ROLA COMPANY (AUST.) PTY. LTD.



the antenna because of the fact that the short-circuiting jumper has a finite impedance and allows the feed line to absorb energy at the frequencies where it resonates.) Then the dipper can be coupled into the jumper to check the various modes of resonance of the antenna. In order to provide an easy means of coupling to the jumper, it may be formed into a one-turn link coil (Fig. 7). The length of the wire in the jumper should be very short compared to the length of the antenna, despite this coupling.

When coupling into a high-current point of an antenna element with no split at the feed point (this test would be merely of academic interest, because addition of a feeding system would undoubtedly de-tune the element), it may be possible to obtain sufficient coupling by placing the g.d.o. coil as close as possible to the antenna element. Since this system provides a combination of capacitive and inductive coupling it would be well to try reversing the position of the coil in the grid dipper for best coupling. Another stunt is that of clipping a test lead across a short length of the element at its centre and coupling into this clip lead.

## QUARTZ CRYSTALS

If a quartz crystal is connected into the coil terminals of any of the popular Colpitts-type g.d.o. circuits (Fig. 8) the g.d.o. becomes a Pierce-type crystal oscillator. The crystal will oscillate on its fundamental frequency in most cases. (Most crystals up to about 10 Mc. are fundamental cuts. Above this frequency they are likely to be third or fifth overtone units.)



Fig. 8.—Using the grid dip oscillator circuit as a crystal oscillator to check the activity of a fundamental frequency crystal. In this arrangement the dipper circuit becomes a Pierce oscillator. The tuning capacitor should be set at or near minimum capacitance.

The activity of the crystal will vary as the tuning capacitor of the g.d.o. is rotated; peak activity will occur at a point near minimum capacitance setting. The meter of the grid dipper gives an indication of relative activity of various crystals. While the crystal is oscillating in the dipper circuit its frequency can be checked on a calibrated receiver or frequency standard. It should be noted, however, that the operating frequency of a crystal depends greatly on the constants of the circuit in which it is used. In fact, it will be apparent that the tuning dial of the g.d.o. affects the frequency of the crystal signal considerably.

To check the activity of overtone crystals: Energy may be coupled into a crystal from the dipper coil by connecting across the crystal terminals (Fig. 9). At the frequency where the crystal looks like a series-resonant circuit it will produce a very sharp

dip, and the relative strength of overtone modes may be judged by the amount of the dip.<sup>3</sup>

## MEASUREMENT OF CAPACITANCE AND INDUCTANCE

The grid dip oscillator can be used to measure the resonant frequency of a capacitor and inductor. If we know either the inductance or the capacitance in a tuned circuit, knowing the frequency we can calculate the unknown element with a fair degree of accuracy, using the simple resonance formula. Most manufacturers of commercial grid dip oscillators provide figures on the actual inductance of the coils for their units, so the unused coils of a set may be used as inductance standards. It is not hard to build up a collection of accurate capacitance standards. A small variable capacitor calibrated directly in micro-micro-farads is also a handy grid dipper accessory. Certain commercial coils (such as the B. & W. Miniductor line) are sufficiently consistent in production that the manufacturer rates the coil in microhenries per inch. The scientifically-inclined Ham should make an effort to acquire suitable standards of inductance and capacitance for use in conjunction with his grid dipper; it's easy to measure effective r.f. reactances by this technique, though extremely difficult by most other systems available to the Ham.

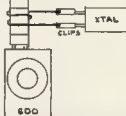


Fig. 9.—We can also use the dipper to check the activity of a crystal on its overtone mode. In the case illustrated, the grid dipper showed that the 8 Mc. crystal also displayed a strong series-resonant effect at 34 Mc.

## OTHER FUNCTIONS OF THE GRID DIP OSCILLATOR

Here we are, almost out of space, and we haven't mentioned the other important applications of the grid dip oscillator. This is probably due to the fact that the grid-dip function is so unique to this type of instrument that this particular application is not as widely understood as the others. After all, we've had absorption wavemeters, test oscillators, oscillating c.w. monitors, etc., in our Ham shacks for years, so we'll kinda skip over these points hurriedly.

## OSCILLATING DETECTOR

Using the grid dipper as a simple regenerative receiver gives us the most sensitive means of detecting the presence of weak unmodulated r.f. signals. It also provides information on the approximate stability and tone of the signal being received. About the only elaboration necessary here is to caution the reader that he should check the circuit of his particular grid dipper to see whether it is suitable for his type

of headphones. Some circuits require that a resistor be added in parallel with crystal headphones to provide a d.c. return. Other circuits might connect the phones in the B-plus lead, which would be bad for crystal phones. Also keep in mind that the headphones are connected to your head when you're probing around in the innards of a transmitter! Be careful!

## NON-OSCILLATING DETECTOR OR MONITOR

The dipper may be used as a tuned r.f. voltmeter to detect the presence and approximate magnitude of a signal applied to the dipper's tuned circuit. Every remark which was made relative to coupling power from the dipper into an external tuned circuit applies equally well to the situation in which it is desired to couple power from an external circuit into the grid dipper coil. Numerous applications of this feature will present themselves—the dipper may be used as a field-strength meter obtaining its signal from a small pickup antenna. It can be used to check the activity and frequency of oscillators in transmitters and receivers. It can be used to search for spurious output signals from a transmitter.

Though the typical grid dip oscillator is not sufficiently sensitive to detect signals capable of causing t.v.i. in the fringe area, it is a valuable tool in tracking down obvious causes of t.v.i. and during the preliminary cleaning-up processes.

Don't expect to have 100% success in "sniffing" out a micro-watt size signal in the output stages of a kilowatt rig, either. After all, the grid dipper has only one tuned circuit in it, and a single circuit does not provide enough selectivity to permit it to read a very weak signal in the presence of a very strong one even though the frequencies may be quite widely separated. If, in searching for a meter reading on a harmonic frequency of the big rig, you notice an up-scale reading on the dipper meter which seems to be relatively unaffected by tuning, it's probably normal, and due to overloading by the main output signal. This effect may mask the weak signal you're looking for. In spite of this tendency, however, it's surprising how well the dipper shows up spurious off-band signals.

Another point to watch out for in using the dipper as a field strength meter—make certain that the signal shown on the meter is the one you want to read. If the dipper is close to the transmitter it may be receiving most of its input signal via the power lines, or by radiation from the output circuits of the transmitter, rather than from the antenna system. For similar reasons, we have had little luck in attempting to use the dipper to check for standing waves on open-wire antenna transmission lines. It is also extremely difficult to arrange pure inductive coupling (or pure capacitive coupling) to the transmission line; therefore the standing wave pattern measured is likely to be a combination of the r.f. voltage standing wave pattern and current standing wave pattern—not much use for accurate work.

(Continued on Page 46)

<sup>3</sup> Simms, "Checking Crystals for Overtone Activity," "QST," Sept. 1951.

# IAN NICHOLS, VK7ZZ



THOSE Amateurs frequenting the c.w. portion of the 7 Mc. band recently have probably heard VK7ZZ, Ian Nichols, 9 Cressy Street, New Town, Tasmania. Ian obtained his A.O.C.P. just in time for the Remembrance Day Contest and wasted no time in getting on the air. Nothing remarkable in that perhaps, except that he is totally blind.

Blinded in an accident at the age of six, he attended High School and University where he obtained his B.A. and LL.B. degrees. Although he has been interested in Radio for a number of years, these studies, and later family responsibilities (he has four children) left no time for swotting for his Ham ticket. When the time came Braille copies of the Admiralty Handbook and the A.R.R.L. Handbook were obtained, and early in August an oral examination, conducted by the P.M.G. Department, was successfully passed. The Morse test was taken down in Braille and typed from that by Ian himself. He is now employed in the accounts section and in legal work for the Electrolytic Zinc Co.

For the present he is limited to an input of 10 watts crystal controlled, his transmitter to be built, installed and maintained by sighted Amateurs for

which VK7BJ, VK7KA and VK7OM have made themselves responsible. The transmitter when completed will have provision for four crystal frequencies in the 7, 14 and 21 Mc. bands with an aural tune-up device. The modulator to come later will be built by Ian himself. A special Avo meter for use by the blind is a recent acquisition.

The photograph shows VK7Z operating in the R.D. Contest while his eight-year-old son, Robert, looks on. The receiver is a SX16 and on top of this is the transmitter, then being used, a portable/mobile 8 watt rig loaned by VK7CH.

## BINDING "AMATEUR RADIO"

In response to many inquiries we are pleased to announce that we have made arrangements whereby members may have their year's file of "Amateur Radio" inexpensively bound into one volume. To avail yourself of this service, you should send, or deliver, your file of magazines, together with a slip plainly marked with your name and full address (block letters), to the office of the "Richmond Chronicle," Shakespeare Street, Richmond, E.I., Victoria.

The total cost to you will be 7/6, including return postage to anywhere in

Block by courtesy of Robert "Mercury"

Australia, and this amount should be remitted when forwarding your magazines.

Please note that magazines should be addressed as shown above, and not taken, or sent, to the Institute rooms or to the monthly meetings

## BOOK REVIEW

### BASIC MATHEMATICS FOR RADIO AND ELECTRONICS

By F. M. Colebrook

This book will take the student of our very diverse subject through from elementary algebra to differential and integral calculus and also includes special chapters on mathematics applied to radio and other special techniques.

We recommend it to the serious electronics student

Iliffe & Sons, London are the publishers. Our copy from Technical Book and Magazine Co., 295-299 Swanston Street, Melbourne, C.I. Price 29/- plus postage 1/-.

# ORYX

(LOW VOLTAGE)

## MINIATURE SOLDERING INSTRUMENT

### PROTECT YOUR TRANSISTORS WITH ORYX

There is a danger of damage when soldering to transistor leads, due to A.C. leakage currents. The use of a low-voltage transformer supply, with earthed secondary is therefore recommended. Take care also that too much heat is not applied to flying leads. The ORYX iron, and a heat-sink such as heavy pliers gripping the lead between the contact point and the transistor, will ensure protection.

*A must  
for  
Transistors*

(actual size)

- Fast heating element, ready for operation in less than one minute.
- Exclusive design features resulting in universal acceptance of ORYX as the standard miniature soldering instrument.
- The ORYX long life element will outlast several bits which are of tight push-on fit.

Bit Dia.:	Volts	Watts	Nett Weight	Length	Recommended Use
Model 6 1/16" (Fixed)	6	6	0.25 oz.	6"	Electrical measuring instrument fine assemblies, hairsprings, R.F. pick-up and speech coils, hearing aid sub-assemblies, etc.
Model 6a 3/32" (Push-on)	6	6	0.25 oz.	6"	As for Model 6 (for extremely delicate work only).
Model 9 5/32" (Push-on)	6, 12, 24-27½	8.3	0.25 oz.	6"	Hearing Aids, Radio and TV Sub-assemblies, Coils, Electronic Instruments, Model Construction, Electro-Medical, etc.
Model 12 3/16" (Push-on)	6, 12, 24-27½	12	0.5 oz.	6.25"	Radio, Television, and Telecommunications assemblies.
Model 18 3/16" (Push-on)	6	18	0.75 oz.	7½"	For heavier work, heat capacity equivalent to that of most 80 watt soldering irons.

Australian Distributors:

## MANUFACTURERS SPECIAL PRODUCTS PTY. LTD.

47 YORK STREET, SYDNEY

MELBOURNE: Amalgamated Wireless (Australasia) Ltd. ADELAIDE: Newton McLaren Ltd.

PERTH: Nicholsons Ltd., Carlisle & Co. Ltd. HOBART: Noyes Bros. Ltd. BRISBANE: Chandlers Ltd.

MSF3.5B



# Rules: 1958 "CQ" World-Wide DX Contest

## i.—Contest Period

Phone section—0200 GMT, October 25 to 0200 GMT, October 27.

C.w. Section—0200 GMT, November 29 to 0200 GMT December 1.

## ii.—Bands

The contest activity will be in the 1.8, 3.5, 7, 14, 21, 27, and 28 Mc Amateur bands.

## iii.—Type of Competition

1. Phone Section: (a) Single Operator, (b) Multi-operator.

2. C.w. Section: (a) Single Operator, (b) Multi-operator, (c) Novice Operator

3. Inter-club.

## iv.—Equipment

There is no limit to the number of transmitters and receivers allowed, and competitors may use the maximum power permitted under the terms of their license.

## v.—Serial Numbers

Phone stations will exchange serial numbers consisting of four numerals, the first two being the RS report, and the last two being their own Zone number. C.w. stations will exchange serial numbers consisting of five numerals, the first three being the RST report, and the last two being their own Zone number.

Stations in zones 1 through 9 will prefix their Zone number with zero (01 and etc.).

## vi.—Points

Contacts between stations on different continents will count 3 points. Contacts between stations in the same continent, but not in the same country will count 1 point.

Contacts between stations in the same country will be permitted for the purpose of obtaining a Zone and/or country multiplier, but no QSO points are credited. More than one contact between stations on each band will not be permitted.

## vii.—Multiplier

Two types of multipliers will be used.

(a) A multiplier of 1 for each Zone contacted on each band.

(b) A multiplier of 1 for each Country worked on each band.

## viii.—Scoring

1. The score for each Single Band is the sum of the Zone and Country multiplier for that band, multiplied by the total contact points on that band.

2. The total All Band score is the sum of the Zone and Country multipliers of all bands, multiplied by the sum of the contact points on all bands.

3. Everyone who sends in a log for a single band is eligible for a Single Band award only. If a log is submitted for more than one band, indicate which band is to be judged, otherwise it will be judged as an All Band entry.

4. Those who submit a log for two or more bands will be judged for the All Band award.

5. A station is not eligible for more than one award.

6. Single operator contestants must show a minimum of 12 hours of operating time to be eligible for an award. If a contestant operates all bands and wishes to be judged for a specific single band, he must show a minimum of 12 hours on that band.

7. Multi-operator stations must show a minimum of 24 hours of operating time to be eligible for an award.

## ix.—Zones and Countries

To check your own Zone number and country for scoring purposes, refer to the A.R.R.L. or "CQ" list as well as the W.A.Z. map. The continental boundaries used for W.A.C. will be recognized. Should any question arise as to the positive location of a station, the official definition will be final.

## x.—Awards

Certificates will be awarded in each sections as follows:

1. To the highest scoring station on each Single Band in the following areas: (a) Each call area of the U.S.A.; (b) Each call area of Australia and Canada; (c) All other countries.

2. To the station having the highest All Band score (more than one band) in the following areas: (a) Each call area of the U.S.A.; (b) Each call area of Australia and Canada; (c) All other countries.

## xi.—Special Awards

1. A cup will be awarded to the highest scoring Single Operator, All Band, Phone Station in the world. (Donated by W2SKE.)

2. A cup will be awarded to the highest scoring Single Operator, All Band, C.w. Station in the world. (Donated by W2IOP.)

3. A cup will be awarded to the highest scoring Multi-operator, All Band, Phone Station in the world. (Donated by K2AAA.)

4. A cup will be awarded to the highest scoring Multi-operator, All Band, C.w. Station in the world. (Donated by K2GL.)

5. A plaque will be awarded to the affiliated DX Club submitting the highest aggregate score of the scores submitted by its members. (Donated by "CQ".)

6. At the request of the donors, previous winners are not eligible for the 1958 awards. In other words the cups cannot be won more than once by the same station. This, however, does not apply to the plaque award.

7. Also such special or additional awards as the Committee shall choose to make. In countries or sections where the returns justify, second and even third place certificates may be awarded.

## xii.—Operating Suggestions

1. Foreign Amateurs, remember, scores are based on the greatest number of Countries and Zones as well as stations worked. Therefore do not concentrate on working only U.S. stations. This is a world-wide competition.

2. DX Stations; it is recommended that you give the call of the station you are working at the end of each transmission. This will prevent confusion.

3. Overseas phone operators; it is strongly recommended that you indicate which portion of the phone band, American or foreign, you intend to cover.

4. C.w. stations; calling on or off the frequency of the DX station, must be left up to the individual operator. This is generally governed by the technique of operators at the DX station.

## xiii.—Log Instructions

1. In keeping log, fill in Zone number and Country **only first time** it is contacted on each band.

2. Use a separate sheet for each band and a final tally sheet or report form.

3. Keep all times in GMT.

4. All contestants are expected to compute their scores. Logs should be checked for contact duplications and proper point credit before they are submitted.

5. Make sure name and address is clearly noted on each log. Print or type.

6. Each contestant must sign a pledge that all rules and regulations have been observed.

7. If official log forms are not available, it is hoped that a duplicate form will be used. The size is 8½" x 11" with 52 contacts to the page.

8. Copies of the Zone and Country list and log report forms are available from "CQ", address listed below. Send a self addressed stamped envelope, or in the case of overseas stations, IRC coupons. Make sure to include sufficient postage, state how many sheets are needed and allow sufficient time for mailing.

## xiv.—Rule Changes

The minimum operating time has been increased to 12 hours for single operators and 24 hours for multi-operator stations. This is a contest, not a leisurely week-end at your hobby.

The Committee is also going to be more critical regarding the observations of the rules and the keeping and scoring of your logs.

## xv.—Deadline

All logs must be postmarked no later than December 1, 1958, for the Phone Section, and January 15, 1959, for the C.w. Section.

Send all logs directly to: "CQ Magazine," 300 West 43rd St., New York 36, N.Y. Attn: Contest Committee.

— . . . —

## SPlicing 300 OHM RIBBON

Cut the ribbon so that a tab of insulation is left after the conductors are bared for soldering. Overlap the tabs, twist the conductors together and secure the tabs by an adhesive or by bonding with a hot soldering iron.

—H. Fackbender, W2BPS, "QST" Jan. '58.



# Obtain Your New and Disposals Equipment from..

# HAM RADIO SUPPLIES

## 5A MELVILLE STREET, HAWTHORN, VICTORIA

Philips No. 4 Receivers, 1.2 Mc. to 20 Mc. Complete with valves, A.C. and 6v. operation. As they come £10 each  
 2" Coil Formers, Plastic, with Tuning Slug . . . . 1/- each  
 2" Coil Formers, Plastic . . . . . 6d. each  
 Two-gang Split-Stator Condenser, 8 to 25 pF. per sect. 30/-  
 Three-Gang Condensers, AR8 High Frequency Type 15/-  
 Four-Gang Condensers, approx. 150 pF. per section 15/-  
 Midget Ceramic Trimmers, 3 to 55 pF. 1/-  
 AT21 Transmitters. Packed in case New condition, £12/10/0  
 108 Mk. III Portable Transceivers. Complete with Valves, Headphones, Mike. Freq. range: 7-9 Mc. Bargain £5

No. 19 Transceiver, complete with valves and genemotor. No Cables £7/10/0  
 A.W.A. Transmitters, Mobile, freq. 33 Mc. Contains four type 6V6s, one 807 final. 6v. vibrator supply Modulated. £7/10/0  
 A.W.A. Battery operated Mod-Oscillator, 150 Kc. to 30 Mc. To Clear £7/10/0  
 A.W.A. B.F.O. Type 4077. 10 cycles to 13 Kc. A.C. operated. Condition as new £25  
 A.W.A. Valve Voltmeter, 1.5v. to 150v. A.C. operated. £15

### ALL Q-PLUS T.V. CONSTRUCTORS PARTS READILY AVAILABLE


### VALVES, CRYSTALS, AND OTHER EQUIPMENT—SEE THE INSIDE FRONT COVER OF THIS ISSUE

3BZ Transmitter, complete with valves, 12v. operation £15  
 AT5 Transmitters, as new, with valves & dust covers, £8/17/6  
 BC455 and BC454 Command Receivers, air tested, with valves, 6 to 9.1 Mc. £5; 3 to 6 Mc., £6.  
 AT5/AR5 Aerial Coupling Units, as new . . . . . £2  
 AR8 Communications Receivers, as new, with valves and dust covers £20  
 AR5/AT5 Cables, 12 ft. long . . . . . 10/0  
 SCR522 Receivers, less valves . . . . . £5

I.F.F. L.F. Coils in Can. Type No. 358-1696, as used in the Transistor H.F. Portable in this issue 8/-  
 Genemotors, Windcharger, 15v. 3.8 amp. input, output 405v. 0.095 amp. When 12v. input applied, 250v. output. £3/5/0  
 Three inch Speakers, well known make, new in carton, less transformer £1 each  
 English Filter Chokes, small type, 40 Ma., 100 ohm resist. 3/6  
 Shielded Wire, single, American 1/6 yard  
 Power Transformer, small, 255v. aside 60 Ma., 6.3v. 2.5 amp.; 200-225-250v. primary. Brand new 25/-  
 Miniature Variable Condensers, screwdriver adjustment, silver plated. Sizes available: 25 pF., 55 pF., 80 pF., 105 pF., or 110 pF. New condition. 7/6 each or Three for £1.
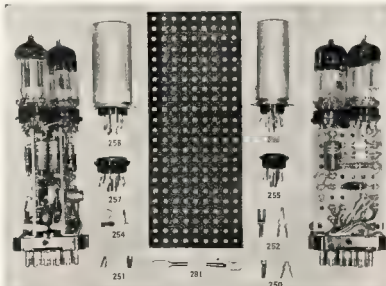
## REDUCE THE SIZE AND COST OF YOUR NEW EQUIPMENT

TYPICAL  
UNITS  
USING  
ZEPHYR  
MATRIX  
SYSTEM



Leaflets and  
Price List available  
from all  
leading Wholesalers.



Enquiries invited  
from  
Manufacturers.

ZEPHYR PRODUCTS PTY. LTD.

58 HIGH STREET, GLEN IRIS, S.E.6, VIC.  
Phone: BL 1300

## THE IMPROVED DIPPER

(Continued from Page 14)

end of the coil with the Dipper capacitor set at maximum.

Then, for point to point calibration, the absorption meter is set at the desired frequency and the Dipper capacitor rotated until dip is indicated. The scale should be marked accordingly, using a hard sharp pencil and the special calibrating dial. The marker points may be inked after calibration. As mentioned previously, the grid current will vary gradually over each range; however, resonance is indicated only at the point where a pronounced dip occurs.

When calibrating with a receiver it is merely necessary to turn on the receiver beat oscillator and tune in the Dipper signal. Care must be taken so as not to become confused with harmonics or receiver images. Calibration points are marked according to the Dipper beat heard on the receiver, instead of observing the grid meter dip.

The instrument may be checked against itself in the following manner: Set the Dipper at 1.75 Mc. and tune in the second harmonic at 3.5 Mc. Then, with the receiver left tuned at this point, set the Dipper at 3.5 Mc. as indicated on its scale. The signal should then be heard on the receiver without any further tuning. This should be repeated at 7 Mc., etc., right down the line. If WWV can not be heard at the higher frequencies, the instrument may be set at a lower WWV frequency and then checked on the harmonics in the above manner.

If an absorption meter or receiver is not available for use at the highest frequencies, Lecher wires may be set up and the same procedure followed as with the absorption meter. For general calibration a signal generator may be employed by listening for the generator beat on a pair of phones plugged into the Dipper. With the lowest frequency coil there is about a 2% error with the phones plugged in due to the addition of the 50,000 ohm resistor in the grid return. On the other ranges, the error is negligible and may be discounted.

It must be remembered that the accuracy of the Dipper cannot be any greater than that of the calibration source and the care exercised during calibration. When employing the Dipper, greatest accuracy is realised when the probe coil is placed as far away as possible from other metal objects and when the coupling to the circuit under test is as small as permissible while obtaining an indication of dip.

[As a 100 pF. miniature split-stator variable condenser is rather hard to obtain, some improvisation may be necessary. Ham Radio Supplies have available 105 pF. miniature variable condensers (screwdriver adjustment). By making a "U" bracket and mounting the two condensers inside the bracket, back to back, the two rear rotor shafts can be joined by a sleeve and solder sweated. Then a shaft should be made to slip over the collar on the front of one of the condensers to tune the pair. Make the connection to the collar a tight fit. Of course the usual Amateur ingenuity will find many other means of connecting two of these condensers to form a split-stator condenser.—Editor "A.R."]

## AMATEUR TELEVISION

(Continued from Page 25)

Under high speed sweep, at low repetition rates, the trace is of course very dim, as the beam is blanked off most of the time, the active time in the example above is only one in a thousand.

### Triggered Sweep

This has to be calibrated in time (duration) and the sweep length adjusted to 4". Assuming all duration capacitors (S8A) have been checked on a bridge before fitting, set duration to 100  $\mu$ sec. position. Inject a c.w. signal from a signal generator at about 50 Kc. Adjust sync. gain and trigger threshold controls as necessary for a stable display. Either positive or negative trigger will do. Adjust the signal generator frequency to display an exact integral number of cycles—say 5. The frequency then should be 50 Kc. If not, adjust the two triggered sweep charging resistors shown as 500K and 100K in series, until 50 c.p.s. gives exactly 5 cycles. When correct on one range, it will be correct on all others.

To adjust trace length to 4", adjust the values of the capacitors on S8B to give the correct length, the values shown being nominal. The higher the value, the shorter the trace.

### Trigger Delay

This assumes the three capacitors have been checked to give a 1:50:100 ratio, absolute values being nominal. Inject a 15625 c.p.s. signal (your line pulses) and display on the 400  $\mu$ sec. duration setting. Use positive trigger on positive pulses, and the reverse, although triggering will occur in the reverse sense, the leading edges are usually sharper. Switch delay to X1. Using "MICROSECOND" dial, shift second pulse to the position of the first. This point on the dial is 64 on X1, and 6.4 on X10. Shift the third pulse to the position of the first. This is 132 on the X1 scale, and 13.2 on X10. With these datum points, use a signal of 100 Kc. to provide 10  $\mu$ sec. points

right round the dial rotation, by shifting one complete cycle left for every 10  $\mu$ secs.

This c.r.o. is an ambitious project for someone new to oscillograph construction, but for the experimenter moving into Amateur t.v., it is no more tricky than anything described before. It is a versatile instrument and will become your right hand.

Next month I will conclude this series with a description of a television transmitter.

## CORRESPONDENCE

### YOUR HELP PLEASE

Editor "A.R.", Dear Sir,

I am an s.w.l. member of the N.Z.-A.R.T. (N.Z. Amateur Radio Transmitter) as well as being an active commercial bands DXer.

The reason for writing is that I will be in Australia for several weeks (approx. six) at the end of the year. At least, will be arriving in Sydney on New Year's Eve.

I am anxious to meet as many s.w.l.'s as possible, and any Hams, too, to say hello. I am trying to plan the tour well before I leave ZL. I intend to spend a week in each State.

—Basil Coombe, P.O. Box 377, Palmerston Nth., N.Z.

## GOING S.S.B.?

### PRECISION AUDIO-PHASE SHIFT NETWORKS

now available.

Assembled and tested. Interchangeable with B. & W. 2Q4.

£2/10/0 plus reg. postage.

D. POLLARD

17 Chiswell Av., Canterbury, N.S.W.

## IRONCORE

*In its Initial Appearance offers Congratulations to*

## AMATEUR RADIO

*on its*

**TWENTY-FIFTH ANNIVERSARY**



**IRONCORE TRANSFORMERS PTY. LTD.**

HIGSON LANE, MELBOURNE, C.I

Phone: MF 4771

## TRANSISTOR H.F. RECEIVER

(Continued from Page 8)

(see coil table). The antenna is tapped at 13 turns through a 75 pF. capacitor. Tracking capacity of 150 pF. was required.

The next switch position (position 2) accommodates the 12 Mc. to 8.4 Mc. coil. On this band the antenna is tapped to the primary at 4 turns through a 50 pF. capacitor. The tracking capacity required was 470 pF. The coil details are to be found in the table.

By using an oscillator coil tunable from 7.25 Mc. to 6 Mc., r.f. injection of harmonics in the range 14.5 Mc. to 12 Mc., it is possible to tune the 14 Mc. band with quite good results.

Both mixer and oscillator coils use 3-30 pF. trimmers for correct frequency adjustment.

### HINTS

Current drain from a 6 volt supply without signal is 14 mA. On very strong signals the current rises to 45 mA.

It is advisable to use transistor sockets, as it makes it easy to change transistors around. If the transistors are soldered into place, there is the danger of them being damaged by excessive heat.

The thermistor R32 is used to protect the OC72 class B audio transistors. Don't leave it out. The potentiometer R31 is adjusted until the OC72s draw 1 mA. each.

The receiver is very quiet in operation. Without an antenna, the set sounds dead, there being no hiss level. Once the antenna is connected, the set becomes quite lively.

The complete set measures 12" long, 4 1/2" wide and 7" high.

One final point. Be sure to by-pass the battery supply, both in the receiver and test set. About 2  $\mu$ F. should prove satisfactory.

The author would be pleased to hear from anybody who may construct this receiver, or answer any queries.

[2N112 and 2N138 Transistors are no longer current types. They are replaced by the 2N485 and 2N632 respectively. See advert on page 18 this issue.—Ed.]

## THE TA2 SPECIAL

(Continued from Page 17)

Before closing, just a few words on the audio requirements are in order. The use of a conventional speech clipping followed by an audio filter (approximately 3000 cycles cut-off) is advised for best results. However, this is not a "must" requirement. Finding an audio transformer with a ratio between 1:2 and 1:3 having a split secondary is not an easy job. The compromise suggested by George Grammer, using two transformers with the primaries in parallel and the secondaries in series works well in my rig. Shunt feed, using two filter chokes approximately 10 to 20 henries at 10 Ma. or more should do as another possibility. Tubes requiring low screen grid voltage are easy to drive so one or two watts of audio should be enough for 6BQ6s. My audio set-up was designed for 807s which required a relatively high screen grid voltage and provided much more audio voltage than is required by 6146s. Three to five watts should be ample for these tubes.

My hope is that this will get the ball rolling for d.s.b.s.c. and d.s.b.c. If so, maybe we will hear more talk and less carrier on the DX bands of the future.

Last, I would like to give credit to K7BG8 (my XYL), though still not convinced that suppressed carrier phone is here to stay, she has been very tolerant of my disruptive influence around the Ham shack.

### REFERENCES

- 1a Costas, J. P., "Single Sideband: Is It Really Better Than Amplitude Modulation?", "CQ" Jan. 1957, "A.R." Jul. 1957.
- 1b Webb, J. K., "A Synchronous Detection Adaptor for Communications Receivers", "CQ" Jun. 1957.
- 1c Harris, H. S., "DSB Considerations and Data", "CQ" Oct. 1957.
- 1d Webb, J. K., "Modulating the DSB Transmitter", "CQ" Mar. 1957.
- 1e Nelsor, Jack, "A 100 Watt DSB Mobile Transmitter", "CQ" Mar. 1957, "A.R." Apr. 1957.
- 1f Stoner, D. L., "Double Sideband with the Heath DX-100", "CQ" Apr. 1957.
- 1g Jonas, F. C., "Low Cost DSB-AM Amplifiers", "CQ" Nov. 1957.
- 2 Grammer, George, "DSBRC" Part I. and II., "QST" May and Jun. 1951.

## G.D.O. APPLICATIONS

(Continued from Page 45)

If you're trying to measure percentage change of voltage or field strength, it's best to run the sensitivity control in the fully "on" position due to meter linearity.

### SIGNAL GENERATOR

There are plenty of times when it's handy to have a wide-range medium-powered signal source in the Ham shack. You can use it for numerous receiver tests. The signal can be substituted for the normal oscillator signal of a superheterodyne receiver if it is suspected that the oscillator is out of order. Why build an oscillator for that breadboard receiver you're experimenting on, if you have a dipper on hand already? You can put the dipper on a local tv channel and proceed to go out and mow the front lawn just to prove to the neighbors that your transmitter isn't the only device that can produce t.v.i. Or you can inject the relatively pure output signal of the grid dipper into a t.v. set to demonstrate that sometimes a clean signal on an authorized Ham frequency can cause t.v.i. You can also use the oscillator of the dipper to drive antenna measuring equipment, such as the "Antennescoper".

Some models of the grid dip oscillator provide means for modulating the signal emitted by the device. Others are arranged so that a modulating signal from an external source may be inserted into the headphone jack. Better check the design of your particular dipper, before attempting to modulate in this way.

### ABSORPTION WAVEMETER

One of the earliest devices for measuring wavelength of a signal was the absorption wavemeter. The dipper, whether it is plugged into the power line or not, may be used as a simple L/C tuned circuit to suck power out of any circuit carrying r.f. current. One precaution should be observed while using the dipper in this fashion around high powered (or even moderately-powered) transmitter stages. Do not couple enough power into the device to flash across the insulation of the internal wiring. The old-fashioned absorption wavemeters had little inside the box except the tuning condenser and it didn't particularly matter if that flashed over. The dipper, however, has a tube socket, several small coupling capacitors (which may also be used to insulate the unit from the power line) and a tube, all of which may be damaged by application of excessive voltages, so take it easy!

It would not be possible to include all the potential applications of such a versatile device as grid dip oscillator in an article of this type. For further information refer to the articles mentioned in the footnotes, and study the instruction booklets available from manufacturers of these instruments.

### APPRECIATION EXTENDED

The publishers of "Amateur Radio" wish to express their appreciation to J. H. Magrath & Co. Pty. Ltd. for their generous gesture in vacating the front cover so that a special design to commemorate the 25th Anniversary of publication of "Amateur Radio" could be printed thereon.

## Duralumin Aluminium Alloy Tubing for Radio Aerials

★ LIGHT ★ STRONG ★ NON-CORROSIVE

STOCKS NOW AVAILABLE FOR IMMEDIATE DELIVERY

ALL DIAMETERS—1/4" TO 3"

RECOMMENDED FOR TELEVISION AND BEAM AERIALS

Price List on Request

STOCKISTS OF SHEETS—ALL SIZES AND GAUGES

## GUNNERSSEN ALLEN METALS

PTY. LTD.

88-92 YARRA BANK ROAD, SOUTH MELBOURNE

Phone: MX 4624 (9 lines)

Telegrams: "Metals," Melbourne.

# I.T.U. FUND DONATIONS

### PREDICTION CHART, SEPT. '58

Mo. E. AUSTRALIA - W. EUROPE S. M.																
45	0	2	4	6	8	10	12	14	16	18	20	22	24	45		
28														28		
21														21		
14														14		
7														7		
E. AUSTRALIA - W. EUROPE L.R.																
45	0	2	4	6	8	10	12	14	16	18	20	22	24	45		
28														28		
21														21		
14														14		
7														7		
H. AUSTRALIA - MEDITERRANEAN																
45	0	2	4	6	8	10	12	14	16	18	20	22	24	45		
28														28		
21														21		
14														14		
7														7		
E. AUSTRALIA - N.W. U.S.A.																
45	0	2	4	6	8	10	12	14	16	18	20	22	24	45		
28														28		
21														21		
14														14		
7														7		
E. AUSTRALIA - N.E. U.S.A. S.E.																
45	0	2	4	6	8	10	12	14	16	18	20	22	24	45		
28														28		
21														21		
14														14		
7														7		
E. AUSTRALIA - N.E. U.S.A. L.R.																
45	0	2	4	6	8	10	12	14	16	18	20	22	24	45		
28														28		
21														21		
14														14		
7														7		
E. AUSTRALIA - CENTRAL AMERICA																
45	0	2	4	6	8	10	12	14	16	18	20	22	24	45		
28														28		
21														21		
14														14		
7														7		
E. AUSTRALIA - S. AFRICA																
45	0	2	4	6	8	10	12	14	16	18	20	22	24	45		
28														28		
21														21		
14														14		
7														7		
E. AUSTRALIA - FAR EAST																
45	0	2	4	6	8	10	12	14	16	18	20	22	24	45		
28														28		
21														21		
14														14		
7														7		
W. AUSTRALIA - N.W. U.S.A.																
45	0	2	4	6	8	10	12	14	16	18	20	22	24	45		
28														28		
21														21		
14														14		
7														7		
W. AUSTRALIA - S. AFRICA																
45	0	2	4	6	8	10	12	14	16	18	20	22	24	45		
28														28		
21														21		
14														14		
7														7		
W. AUSTRALIA - FAR EAST																
45	0	2	4	6	8	10	12	14	16	18	20	22	24	45		
28														28		
21														21		
14														14		
7														7		

word, VK3US, R. M. Churchward, VK3VL; Dr. E. Marks, VK3VM, L. F. Shutterling, VK4CK, W. J. Robertson, VK4WL; F. B. Bond, VK4ZM, S. J. Smith, VK5BJ, Senator G. Heenan, Vic. J. N. Paris, S.A.

### £10/0

R.A.A.P. Radio Club, VK1AF, R. Isaac, VK2ABO, C. Orr, VK2ACO; W. Shakespear, VK2AG; J. Meyer, VK2AGY; C. Fletcher, VK2ASP, A. Isaac, VK2AVI, E. Crouch, VK2EC, A. Phibbs, VK2EU; R. Black, VK2EA, R. Adams, VK2YR, P. Pospol, VK2ZBP, J. Mackie, VK2ZIM, F. Caton, VK2ABQ; J. Young, VK2OY, E. Hocking, VK2AE; A. Fox, VK2KP, A. Pletz, VK2QE, P. Sara, VK2OV, L. West, VK2SE; J. Mulcahy, VK2E, F. Ende, VK2AE, A. Magennis, VK2AFE, L. Lee, VK2AGL, C. Jarlett, VK2AK, N. Young, VK2OY, F. Curran, VK2CP, C. Peters, VK2SV, Maj. C. Allen, VK2ALC, D. Kerr, N.S.W., M. O'Brien, N.S.W.; A. Sullivan, N.S.W.

C. Edmonds, VK3AE, D. Laws, VK3AM; G. Waad, VK3AUU, P. Gremser, VK3AYO, C. Donoghue, VK3JQ; L. Kermond, VK3DX, A. Buchanan, VK3JG; G. Gooby, VK3GV, B. Fayle, VK3W, W. Alder, VK3JE, K. Green, VK3KG, F. Bibby, VK3OL; V. Barnes, VK3OT; A. Cretcher, VK3SM, M. Dempsey, VK3WD; Mrs. A. Henry, VK3YL, K. Thompson, VK3ZBT, L. Ion, VK3AIO, M. Tulloch, VK3AKT; A. Puill, VK3EF, J. Keenes, VK3KE, I. Adams, VK3OA; W. Hehir, VK3RE; C. Golden, VK3TI, R. Bailey, VK3ZAO; R. Simpson, VK3ZES; J. Andersen, VK3ZFO; O. Fudge, VK3ZFP; W. Stevens, VK3ZG; H. Stevens, VK3JO; R. Stevens, VK3OD; K. Milburn, VK3W; K. Jans, VK3MG, R.A.A.P. Apprentices Radio Club, VK3APP; V. McKenna, VK3AVM; L. Seedsman, VK3IE, W. Jardine, VK3PR, W. Trefgar, VK3KT; J. Becher, Vic. J. Hayward, Vic. G. Orton, Vic. E. Treblecock, Vic. T. Millbourn, Vic. E. Fell, VK4EF; W. Bestman, VK4LN; J. Young, VK4JY; J. O'Rourke, VK4SO; R. Morris, VK4MT; H. Overend, VK4OH, R. Simmons, VK5GK; A. McRiche, VK5CE; H. Bowman, VK5FM; J. Brown, VK5G, E. Van Stanke, VK5KU; K. Metcalf, VK5ND; T. Davies, VK5TD; University of Adelaide Radio Club, VK5UJ; L. Mullins, VK5XM; T. Drake, VK5DL; R. McCarthy, VK5MC; K. Tauber, VK5SQ; D. Kelly, VK5DK, R. Richards, VK5DO; D. Scott, VK5DS; J. Watson, VK5AW; K. Ring, VK5KH, W. Belling, VK5KK; C. Othen, VK5ON, R. Scott, VK5RU; N. White, VK5ZAW; B. Warman, VK5ZBI; B. Bythe, VK5ZBL, M. Lane, VK5AO; K. Cahill, VK5KC; E. McGrath, VK5MO; R. O. Edmeades, S.A.; F. Fergie, S.A.

J. Hunt, VK6JD; R. Trew, VK6RP; L. Gooding, VK6ZAH, P. Zari, VK6ZB; G. Richardson, VK7GR (omitted from July list), T. Allen, VK7AL; T. Connor, VK7CT, L. Edgington, VK7LS; M. McGinniss, VK7MF; F. Fith, VK7FP; E. Nicholas, VK7RY; M. Sidebottom, VK7SK; R. Harrex, VK7ZAC; D. Thorpe, VK7ZAI; R. Milne, VK7ZAL; J. Milway, VK7ZAM; D. Taylor, VK8DT; W. Holland, VK8BW; M. Ewen, VK8CK; M. Lang, VK8ML; L. Howell, WIA-1903.

### Under £10/0

H. Fitzsimmons, VK3FI (10/0); E. King-Smith, VK3AKS (10/-); A. Wrenbeck, VK4YO (15/-).

### Amendments to Previous Lists

August list: Amend R. F. Gille, Qld., to read £13/0.

September list: Amend K. Nutt, VK4OD, to read K. Nutt, VK4KD.

The progressive total as at 31st August is £1,513/19/3.

### 1957 R.S.G.E. TELEPHONY CENTENT

### Poor Entry from Australasia

The first three placings of G Hams were: G3DO, 4140 points; G4ZU, 4060 points; and G2CDI, 3765 points.

The first three placings of the overseas entrants were: VQ4RF, 2120 points; ZD4BV, 1960 points; and OH5E, 1940 points.

Following are the entries from Australasia: ZL3RB, 1045 points, 18th position in overseas entries; and VK2AKV, 615 points, 29th.

Listed below are additional subscribers to the Fund to send a Region 3 Amateur delegate to the International Telecommunication Union Conference at Geneva in July 1959.

Amateurs throughout Australia will be pleased to learn that the Postmaster-General has accepted the representations of the Federal Executive of the W.I.A. and has agreed to the Amateur delegate being officially accredited as part of the Government delegation to the Conference.

Many Amateurs may have refrained from sending in their subscriptions as they were not sure of the status of our representative and perhaps thought the monies collected may have been wasted. The recognition of our delegate by the Postmaster-General will now dispel any false impressions that may have been created on this surmise.

Now that official recognition has been made, it behoves every Amateur who has so far not subscribed, to immediately send his donation to—

**Federal Secretary,  
Box 2611W, G.P.O.,  
Melbourne, C.I, Vic.**

Our target figure is £2,500—every effort must be made by Amateurs and by Divisions to assist in our endeavours to reach this figure. Your donations, large or small, are equally welcome.

The following is a list of contributions to 31st August, 1958:—

### £10/10/0

C. McC Hicks, VK2ADV.

### £10/0/0

Vic. Railways Institute Radio Club, VK3RI.

### £5/0/0

A. Fairhall, VK2KB; Moorabbin Radio Club, VK3ACP; Townsville Amateur Radio Club.

### £3/0/0

R. W. Johnston, VK1AUJ; J. F. Picketts, VK4FP.

### £2/15/0

S. Clark, VK3ASC (from sale of wire).

### £2/10/0

A Roudie, VK2JUJ.

### £2/0/0

L. T. Swain, VK3CS; V. Cahill, VK3VC; A. J. Kelsa, VK3WK; W. W. Jenvey, VK3ZO; A. Downward, VK3AHD; R. R. Anderson, VK3UR; L. G. Robertson, VK3WJ; D. H. Goldsworthy, VK3ZL; J. Wright, VK4AR, C. D. Tilbrook, VK3GL; R. E. Conrad, VK3TR; J. McAllister, N.S.W.

### £2/0/0

T. G. Hewitt, VK2LH, S. Fairbairn, VK3ZDF; R. J. Cayser, VK3ATC; H. F. Bremnerman, VK4HB, A. H. Morrisby, VKTMY; R. Sutherland, VK9BS.

### £1/10/0

J. M. Endacott, VK3EB, D. Beadell, VK8DB; N. Casey, VK3NT.

### £1/8/0

R. Grivas, VK3AQX.

### £1/5/0

R. W. Edwards, VK3RE; W. T. Boon, VK2ZAR, A. J. Brackeen, VK7BR.

### £1/1/0

P. Hargraves, VK4AOH, E. M. Simpson, VK2ES; F. M. Stean, VK2FZ, C. E. Rordwell, VK3IR, R. N. Sneddon, VK2WS; C. Gibson, VK3FO, E. Wardle, VK3OO, Mrs. G. Church-

1997, 1998, 1999, 2678, 26

I have an interesting article from the Ionospheric Prediction Service, regarding, for those who can remember it, the Geomagnetic storm which occurred on Feb. 11 of this year. This storm was reported as one of the worst in severely ever recorded, and no advance warning was available of the accompanying ionospheric disturbance. One thing has come out of it all, and that is steps have been taken to prevent getting caught like this again.

The DKPedit on by the VSI boys to the Nischar is looks like being off, according to VSIFF, due to the probable refusal of the Indian Govt to grant the necessary permission. At the time of writing, there is no news of the one planned by the VU boys.


ZSGIF/1 was operating from Swastika this morning, one week after he had left for a card binge and should go to his home QTH. If he thinks, as a result of this trip, it worth while, he will visit ZSS and ZSN next year.

ZDRI.N is a foney ZDASC is leaving the area and his rig will probably be taken over by ZDAP.

VE2LO is on from 84, Lsola using c.w. 1470. Kc

ing reports on his signal and guarantees a QSL. As you can see by his call letters, he is connected with the L.G.Y. programme. QSL may be sent direct or via the Bureau to Geophys. Obs. Collm., near Oschatz, Germany. D.D.R. As 28 Mc. will improve from now, he should be easily found.

[illegible]



## VACUUM MOUNTED CRYSTALS



for general communication frequencies in the range 3-14 Mc. Higher frequencies can be supplied.

### THE FOLLOWING FISHING-CRAFT FREQUENCIES ARE AVAILABLE IN FT243 HOLDERS, 6280, 4095, 4535, 2760, 2524.



### ALSO AMATEUR TYPE CRYSTALS—3.5 AND 7 Mc. BAND.



Commercial—from £3/15/6 each, plus 12½% Sales Tax.  
 Amateur—from £3 each, plus 12½% Sales Tax.  
 Reprints 2/10/-.

### CRYSTALS FOR TAXI AND BUSH FIRE SETS ALSO AVAILABLE.

We would be happy to advise and quote you as to the most suitable crystal for your particular application, either in the pressure or vacuum type holder.

New Zealand Representatives: Messrs. Carrel & Carrel, Box 2102, Auckland.

## BRIGHT STAR RADIO

46 Eastgate Street, Oakleigh, S.E.12, Vic.

Phone: UM 3387





**You'll make *DOUBLE* savings**



### SAVE ON SPACE

MICROCAP'S exclusive metallised paper construction results in a lightweight ultra-miniature space-saving capacitor, which can be fitted in a fraction of the space required for ordinary units of the same rating. Resultant overall savings in space mean worthwhile savings on cost.



### SAVE ON SERVICING

Outstanding "self-healing" feature enables MICROCAP to sustain accidental over-voltage. This results in long, stable life in miniature form, reducing servicing problems, greatly overcoming the bug-bears of "intermittent" and open or short circuits.

**Wide range covers requirements of modern design**

\*Registered Trade Mark



#### A.E.E. TYPE W99

Available in working voltages of 200, 400, 600 V. D.C. and 300 V. A.C. in values up to .04  $\mu$ f.

#### A.E.E. TYPE W48

Covers range .05  $\mu$ f to 2.0  $\mu$ f in working voltages of 200, 300 and 400 V. D.C.

M12.

Manufactured under licence from A. H. Hunt Capacitors Ltd., London by

# Australasian Engineering Equipment

476 LATROBE ST., MELBOURNE. FY 2638

CO. PTY. LTD.

N.S.W. Agents:—Wm. J. McLELLAN & Co. Pty. Ltd., 126 Sussex St., Sydney. BX1131



# NOTES

## FEDERAL

### BOY SCOUTS PAN PACIFIC JAMBOREE

This event will be held in Auckland, N.Z., from 10th January, 1958.  
The N.Z.A.R.T. intends to install and operate an Amateur Radio Station from the Jamboree during this period and has been granted the use of the special call sign ZL1PJP (Pan Pacific Jamboree).

Operation of this transmitter will be from 0900 to 2100 NZT (1000 to 0900 GMT) and will cover all bands from 30 metres to 2 metres.

A special QSL card will be used to acknowledge all contacts.

Those stations wishing to arrange exchds with ZL1PJP are requested to contact ZL1 Amateurs or write direct to Jack Freeman, ZL1VA, who will be particularly pleased to hear from Radio Amateurs who are Scouts or are connected with this Movement.

### AMATEURS HELP CHILDREN AWARD (A.H.C.B.)

The Austrian Radio Amateurs Club, in co-operation with the OEVSFV, have established the above award which has a two-fold purpose:

(a) To encourage Radio contact with Austrian Amateurs.

(b) To help the work of the S.O.S. Children's Villages which have been established to provide a solution to the world-wide problem of neglected and orphaned children.

and in order to give such children a real, normal and family-type home, and the security of a mother's love.

This award is open to all licensed Amateurs throughout the world and short wave listeners, and is issued in these classes:

(a) Class Three: Will be issued upon submission of 10 S.O.S. Kinderdorf QRL cards verifying 10 QSOs with Austrian Radio Amateurs.

acurs. (b) Class Two: 20 S.O.S. Kinderdorf QSLs. (c) Class One: 40 S.O.S. Kinderdorf QSLs.

Contacts on all bands, telephony or telegraphy, are eligible, but a QSL card from the station may be worked only once per band and type of contact.

Fees for issue of this award will go towards the expansion and upkeep of the S.O.S. Children's Villages and are as follows:

(a) Class Three: 10 L.R.C. (b) Class Two: 20 L.R.C. (c) Class One: 40 L.R.C. These fees may be paid in the currency of any country, cash, L.R.C., cheques or money orders.

### DEF MORE TRANSMISSION

These transmissions are operated by the R.N.Z.A.P. for the benefit of all world-bee movie operators, and those who wish to increase their proficiency in R.N.Z.A.P. have advised that the following is the current schedule:

Frequencies: 2238 and 2855 Kc., Monday to Friday inclusive, at the following times:

1820-1845	5 w.p.m.
1845-1900	10 "
1900-1915	15 "
1915-1930	20 "
1930-1945	25 "
1945-2000	30 "

The above transmissions should be of interest to all those requiring practice in slow and fast Morse.

### I.A.R.U. OFFICIAL COUNTRIES LIST

A proposal submitted by the W.I.A. regarding the establishment of an official I.A.R.U. Countries' List has been accepted.

As a result of the acceptance of this proposal, an official I.A.R.U. Countries' List is to be prepared by a committee consisting of the R.S.G.B., A.R.R.L. and the W.I.A.

### SPARE VALVES FOR INDIAN AMATEURS

The question of types was considered by F.E. and the conclusion was that any type of valve at all can be put to some use by a Ham.

Tubes should be in serviceable condition, and if the type number cannot be read, should be labelled. Tubes will be sent to the Amateur Radio Society of India for distribution by that body as it sees fit.

Further to the recent note on the above, valves may be forwarded to:-

VKSAG, 327 Wellington Street, Perth, by VKASAs who desire to do so.

VKSGK, D.C.A. Marine Base, Port Moresby, by VKSGKs who desire to do so.

by VKS As who desire to do so.

## CONTEST CALENDAR

Compiled by W.I.A. Fed. Contest Com.

### ★

#### VK-ZL DX CONTEST:

Dates: Phone—4th-8th Oct, 1958.  
C.W.—11th-12th Oct, 1958.  
Times: 24 hours from 1000 GMT, Sat., to 1000 hours Sun.  
Bands: All h.f. bands (including 11 mx).  
Rules: See issue, page 14.  
Legs: For VK-ZL Stations—To Contest Manager, ZL2GX, 60 Lytton Rd., Gisborne, N.Z., before 20th Dec, '58.

#### "CQ" WORLD-WIDE:

Dates: Phone—20th GMT, Oct 25, to 0900 GMT, Oct 27.  
C.W.—0900 GMT, Nov. 29, to 0900 GMT, Dec. 1.  
Bands: All h.f. bands (including 11 mx).  
Rules: See this issue (Note Rule 8, Secs. 4 and 7).

#### R.S.G.B. TELEPHONY CONTEST

Dates: Nov 23 and 24.  
Rules: Restricted.

Rules: Same as for 1957 except for scoring bonus for working 24 stations.

#### ROSS HULL MEMORIAL V.H.F.

Dates: 1st Dec, 1958, to 31st Jan, 1959.  
Bands: All v.h.f. bands.  
Rules: Same as for 1957.  
Special Award for greatest distance over 3,000 miles.

#### NATIONAL FIELD DAY:

Dates: Sunday, 23th January, 1959.  
Bands: (1) H.F. (2) V.H.F.  
Rules: To be published Dec. 1958.

#### BELT, C.W.:

Dates: Probably January, 1959.  
Rules: As for 1958.

#### OK DX CONTEST:

Date: December, 1958.  
Bands: All h.f. bands.

## FED. CONTEST COMMITTEE

The Contest Manager, Mr. Rex Richards, VKSDO, reports that all Certificates awarded to the winners of Contests to date have been posted. Any Australian contestant nominated for an award in the published results who has not yet received his Certificate should contact the F.C.C. immediately. The VK-ZL Contest is included.

Overseas awards may take some time to reach the recipients and a copy of the results was forwarded to each one about 10th Oct.

As this is the last VK-ZL Contest that this Committee will handle the results are extended to those Amateurs who made the Contest so popular with the overseas contestants. The compilation of all these results will be ready as your stamp is put VK-ZL land late the 1958 one.

You may have noticed that the Committee has standardised the form of the Rules for each Contest. If not, then take another look, and compare, say Rule 3, in the VK-ZL and the Field Day, when you will see how it has been done.

Whilst on the matter of the Field Day Contest, what about some really overwhelming participation in the Contest this time? The scope of the Contest has been widened and the Committee has made an all-out effort to attract you and YOU and YOU into taking part.

Make your plans now. —Chairman, F.C.C.

## FEDERAL AWARDS

### W.A.V.K.C.A. AWARD

The following are new members of this Award: WBSU, KMRH, WDKT, and LUSAQ.

Altogether, 98 Certificates have been issued.

### D.X.C.C. AWARD

The following are amendments to the current list:

C.w. Section: VK2KB, No. 16, 244 countries. Open Section: VK3UG, No. 4, 212 countries. Details of Credits: All Kermadec Island D.X.C.C. credits are deleted as at 31/8/58 because of the fact, already well established, that a significant number of QSL cards presented for credit had been in the "undisputed" category. We are, therefore, unable to give credit for contacts with ZL1ABZ.

Additional Countries: Consideration is currently being given to the adding of additional countries for the D.X.C.C. list. There are about a dozen of them to be added in due course. G Weynton, VK3XU, Manager.

## FEDERAL QSL BUREAU

The new address for the W7/K7 QSL Bureau is Salem Amateur Radio Club, Box 61, Salem, Oregon, U.S.A.

The Israel Amateur Radio Club, Box 4698, Tel Aviv, Israel, sends a further reminder of their Jubilee Marathon Contest which commenced on 24th April and ends on 31st October. The object is to work as many 4X4 stations as possible. Each 4X4 station can be contacted once an evening during any 24 hours. Each station sending in a log will receive a participation certificate.

On a recent QSL received by BERS154 from Jonathan Alvarez, M0AH, it is stated that John is spending most of his time nowadays on 14005 Kc. s.h., and only odd bursts on 14025 Kc. c.w. He adds that he is only four current licensed CR3 calls: 9AE, 9AH, 9AI, 9AC. CUBAF is now CTID and CRAL is now CTIB.

Aurora VK3YI, who has already received her card from FOAT, will be QRT during early September due to moving QTH. Her new address is 1444 Main St., East Malvern, and is 1377 Dandenong Road, East Malvern. Kipping up the shack at the new location has been a high priority.

Tom, VK3JTL, who made the Northern Territory contact for so many overseas aspirants for the W.A.V.K.C.A. award, writes from Perth, S.A. on Sunday, 24th of August, 1958, wishes it to be known here and abroad that he is no longer at Alice Springs. Tom has sent his card for credit for contacts made during his journey at the Alice. He ceased activity at that location on Feb. 7. Tom expects to settle down again at Renmark about the end of October. He ceased activity at his old band on a Type 22 and gave the VK3 Division great help during the recent R.D. Contest. Tom is receiving cards for contacts already made after he had QRT at Alice Springs. Tom adds that as far as he knows the only station in Northern Territory now active is VK3AE at Darwin.

The "A.M.P. DX Club" of Sweden is sponsoring a 1959 Low Frequency Award. A certificate will be available to any station in the world who runs up 80 points during 1959. One point is earned when contacting any country in the A.R.R.C. Codebook. The certificate must be made on the 40 or 80 metre bands. The cost of the certificate is 16 L.R.C. It is unnecessary to send confirmations, providing a list signed by a responsible member of your country's recognised Amateur Radio Society is submitted. Applications for the award should be made to the Swedish S.W. Hjalmarsson, Vallentuna, Sweden.

—Ray Jones, VK3JR, Manager.

## NEW SOUTH WALES

### HUNTER BANCH

Our popular Treasurer, Bill ECT, should be almost back from his trip to Orange-bloom, so I trust that he has taken an efficient photo to keep an s.b. lecturer at bay for another month. Bet he keeps two sections, one to show the Hunter boys and the other to show his s.b. lecturer. The s.b. lecturer was present at our social to bid Bill bon voyage, as a good-will gesture 24QR set him back home for the first time in a while for a long time, rumor has it that Bill's XYL got Alec 2ABU to be on the same ship to keep an eye on him.

## SILENT KEY

It is with deep regret that we record the passing of: VK3UI—A. (Alan) Rodger, 25th August, 1958. VK3VE—A. R. ("Bill") Williams, Fred Leader ("The Monitor"), of New Zealand, 9th August, '58.

Thirty-three chaps were in attendance at our August meeting to listen to Barry 2ZAG give a very interesting lecture on the practical aspects in the application of radio valves and also a dash of transistorised power supplies. The rapid fire of questions shot at Barry was indicative of the interest shown and naturally it was left to Stuart 2ZDF to move a vote of thanks to a "fellow v.h.f.-hound" on his words. Not only the boys present were 2ZJ, 2ZL, 2AGQ, 2AFA, 2CN, 2ANA, 2ADS, 2RJ, 2AOR, 2QZB, 2AEE 2XT, 2FP, 2CS, 2ZDF, 2ZK and associates Sutherland, O'Brien, Berkman, McLaughlin, Jackson, Price, Slobo, Davis, Nichol, Finch, Richardson, Bailey, Ward, Broad, Witherall and one unidentifiable signature. Two other chaps either missed the book or couldn't write.

Stan 2ZDL doing very well on 144, was 3 and in Sydney. The other night, however, several of the boys are contemplating coming up on this band, in fact if a better response to the L.T.U. Fund is not forthcoming, 144 may be all we will have left, that is of course until we have perfected the band and no doubt then we will again be told to shift.

Probably by the time you got this mag., our Dinner will be half eaten, but it will not be too late to get ready to amble forth on the Sunday to Blacklacks where an entertaining programme has been arranged.

The usual meeting of the Branch will be held at the University of Technology, Tighes Hill, Newcastle on Friday, 10th October, at 8 p.m., and the social "do" at 2XT's on Wednesday night 22nd October.

Any information or suggestions regarding the L.T.U. Fund can be got from me by phoning West Wallend 8 during business hours or 53 thereafter—2AQR.

## VICTORIA

Unfortunately for me the monthly meeting which is usually my only source of information for those notes was delayed a week this time owing to school holidays and copy is due before the meeting is held. However, the fervent entreatment of the notes on this account will serve a good purpose as space is required for the notes and the literary issue of our magazine. A truly fine effort for an organisation such as ours where voluntary effort is the order of the day.

However, despite this fine achievement, I feel that we are missing the bus somewhat in other directions as we don't seem to be conscious of our responsibilities in using the bands, even after several impassioned pleas by those who know what this means to the cause. The L.T.U. Fund results to date have been outstanding and it seems that the average chap has his hobby at heart, but there it seems to

end, because he doesn't bother to exercise his rights on the bands provided. You don't have to take my word for this. Just listen around any night or over the week-end when activity should be at its peak and what do you find? Yes, I know, commercials, but there are still a few spots left if you hang around. Don't blame officialdom for failing to see why we should be allowed to retain our allocation if we don't substantiate their claims to the space.

There is also another very important aspect to be considered in this matter and that is how it affects the newcomer to the band. We seem to leave nothing to be desired in catering for the prospective Ham in his efforts to get his ticket, but once through we leave him to his own devices. Their claims to the space, anyway, as we have a request from a new Ham for QSOs. His name is Gill Robinson (GVR) of Birmingham and he is looking for QSOs on 50, 60 and 20. Never let it be said that we can't meet this request.

While on the subject of personalities, the v.h.f. boys and no doubt many others will recall Quinton Porter (8IM), who left for overseas some months ago to further his studies. As a result of these later efforts he has now completed his Doctor of Science degree and we offer him our congratulations.

The next meeting will be held on 1st October when members of the Publications Committee will speak on the activities of this committee.

As you have heard on recent broadcasts, a committee is investigating the possibility of obtaining other accommodation for Divisional headquarters as it is anticipated that the rent for the present rooms will soon be too high. If such after restrictions are lifted next June. In order to test the feelings of members in this matter and to obtain guidance in carrying out the wishes of a majority of the members, Council has asked that the subject be thrown open for discussion at the October meeting. Your own opportunity to air your views on this very important question, so come prepared.

## SCOUTS LEARN OF HAM RADIO

On Wednesday, 27th August, three of the local Melbourne boys travestied in Eucalyptus Gully, about 80 miles from the city, to provide a demonstration of Ham Radio and Short Wave Listening for the 1st Upper Fernside Scout Group. They were Norm 2ZEU, Ian 2ZBP and Ian Hunt, Sec. of the S.W.I. Group. They were welcomed by the Scout-Master, Mr. Barrett, and Andy 2SM, the Scoutmaster, and eagerly by the Boy Scouts, about 20 in number. Ian Hunt opened the evening with a talk on what may be heard on the bands and demonstrated with the aid of his AMR300 rx. At the finish of his talk he distributed copies of an article on v.h.f. for their further guidance. By 10.15 the 2ZEU group was up and in operation. Ian Hunt then gave a short talk on Ham Radio and the big moment had arrived. Norm, with mobile gear in the car, took about five Scouts at a time for a drive around the locality, at the same time allowing them to talk back to their mates in the Scout Hall via the fixed station set up there. A wonderful time was had by all and a QSO with the Divisional President, JYB, was squeezed into the proceedings.

## WESTERN ZONE

Jim SAGE of Nopelton, who has recently built a higher powered rig, was working some nice DX. His best results have been obtained on the 21 Mc. band. Herb 3NN of Nopelton has been a active on the bands and has had some nice contacts there. Merv JAGO of Nopelton will spend his forthcoming annual leave in V.I. land, so we wish he and Norm an enjoyable holiday.

A Hobbies Exhibition will be held in Stawell beginning on 11th November, finishing on 15th

November. With the help of local Amateurs we expect to have a station operating from there during these times, so we will be happy to have as many contacts as possible.

## MOORABBIN AND DISTRICT RADIO CLUB

There has been improved activity on all bands in this district lately. Jack 8YT has been trying out his new wings on the "d.s." bands with 120 watts to 4140, and has even been heard mentioning DX contacts. (It's all been

## OBITUARY

### M. A. (ALAN) RODGER, VK8UI

It is with sadness we learn of the death of Alan VK8UI, licensed sea-war, Alan served in the Royal Australian Navy as a Radio Operator. His main interest was in v.h.f. work, where his patience and good operating were rewarded with some notable "firsts," both home station and portable on field days. As a W.I.A. member, he has been President of the N.E. Zone of the Victorian Division.



Unmarried, Alan is survived by his mother and sister, to whom we extend our most sincere sympathy.

### FRED LEADER—"THE MONITOR"

It is with deep and sincere regret that we record the passing of possibly the best known listener member of N.Z.A.R.T., Frederick Arthur Leader. Fred, known to Amateurs throughout Australasia in particular as the "Monitor", passed peacefully away on Friday, 9th August, last after celebrating his 84th birthday on the previous Monday.

Fred had been a member of the Association since 1931. He was elected as a member of the Executive Council in 1948 and in June 1949 at the Annual Conference he was made a Life Member of N.Z.A.R.T.

Life Member of N.Z.A.R.T. was the first and so far the only listener member to be so honoured. He was also an honorary member of the Victorian Division. Born in Bristol, Fred came to New Zealand in 1919 and became interested in Radio in 1928 since which date he became known to many as the "Monitor". In his friendly reports. His election to Life Membership of N.Z.A.R.T. an honour reserved for few, was an indication of the high esteem in which he was held and of the outstanding work he had done for the Association over the years. He not only followed his hobby in a practical manner, but his voluminous listener reports testify that he also interested himself in the Amateur's family and hence Fred's periodic trips around New Zealand—often accompanied by Monty "The Pilot" left a trail of good-will and friendship behind him with old time courtesy to XYLs or children.

The funeral service was conducted on Tuesday, 11th August, by Rev. Roy Campbell 2ZJED, who came from Wanganui especially for the service accompanied by Past President Chas. Barry, 2ZBYB. The service was well attended by a representative gathering which included many Radio Amateurs, not only from Auckland but from other parts of the North Island. Pay-bearers included Fred's old friend "The Pilot" and President Jack Freeman, 2ZLVA, on behalf of the Association.

Fred's wife, Fredette, died some years ago and he had no relatives in N.Z. To his many friends we express our deepest sympathy.

## WIRELESS INSTITUTE OF AUS. HUNTER BRANCH, N.S.W. DIV.



SEVENTH ANNUAL  
**CONVENTION**  
SATURDAY AND SUNDAY,  
4th and 5th OCTOBER, 1958

Canberra Radio Society and  
South Western Zone, W.I.A.

present

.6th SOUTH WEST. ZONE  
AMATEUR RADIO  
**CONVENTION**  
at  
CANBERRA, A.C.T.  
4th and 5th OCTOBER, 1958  
to be held at the Canberra Club  
House, Riverside, Canberra.

## W.I.A. VICTORIAN DIVISION



**SOUTH WESTERN ZONE  
CONVENTION**  
will be held at  
**BALLARAT**  
on  
**SATURDAY AND SUNDAY**  
**NOVEMBER 15-16, 1958**  
Enquiries to Brian Stars, VK3ZBS

## "WILLIS" CHASSIS PUNCHES



3/8"	21/-	1-3/16"	35/-
1/2"	22/6	1-1/4"	42/6
5/8"	22/6	1-3/8"	47/6
1 1/16"	23/6	1-1/2"	47/6
3/4"	24/6	1-3/4"	57/6
1 1/8"	33/6	2"	62/6

Any special size requirements made to order.

## Q-MAX SCREW-TYPE CHASSIS CUTTERS

5/8"	28/7	1-3/8"	38/6
3/4"	28/7	1-1/2"	38/6
7/8"	29/4	1-3/4"	42/-
1"	34/10	2-3/32"	68/9
1 1/8"	34/10	2-1/2"	81/7
1 1/4"	34/10	1" Square	52/8

One key supplied with each cutter. Spare keys 1/8 each.

## PI-COUPLER FOR HIGHER POWER

Compact, bandswitched, high power pi-coupler inductor for co-ax output. Rated for a max. 1,200v. d.c. at 500 ma. input. Higher voltages on c.w. and a.s.b. For max. efficiency the 10-metre coil is made of 1/2 in. silver-plated strip, 15 and 20-metre coils of 1/8 in. silver-plated wire, and the 40 and 80-metre coils of 12 B & S. tinned-copper wire.

Input capacity 250 pF. max., output capacity 1,500 pF. max. A single pole five-position switch is provided which can be used for switching in parallel capacities when required.

Recommended input capacitor Eddystone Type #17 Recommended output capacitor Standard miniature 3-Zeng BC condenser which is suitable in this position up to 1 kw.

Price: £4/17/6 nett

**WILLIAM WILLIS & Co. Pty. Ltd.** extends its hearty congratulations and best wishes upon the 25th ANNIVERSARY of the W.I.A. magazine, "AMATEUR RADIO."

With Typical Precision Engineering and Calibration Accuracy comes the GRUNDIG Model 701

## GRID DIP OSCILLATOR

- Continuous frequency coverage from 1.7 Mc. to 150 Mc.
- Operates on 110/220v. a.s., 40 to 60 cycle mains.

Price: £33/15/0 (incl. Sales Tax)

Dress your Rig with **INDICATOR BEZELS** Bulgin Type D170

3/9 each

Available in -  
Red  
Green  
Blue  
Amber  
Clear



LST No P 240

## MAINS CONNECTORS

Bulgin Type P73, similar to illustration. Flush 3-Pin Plug and Socket. Ideal for any equipment, 7/- each.

## GELOSO PI-COUPLER

Another winner for the Amateur. The answer to TVI and antenna matching. Will match any impedance from 40 to 1,000 ohms over 80 to 10 metre Amateur bands.

Price (inc. tax): 31/6

## VFO's FOR THE A.O.C.P. AND LIMITED A.O.C.P. LICENSE HOLDER

### MODEL 4/103 V.F.O. UNIT EXCITER

Freq. Range: 144-148 Mc.

R.F. Power Output, Sufficient to drive an 885 or 5753

Valve Line-Up: Two 6CL6 oscillator multipliers, one 12AT7 multiplier, one 5753 driver.

The unit incorporates two different oscillator multipliers, one variable for establishing communication, one crystal-controlled fixed frequency oscillator for driving.

Price: £12/1/11

### MODEL 4/104 V.F.O. UNIT EXCITER


Six Bands: 80, 40, 20, 15, 11, and 10 metres.

R.F. Power Output Sufficient to drive one 807 or 5148 for phone or c.w.


Valve Line-Up: 6CL6 oscillator, 5753 driver.

This is an oscillator exciter of high stability, because of its conveniently selected C/L ratio and the 6CL6 oscillator tube employed.


Price: £10/19/5

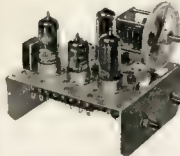


4/103 V.F.O. UNIT EXCITER

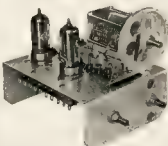

4/104 V.F.O. 6-BAND UNIT EXCITER

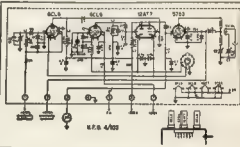

CIRCUIT DIAGRAM FOR 4/103

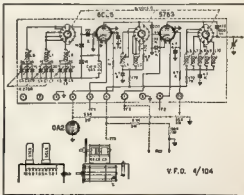

CIRCUIT DIAGRAM FOR 4/104

THE HOUSE OF  
QUALITY PRODUCTS  
Phone: MU 2426

**WILLIAM WILLIS**

& CO. PTY. LTD. 428 BOURKE STREET,  
MELBOURNE, C.I,  
VICTORIA



e 55

by the same thing in his tx. Finally after fixing these two items a short in the key click after a bit of business. Wal 817 still in bother with his modulator, so comes up on c.w., not many takers he finds, a good 79 note, W.

The W.I.C.E.N. boys still hard at practice and improving each time, they have been keen enough to go out into the hills districts, on very hot and very cold nights, to test sites, frequencies, etc., and carry out exercises. Some talk of possibly trying out v.h.f., so you take it from there Neil.

## WESTERN AUSTRALIA

The August meeting of the Division was well attended, a feature of the meeting being the auction of the late Fred Tredrea's books. A visitor to the meeting was Herb 6XO, of Kalbarning. Herb had just received his license papers and call sign, and had a rig at home all ready to fire up. Since then, most of the new frequency boys have enjoyed 6XOs with Herb. Also in Kalbarning and just about ready to go is 6XKR. Best of luck there, boys.

In place of having a full-sized lecture by a guest speaker during the meeting, we are trying new ideas having short lectures, dealing with topics, purely Ham. BBE was the speaker at the August meeting, his subject being 'The Tale of the Ham'. The speaker was GRP (problems associated with using 6146), and 6KW (building out modulators). Comments so far have been very favourable. You would like to see this particular Ham's work, no matter how elementary it may be, let us know and we'll see what we can do.

Another OT in John 6GB has re-appeared on 40 and 80 m. Jack has been exclusively v.h.f. for many years, but has now completed a Gelsco controlled rig. Heard Jack renewing acquaintance with 6WL the other night. Only needed 6N to complete the trip.

Bernie 8KJ has just finished a "mobile" holiday. Some of the boys worked him all the way round on his trip, Albany-Perth-Miling-Perth-Albany-Albany. Bernie's reward was 10 19 did a very nice job on the trip, apart from a little trouble which was located and cleared up during Bernie's stay with 6CL and XYL.

The R.D. Contest has come and gone again, but this time VK8 is not quite so confident of success. The contest was held on 20th and 21st, very close result. VK8 operators scored very heavily, while relatively poor conditions on 80 early on the Saturday night, plus the absence of two top scorers, 6GTH and 6PDL, told against VK8. Remarks have been made in the high standard of operating in the Contest this year, apart from the usual few people who think they can get through on the modulator alone (known as "Winding up the Wick"). Unfortunately, the extra points gained by these boys are lost by their fellows who can't copy through the GRM.

6GTH has been absent on business in Sharks Bay, unfortunately missing the Contest. Since his return, Tom has a pit tank in his final rig and I hear it is working out very well.

The Slow Morse Transmissions have resumed now that BBE is back at work. If you're interested in Slow Morse, get in touch on Wednesday night.

The 6 m. gang has been watching anxiously for a sign of life from the 6 m. gang. It is a pity that since reports have been received that 4NG and company are into the DX again. Living in the tropics has some compensations compared with even like the climate! Good luck to you anyway, boys, even if we're a little envious.

A funny story: S.W.I. (now passed ticket) was visiting a VK8 shack. On

one chair was the remains of a long defunct TAID; on another was a cage, complete with a pink and grey zebra. S.W.I. bends over to examine the remains; Cocky eyes the expanse of tightly stretched trouser and, ever an opportunist, he says, "What a beautiful sight the matter." S.W.I. straightens up with a howl of anguish, and turns to see what has attacked him. Cocky just looks at him with one eye and says nothing! . . . . .

## TASMANIA

### NORTH WESTERN ZONE

Well chaps, another R.D. Contest has come and gone with its usual crop of breakdowns; minor and otherwise. The boys, however, of the locals plugging away steadily. One, I won't mention names, reported that he went to sleep and forgot the Contest, so made a late start.

At our August meeting a new associate was welcomed in the person of David Waldon, another reinforcement for Ulverston. How is the Morse going David?

On August 13 about nine associates gathered at the home of Jim 7ZO, where they were solidly thrashed on the subjects the examiners reveal in. Our worthy Secretary looked longingly at Jim's rig and dreamed of the time when he would be able to get his hands on it. XYL turned on a lovely supper as a final to Ohm's Law, etc. Once again our thanks to you and your wife for the very good time the boys benefited greatly. On Aug. 21 Max lives, John Lee and myself got together on some more. Practice must be kept up at all costs.

At the moment of writing yours truly is in VK3-land returning from Sydney where I visited some of the boys. I was very busy. Boys! did I walk some miles. Those stores are scattered and Sydney is a big place. I am afraid their goods are easier to locate by reading advertisements, mainly bug piles of equipment. Melbourne stores proved much the same, but with higher prices. Broadcast reception here on the mainland is not as good as at home, but the boys have something very useful; so I suppose we have something to be thankful for in our location.

I trust all the hopeful associates got their applications accepted. I have a bag of luck chaps, I hope we all pass OK, then there'll be some difficulty finding a clear spot on the bands for us.

Several committee members met the Burnie Fire Brigade in August to discuss two-way radio equipment for Brigade vehicles. I guess we will hear about this in the near future.

Had a yarn to Max 32Z whilst in Melbourne, also Dave 2AYE, main topic being the I.T.U. Conference. They both stressed the importance of sending a representative, so don't forget your contributions, please.

Saw another t.v. set like yours Syd, covered just as great an area, too.

Many Happy Returns to -"A.R."

## PAPUA-NEW GUINEA

We are back on deck this month after the mud run getting ready for the R.D. Contest; the XYL is very pleased, she can walk into the lounge again without falling over her ears of rig. By the time this goes to press Bob 9BS will be back from the bush and possibly back on the air. The time he was in the bush he was in the bush. Roy 8J has left Wewak and is now stationed in Port Moresby. We hope to see you take an active part in the doings of the Division Roy, and when you get settled in, get settled in. In the Sunday hook-up at 8.30 a.m. Bob Murphy will be travelling round in the future and will be in use for about three months, and also in Mangrove for the same period. Bob has bought an SX300 and reckons it's the goods. Another Bob, B.A., is on leave at present and will be bringing a new SX300. This will be a new SX300 that neat Viking Ranger Bob and by the way, it's time that conical quid was taken out of the lounge. J. Whitaker. He has been very quiet of late and you know why. He has set up a ringer on the roof and a television rx in the lounge and just sits staring, sure he has heard it. Hope to hear from you soon, but as yet there has been no pretties to look at. I think you better give it away and come back on the air; it won't be such a strain on the eyes.

Eddie 8AT is back from leave and has been transferred to Garoka. Hope to hear your yellow voice again on Saturday. S.W.I. says, "how is your t.v. going?" Doug 9DB has learned to play golf at last and once again can be heard on the bands occasionally. Another change has been made by the boys who has been off the air for about 13 months, and has just built a table-top rig using a

Geloso and reckons he'll have a tri-band quad in operation for the VK-ZL Contest. Red 88P is down south, having a spot of leave at present. Also down that way is Bill 9WP. Cur Secretary, Peter 8PO, is back on his feet again after his recent illness and we trust you don't have any more bad luck. Another old member, Charlie 8WG, has also been in hospital recently with a bad leg complaint. The birds talk me he is doing sound, shortly to recuperate. We wish you all the best, Charlie, and hope it won't be long until you are your old self again.

Well chaps, that's it for this month, and remember the meeting night is the last Wed. night of the month and the Sunday broadcast and hook-up is on every Sunday at 8.30 and on both 7 and 14 Mc. We'll be looking round for you.

## HAMADS

1/- per line, minimum 3/-

Advertisements under this heading will only be accepted from Institute Members who desire to dispose of equipment which is their own personal property. Copy must be received by 8th August. No advertising or testimonials may accompany advertisement. Calculation of cost is based on an average of six words a line. Dealers' advertisements not accepted in this column.

**FOR SALE:** Conv. 50-65 Mc, out 7 Mc. Also Heathkit Q Multiplier, £10 each. K. Hughes, 42 George St, Oakleigh, Vic. UM 4964.

**FOR SALE:** Freq. Meter, "Zenith," crystal controlled, Type BC212T, three valves, new condition. G. H. Choules, 26 Donald St., Ashburton, Vic. BL 1854.

**PANDA** Table Top 150 watt Tx, self contained Modulator and Power Supply with accessories. Best offer. Halli-cracker 540A Receiver, £45. National NC46 Receiver, £35. 15 metre Crystal Converter, £10. Enquiries 11 Gleeson Ave., Burwood, Vic. BX 7609.

**SELL:** Complete power supply, AT21, 650v, 0.350 amp, 300v, reg. dec., 60v, and 12.6v. Built-in time delay and keying circuits, cables and circuit, £22/10/0. RME DB23 Pre-selector, 80, 0, 20, 15, 10, three 6J6s as grounded grid triodes, circuit manual supplied, £17/10/0. Both in perfect condition. L. Frith, 49 Lynton Street, Glenroy, W.9, Vic.

**SELL:** Modulator: 6SJ7, 6J5, tran. coupled 2A3s, 600s (or 811s), Trimax 150w, mod. tran. and driver, shielded hook-up wire used and heavy built best components. Power Supply (on separate chassis): 600, at 300 mA. with 806As 350v, at 150 mA.; filament transf. and chokes; all power components special orders when built; mod. and pwr. firmly including tubes and some spares, £35. Further details on request. Dural Cubing: 6 x 16 ft. lengths 1 inch x 17g., £10 the lot. J. K. Herd, Reid Street, Wangarata, Vic.

**WANTED:** EC-348 Repair Manual. L. Pinkewitch, 30 Buchanan Street, Newcastle, N.S.W.

**WANTED:** May 1956 "QST". H. Webster, 3 Kharotum Street, Caulfield, Vic. UY 8023.

**WANTED:** Prop. Pitch Motor, J. A. Mitchell, C/o. Cann's, Albury, N.S.W.

**WANTED:** Urgently, Circuit, Data, Modifications and Handbook of MN26H Bendix Compass Receiver. Price and Particulars to B. J. Booth, 229 Hanson Road, Athol Park, South Aus.

### Coil Formers and Slugs

TV type, single, unscreened	1/-
Single, in can	2/-
Double, in can	3/-

All slugs 6 mm. diam., formers 5/16 inch approx.

Specify operating frequency so correct slugs can be fitted.

Postage 1/- Packet.

Limited Quantity Available.

**S. T. CLARK**

68 Jensen Rd., N.18, Vic. JU 6140

# Homecraft

EVERYTHING IN RADIO AND TELEVISION

**CONQUEST — The New**  
Cellaro 4-Speed Automatic  
Record Changer, £18/17/6.

**Q PLUS CRYSTAL SET**  
Complete with headphones and  
aerial ..... £4/10/6

**PARTS FOR "R. & H." TV**  
CH51 Horizontal Line Wave  
Coil ..... 8/7  
CHW1 Horizontal Width Coil, 12/1  
CHW2 Horizontal Width Coil, 12/1  
CHL1 Horizontal Linearity  
Coil ..... 9/8  
T511B Horizontal Blocking Oscil-  
lator Transformer ..... 10/4  
THO1 E.H.T. Transformer, £3/1/1  
THO2 (4 deg.) E.H.T. Trans-  
former ..... £8/0/0  
YND1 10 deg. Deflection Yoke  
£4/12/3  
YND2 90 deg. Deflection Yoke  
£4/12/3  
And all other parts, including  
Chassis and E.H.T. Boxes.

## VARIABLE CAPACITORS

**ROBLAN MIDGET—**  
Single gang ..... 31/-  
2-gang RMG2 ..... 39/-  
2-gang RMG3 ..... 39/-  
2-gang vernier drive ..... 36/-  
2-gang vernier drive ..... 41/-  
2-gang FM ..... 37/-  
**A.W.A. STANDARD—**  
Single gang ..... 31/-  
2-gang ..... 39/-  
2-gang ..... 39/-  
2-gang ..... 39/-  
**A.W.A. MIDGET—**  
2-gang ..... 36/-  
2-gang ..... 37/0  
R.C.S. 100 p.p. Reaction  
Capacitor CV40 ..... 17/9

## ROLA LOUSPEAKERS

3C	£1/13/0	8M	£2/3/0
4C	£1/11/6	12-O	£6/9/0
4F	£3/1/0	12-O De Luxe	£6/9/0
4-3F	£2/9/0		£6/19/0
5C	£1/13/0	12-MX, twin	
5F	£2/5/6	cone, £6/18/6	
5FX	£2/5/6	cone, £11/4/0	
5-TH	£2/8/0	12-OK, twin	
5-L	£2/3/6	cone, £11/4/0	
5-TH	£2/9/0	12UX HI-FI, 15	
6M	£2/18/6	ohm V.C.	
6MFA	£2/3/0	£2/18/6	

"Macron" Crystal Pick-up Car-  
tridge with 2 sapphire styl. Ideal  
replacement for any P.-up, 45/-

**SAPPHIRE REPLACEMENT**  
STYLIE to suit Cellaro, BSR, Gar-  
rett, velvet action record chang-  
ers and players, easy to fit yourself  
55/6 each.

**DIAMOND STYLIE** for Cellaro,  
BSR, Garrard players and chang-  
ers ..... £7  
P.T. Dual players and changers  
std. sapphire, LP diamond £7/11/6

The world's best **CELLARO**  
3-SPEED TAP DECK with  
4 HI-FI Heads ..... £22/19/6

**DUAL 1965 HI-FI** fully automatic  
4-speed Changer ..... £37/9/6

## DUCCON HIGH-SEAL TUBULAR CAPACITORS

0.001, 600	1/2	0.22, 200	2/-
0.002, 600	1/2	0.27, 200	2/5
0.003, 600	1/2	0.37, 600	2/5
0.004, 600	1/2	0.37, 600	3/2
0.01, 200	1/2	0.47, 200	3/2
0.01, 400	1/2	0.47, 400	3/2
0.02, 600	1/2	0.47, 600	3/2
0.1, 200	1/2	0.56, 200	4/2
0.1, 400	1/2	0.56, 400	4/2
0.1, 600	2/-		

## ELECTROLYTICS

8 mfd., 125v.	5/-
8 mfd., 350v.	5/1
8 mfd., 325v.	5/6
8 mfd., 600v.	6/5
16 mfd., 350v.	6/5
16 mfd., 325v.	7/4
16 mfd., 600v.	8/6
24 mfd., 350v.	6/9
24 mfd., 325v.	8/9
24 mfd., 600v.	10/-
32 mfd., 350v.	7/4
32 mfd., 325v.	12/2
32 mfd., 600v.	7/6
100 mfd., 40v.	6/4
30 mfd., 40v.	4/1
25 mfd., 40v.	4/1
250 mfd., 12v.	6/1
1000 mfd., 12v.	10/-

**METAL METER BOXES**  
Large 7 1/2 x 2 1/2 inches 20/8  
Med. 6 1/2 x 3 1/2 inches 17/8  
Small—5 1/2 x 3 1/2 inches 15/1  
12 1/2% Sales Tax to be added.

One only used by 16 inch Turn-  
table and Overhead Cutter, £5  
each ..... £25/0/0

## TV INSTALLATION ACCESSORIES

No. 1 Chimney Bracket Kit, single wire type	55/8
No. 3 Chimney Bracket Kit, single strap type	38/6
No. 4 Chimney Bracket Kit, double strap type	73/7
Acme Flash Wall Outlet	4/3
Skyline slid. Wall Outlet	6/9
Nail type Stand-off Insula- tors, per dozen	18/-
Must type Stand-off Insula- tors, per dozen	30/-
Wood Screw type Stand-off Insulators, per dozen	21/-
Gutter Clips, each	1/-
TV Lightning Arrestor	16/8

**Q PLUS HIGH IMPEDANCE HEADPHONES** ..... 41/-  
Custom built 5 WATT AUDIO  
AMPLIFIER, complete with 12 in.  
speakers ..... £19/19/6

Call in and see our Mr. S. Hurrey. Let him solve  
your HI-FI problems for you! We are suppliers of  
LEAK, QUAD, WHARFDALE, ORTOFON, FERRO-  
GRAPH, and STEREOGRAPHIC equipment.

**Cellaro HI-FI Transcription Turn-  
table with P.X. P.-up** ..... £31/3/0

## ZEPHYR HIGH QUALITY MICROPHONES

3XA gen. purpose Crystal	£5/8/7
4XA gen. purpose Crystal	£6/3/4
4XA tilting head, hand or stand	£11/11/11
10XA tilting head, chromium cased Microphone	£8/15/6
12XAD lapel type Crystal	£13/11/11
14CS carbon hand mike with off switch	£4/9/3
18XA Dual Cell high quality Crystal Microphone	£14/9/0
30CR Ribbon Studio Mike	£16/11/8
65MA P.A. Dynamic Microphone, high impedance	£12/9/7
65MD P.A. Dynamic Microphone, 50 ohm	£8/1/10
6 inch Mike Desk Stand	17/3
9 inch Mike Desk Stand	19/3
9 inch Flexible Mike Arm	£12/12/1
P/1511 Mike Rest Plate, £2/9/0	
Instrument Knob with numbered flange, 0-10	5/5
Instrument Knob with numbered flange, 0-12	5/5
Oval Desk Stand with on-off switch	£3/9/8
Bonquet Stand, 15 to 30 inches high	£4/2/0

## ZEPHYR MATRIX BOARDS

P/N229 12 holes x 11 inches	1/11
P/N289 6 holes x 6 inch long 3/10	
P/N281 6 holes x 9 inch long 4/3	
P/N282 6 holes x 12 inch long 8/4	
P/N283 6 holes x 26 inch long 16/1	
P/N284 7 holes x 11 inches long 2/3	
P/N285 7 holes x 8 inch long 4/11	
P/N286 7 holes x 9 inch long 7/1	
P/N287 7 holes x 12 inch long 9/7	
P/N288 7 holes x 36 inch long 19/7	
P/N289 9 holes x 11 holes long 2/6	
P/N290 9 holes x 6 inch long 4/11	
P/N271 9 holes x 9 inch long 5/7	
P/N272 9 holes x 12 inch long 10/11	
P/N273 9 holes x 36 inch long 23/11	

All Matrix Boards are made from  
High Grade Bakelite.

"AVO" precision built pocket size  
Multimeter, sensitivity 10,000  
ohms per volt, only ..... £11

## PARTS FOR TRANSISTOR PORTABLE

Complete Collis Kit including printed circuit and loop stick	£5/14/6
Subminiature Elec. Capacitors, 5/2	
0.1 and 0.05 u.f. Ceramic Disk, 1/2	
2N525 Transistor	35/6
2N526 Transistor	35/6
2N151 (OC70) Transistor	28/10
TS2 (OC71) Transistor	29/8
2 x 2N155 Transistor	£3/5/6
GD4 Diodes	6/2
CZ9 Terminals	2/11

## AMATEURS' BARGAIN CENTRE

**COLLAARO, 4-Speed Record  
Player, £12/10/0**

## HOME CONSTRUCTORS' SPECIALS

Jabel N2 planetary drives	10/6
Jabel dial scale assy. for N2 drive	28/-
Zephyr front-loading fuse holders	5/5
1-3 amp. amp. bases for p.kts. of 3, 5/7	
Buron crystal set colla, N1,	9/-
Buron crystal set colla, N2,	9/3
Buron Reinartz colla	12/9
Q Plus WFL1, 10 Kc. whistle filter	11/9
RCS 1 1/4 in. 6-pin plug-in coil	2/9
Q Plus coil dope	3/3
Nylon dial cord, 25 yd. reel, 13/0	
Q Plus single slide D/W bracket	165/-
Q Plus RF stage D.W.	108/-
PN351 noise suppressors	14/4
2 x 0.1 mfd.	15/4
BSR HFMF motor only (BSB, AC)	£13/0/0
Nema test pencils	10/-
Zephyr 4XA crystal microphone	44/7
A2 1/4 inch grommets, 3/8 per doz.	13/7
Telephone cords	13/7
Crystalline transformers	3/1
Small pointer knobs	1/5
Large pointer knobs	2/5
Amphenol 4, 5, 6, 7, 8 pin plugs	3/8
Plug covers	2/5
Teletron 4-pin min. plugs	1/3
Teletone 4-pin min. sockets	1/3
Scops AC-DC 6v. 5 seconds soldering iron	£19/10/0
Scops transformer	49/1
1/8, 5/32, 3/16 in. spin bits, 11/6	
P.V.C. Hook-up wire (ass. colours) 1 lb.	£13/0/0
Single shielded hook-up wire,	2/1 per yd.
Twin shielded hook-up wire	3/1 per yd.
Single shielded thin hook-up wire	1/5 per yd.
Tinned copper wire, 16, 20, 22 SWG (1 lb. reel), 16/3	
18, 20, 22, 24, 26, 28, 30, 32 B. & S. enamelled wire, 4 oz. reels, 10/6	
Multi-core solder	1/- per yd.
Test probes flexible flex (red or black)	4/8 per yd.
TV aerial 300 ohm twin ribbon	1/1 per yd.
Small alligator clip with screw,	11d. ea.
220 ohm/2 ohm line transformer, brand new	16/10
Zephyr 6 in. table mike	16/10
V237 6v. non sync. vibrators, 30/3	
V238 12v. non sync. vibrators, 30/3	
On-plan potentiometers, from 10K to 2 meg.	7/4
Duccon detectors, with 12v. coil 1500K and 1 meg., 31/10	
Philips latest Valve Manual	3/0
Philips air trimmers, 3-30 pf. 4/6	
Jabel compression trimmers	1/3

## TV CONSTRUCTOR PARTS

Philips Turret Tuner	£18/0/0
Phicos detectors and focusing assembly	£6/4/0
Picture Tube sockets	5/5
Teletone 4-pin min. sockets	1/3
17 in. or 21 in. E.H.T. Assy.	25/10
Astor Turret Tuner	£19/15/0
T123 frame out (former, 30/3)	
T125 line blocking (former, 14/3)	
T126 p.c. line transformer, 32/6	
T110 616 choke	25/0
A.W.A. Roster components for T11P413 tube	£13/9/6

290 LONSDALE STREET, MELBOURNE

FB 3711


# 3 GELOSO V.F.O. UNITS

## for the Amateur
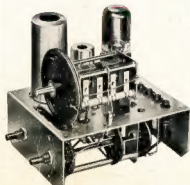
### MODEL 4/102 V.F.O. UNIT EXCITER

Five Bands: 80, 40, 20, 15, 10 metres  
Using 6J5, 6AU6 and 6L6 Valves

- Instant change of frequency on any band by coil switching.
- Controllable output over entire tuning band.
- Single control full bandspread on each band.
- Capacitive output.
- Utmost frequency stability (plus or minus 200 c.p.s. on all bands).
- No plug-in coils required.
- Laboratory tested.
- Power supply required: 400 volts at 32-54 Ma.



4/102 V.F.O. UNIT EXCITER


### MODEL 4/103 V.F.O. UNIT EXCITER

Freq. Range: 144-148 Mc.

R.F. Power Output: Sufficient to drive an 832 or 223B.

Valve Line-Up: Two 6CL6 oscillator multipliers, one 12AT7 multiplier, one 5763 driver.

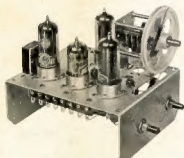The unit incorporates two different oscillator multipliers, one variable for establishing communication, one crystal-controlled fixed frequency oscillator for working.



4/103 V.F.O. UNIT EXCITER


### MODEL 4/104 V.F.O. UNIT EXCITER

Six Bands: 80, 40, 20, 15, 11, and 10 metres.

R.F. Power Output: Sufficient to drive one 807 or 6145 for phone or c.w.

Valve Line-Up: 6CL6 oscillator, 5763 driver.

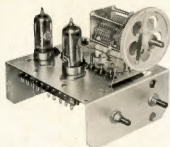This is an oscillator exciter of high stability, because of its conveniently selected C/L ratio and the 6CL6 oscillator tube employed.



4/104 V.F.O. 6-BAND UNIT EXCITER

### REVISED PRICES


(1st September, 1958)

(Incl. Sales Tax; excluding Valves)


4/102 ..... £10/4/9

4/103 ..... £12/1/11

4/104 ..... £10/19/5

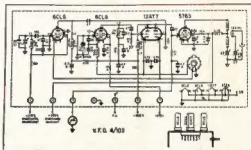

CIRCUIT DIAGRAM FOR 4/103

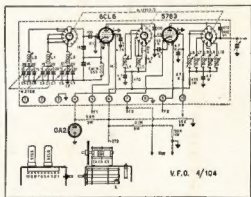

CIRCUIT DIAGRAM FOR 4/104

SEE YOUR REGULAR WHOLESALE NOW!

Sole Australian Factory  
Representatives:

**R. H. CUNNINGHAM PTY. LTD.**

8 BROMHAM PLACE, RICHMOND, E.1, VIC. Phone: JB 1614. Cable: "Cunnig" Melbourne.  
16 ANGAS ST., MEADOWBANK, N.S.W. Phones: WY 0316, WY 3852. Cable: "Cunnig" Sydney.